
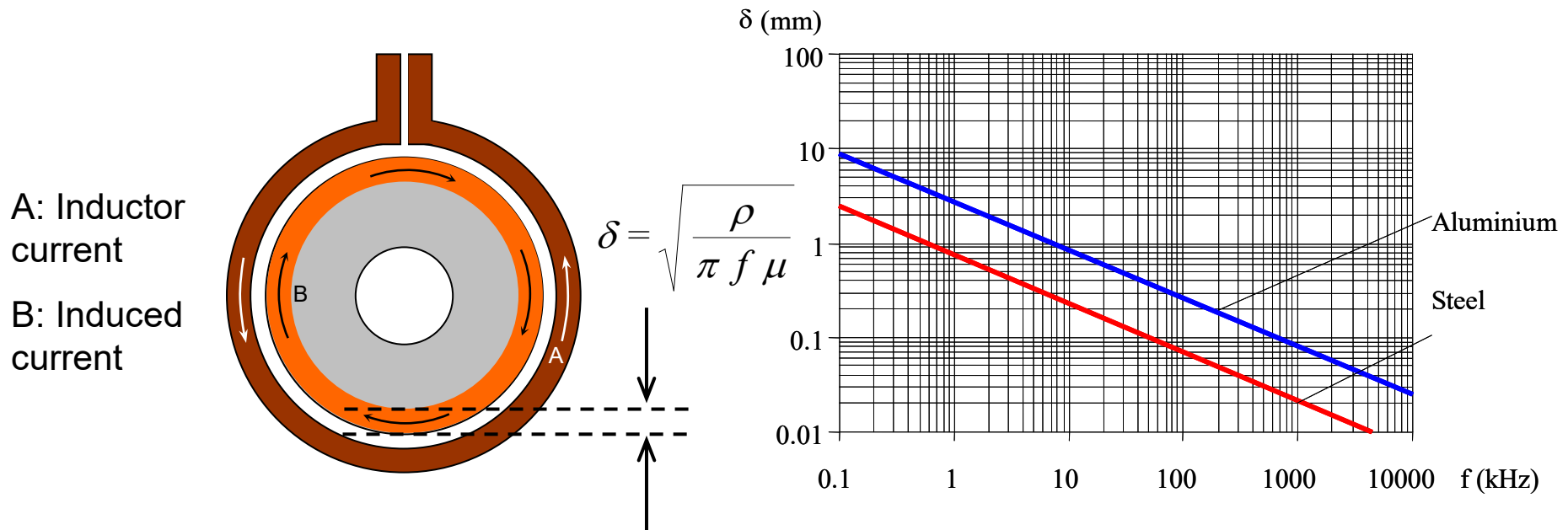


POWER CONVERTERS FOR INDUSTRIAL INDUCTION HEATING APPLICATIONS

Vicente Esteve


Department of Electronic Engineering
ETSE, University of Valencia
Av Universitat s/n, 6100 Burjassot, Spain
e-mail: vesteveg@uv.es

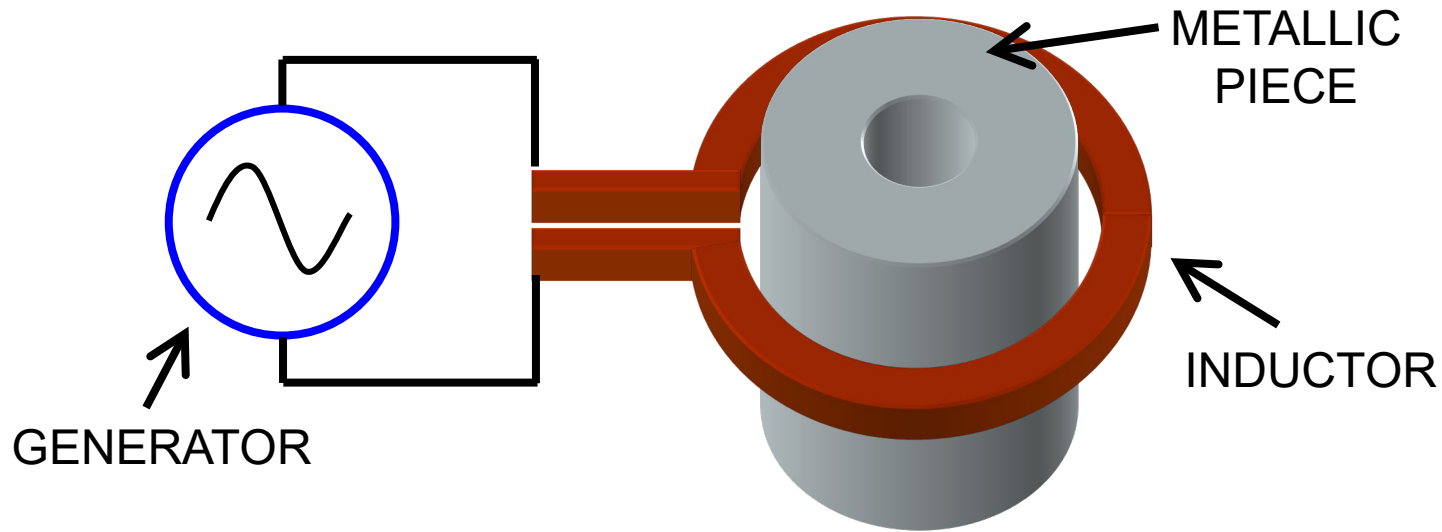- ✓ Basic Concepts in Induction Heating
- ✓ Compensation of the Load
- ✓ Series Resonant Converters for IH
- ✓ Parallel Resonant Converters for IH
- ✓ Semiconductors used in IH
- ✓ Applications
 - ✓ Forging
 - ✓ Hardening
 - ✓ Multipurpose Generators
 - ✓ Bonding
 - ✓ Welders
- ✓ Controllers
- ✓ Roadmap



- ✓ Basic Concepts in Induction Heating
- ✓ **Compensation of the Load**
- ✓ Series Resonant Converters for IH
- ✓ Parallel Resonant Converters for IH
- ✓ Semiconductors used in IH
- ✓ Applications
 - ✓ Forging
 - ✓ Hardening
 - ✓ Multipurpose Generators
 - ✓ Bonding
 - ✓ Welders
- ✓ Controllers
- ✓ Roadmap


• PARALLEL COMPENSATION:

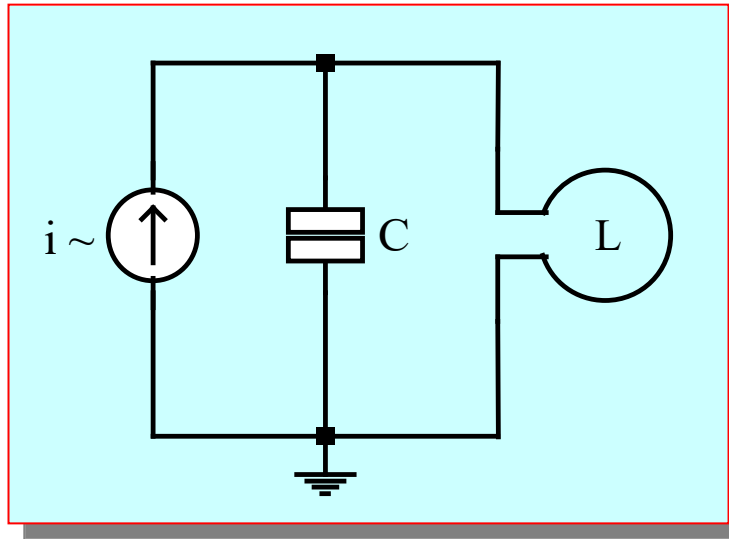

CURRENT-FED


$$P = \frac{i^2}{2} \operatorname{Re}(Z)$$

• SERIES COMPENSATION:

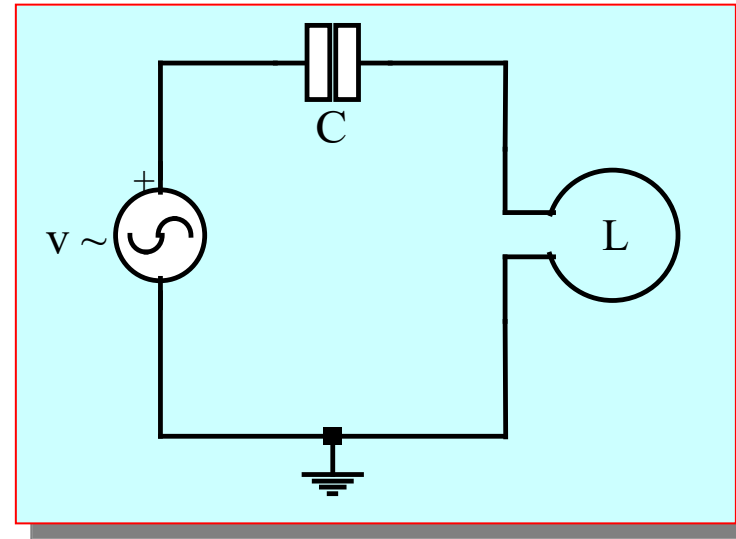

VOLTAGE-FED
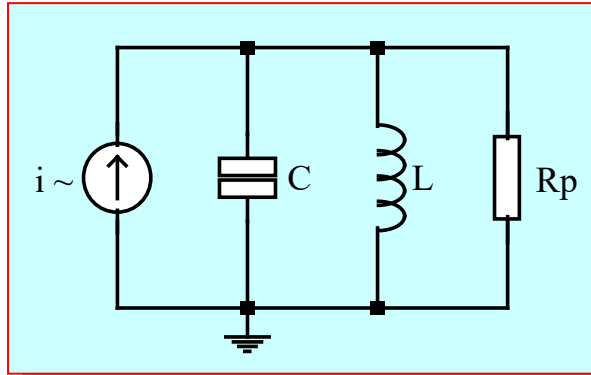
$$P = \frac{v^2}{2} \operatorname{Re}(Y)$$



$$Z(j\omega) = \frac{R_p}{1 + jQ\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)} = \text{Re}\{Z(j\omega)\} + j\text{Im}\{Z(j\omega)\}$$


$$\varphi = \arg\{Z\} = -\arg\{Z^{-1}\} = -\text{atan} Q\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right) \Rightarrow \tan \varphi = -Q\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)$$

$$Z = \frac{R_p}{1 - j \tan \varphi}$$


$$|Z| = \frac{R_p}{\sqrt{1 + \tan^2 \varphi}} = R_p \cos \varphi$$

$$\text{Re}\{Z\} = \frac{R_p}{1 + \tan^2 \varphi} = R_p \cos^2 \varphi$$
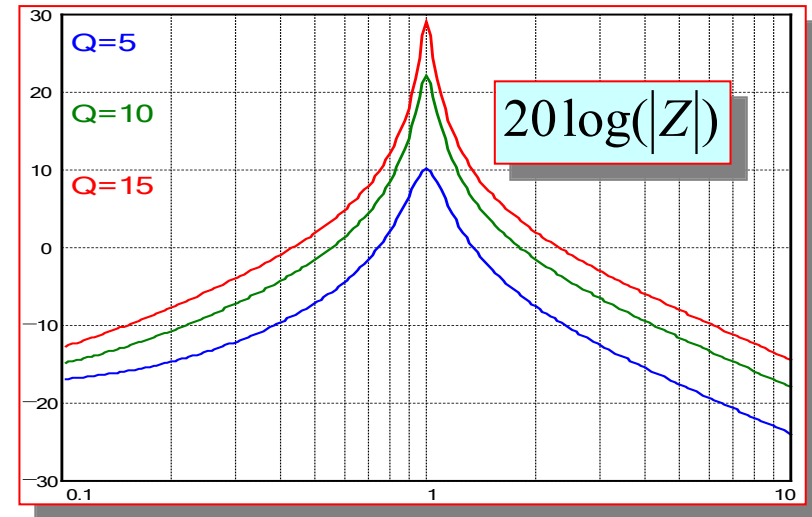
$$\text{Im}\{Z\} = \frac{R_p \tan \varphi}{1 + \tan^2 \varphi} = R_p \cos \varphi \sin \varphi$$




$$\omega \leq \omega_0$$

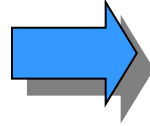

$$\varphi \geq 0$$


PHASE LEADING
VOLTAGE LEADS OVER THE CURRENT
INDUCTIVE MODE

$$\omega \geq \omega_0$$

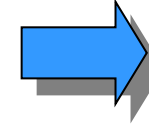


$$\varphi \leq 0$$

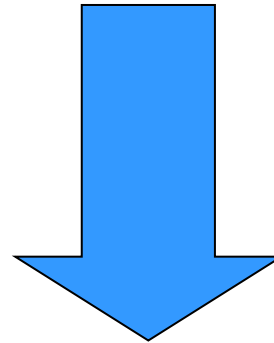PHASE LAGGING
VOLTAGE LAGS OVER THE CURRENT
CAPACITIVE MODE



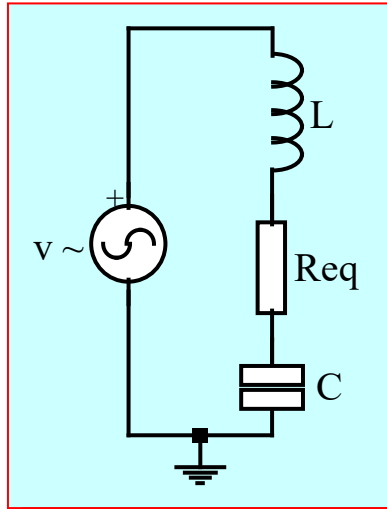PARALLEL RESONANT LOAD HAS TO BE DRIVEN IN RESONANCE.
POWER REGULATION IS ONLY POSSIBLE WITH A VARIABLE
INPUT POWER SUPPLY



$$Y(j\omega) = \frac{G_{eq}}{1 + jQ\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)} = \text{Re}\{Y(j\omega)\} + j \text{Im}\{Y(j\omega)\}$$

$$G_{eq} = \frac{1}{R_{eq}}$$


$$\varphi = \arg\{Z\} = \arg\{Y^{-1}\} = \text{atan} Q\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right) \Rightarrow \tan \varphi = Q\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)$$

$$Z = \frac{G_{eq}}{1 + j \tan \varphi}$$


$$|Y| = \frac{G_{eq}}{\sqrt{1 + \tan^2 \varphi}} = G_{eq} \cos \varphi$$

$$\text{Re}\{Y\} = \frac{G_{eq}}{1 + \tan^2 \varphi} = G_{eq} \cos^2 \varphi$$
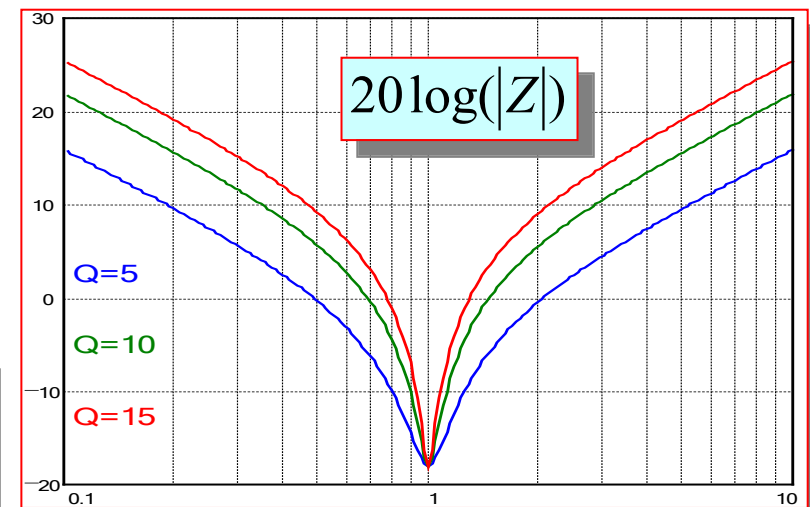
$$\text{Im}\{Y\} = \frac{-G_{eq} \tan \varphi}{1 + \tan^2 \varphi} = -G_{eq} \cos \varphi \sin \varphi$$




$$\omega \leq \omega_0$$

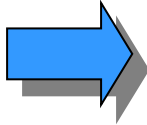

$$\varphi \leq 0$$


PHASE LAGGING
VOLTAGE LAGS OVER THE CURRENT
CAPACITIVE MODE

$$\omega \geq \omega_0$$

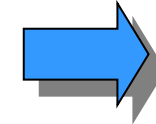

$$\varphi \geq 0$$


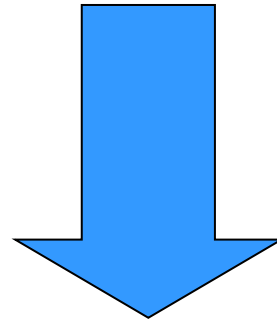
PHASE LEADING
VOLTAGE LEADS OVER THE CURRENT
INDUCTIVE MODE




**A SERIES RESONANT LOAD CAN BE DRIVEN IN RESONANCE OR
ABOVE OR BELOW RESONANCE. POWER REGULATION IS
POSSIBLE WITH A VARIABLE INPUT POWER SUPPLY OR BY
THE INVERTER ITSELF**

- ✓ Basic Concepts in Induction Heating
- ✓ Compensation of the Load
- ✓ **Series Resonant Converters for IH**
- ✓ Parallel Resonant Converters for IH
- ✓ Semiconductors used in IH
- ✓ Applications
 - ✓ Forging
 - ✓ Hardening
 - ✓ Multipurpose Generators
 - ✓ Bonding
 - ✓ Welders
- ✓ Controllers
- ✓ Roadmap

FULL-BRIDGE

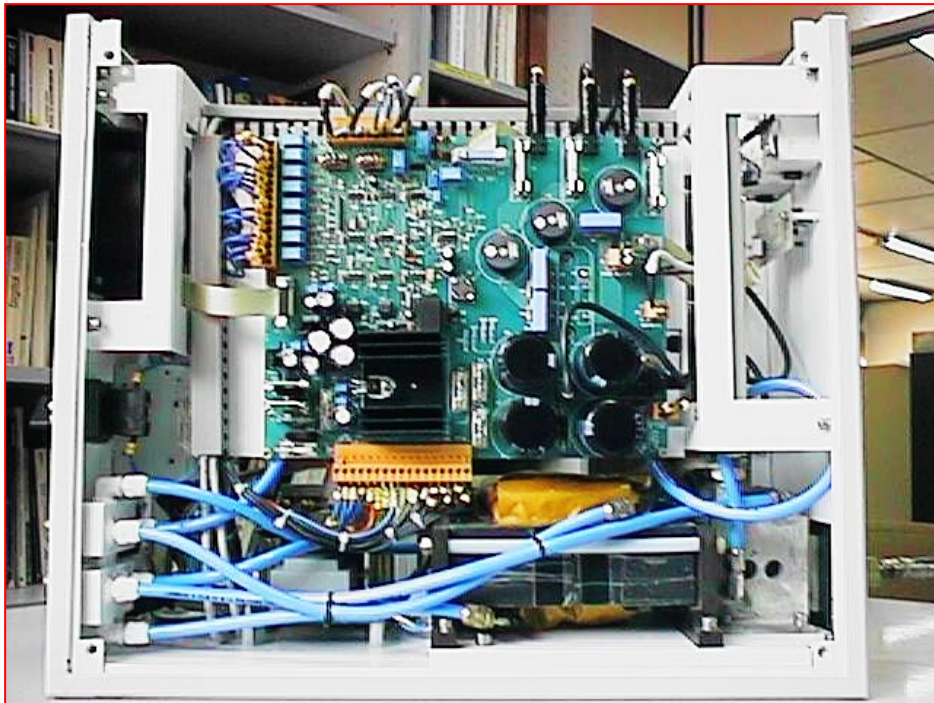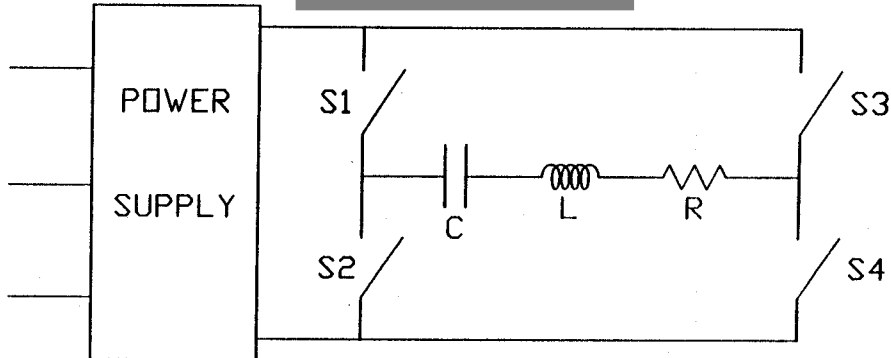


HALF-BRIDGE

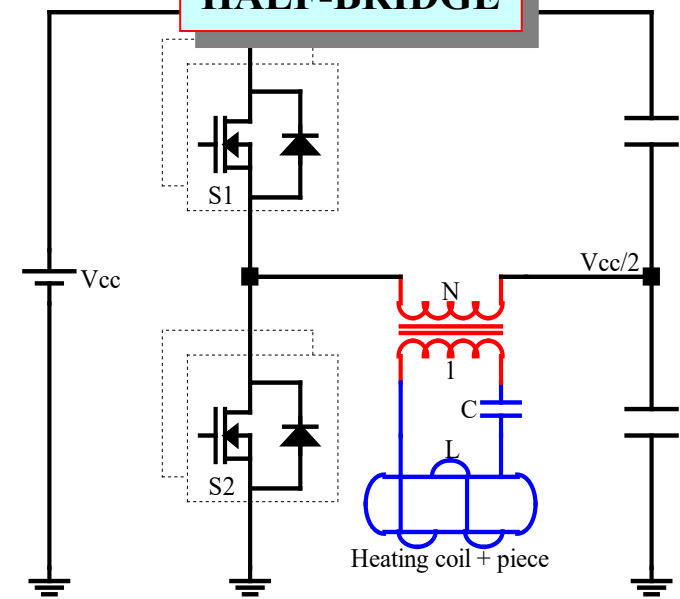


**SWITCHES ARE UNIDIRECTIONAL
IN VOLTAGE AND BIDIRECTIONAL
IN CURRENT.**

CAPACITIVE OR ZCS SWITCHING

$$\omega < \omega_0$$

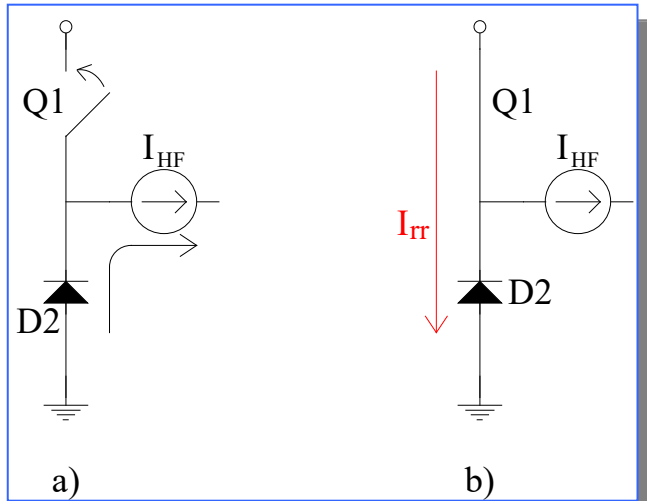


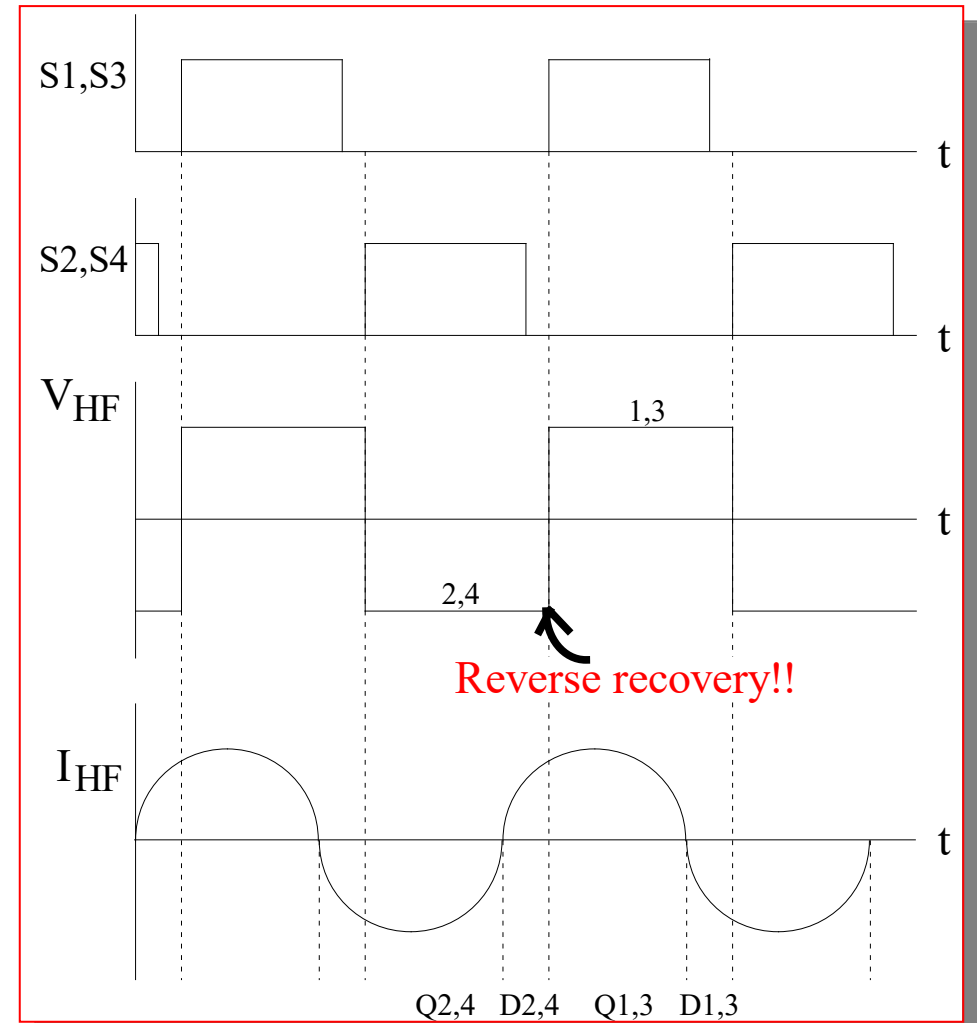- FOR CURRENT LEADING, THE SWITCHING PROCESS IS FIXED BY THE TURN-ON OF THE TRANSISTORS.
- NO TURN-OFF LOSSES.
- TURN-ON LOSSES (TURN-ON SNUBBER).
- REVERSE RECOVERY PROBLEMS WITH THE ANTI-PARALLEL DIODES.
- ADDITIONAL LOSSES DUE TO THE DISCHARGE OF THE PARASITIC CAPACITOR C_{oss} .




INDUCTIVE OR ZVS SWITCHING

$$\omega > \omega_0$$

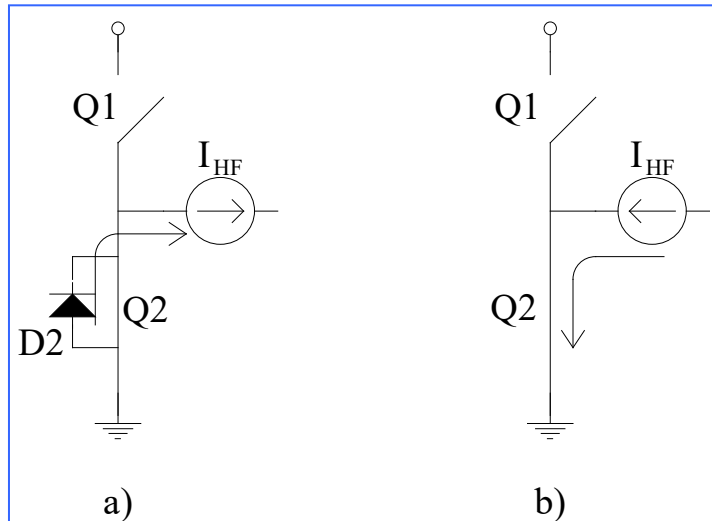

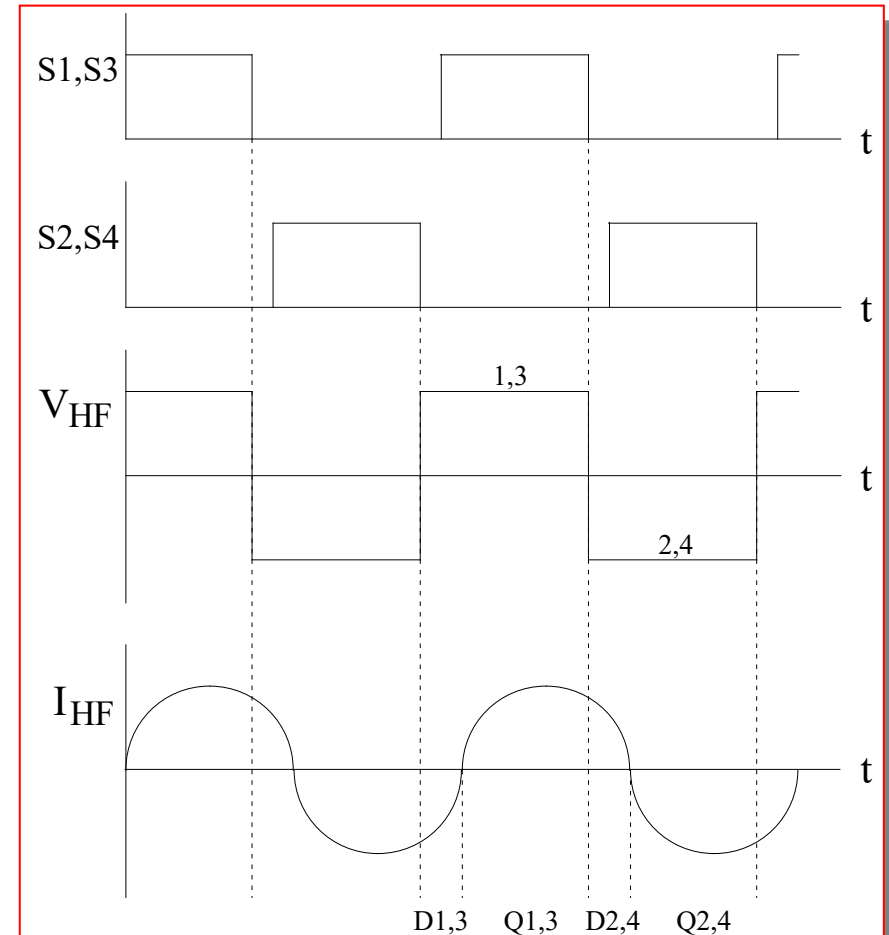- FOR CURRENT LAGGING, THE SWITCHING PROCESS IS FIXED BY THE TURN-OFF OF THE TRANSISTORS.
- NO TURN-ON LOSSES.
- TURN-OFF LOSSES (TURN-OFF SNUBBER).
- NO REVERSE RECOVERY PROBLEMS WITH THE ANTI-PARALLEL DIODES.
- PARASITIC CAPACITOR C_{oss} ACTS LIKE A LOSSLESS TURN-OFF SNUBBER.



INDUCTIVE PHASE ZVS OR TURN-OFF CONTROLLED

	ON	OFF
S	ZVS	HARD
D	HARD	ZCS



- HIGH TURN-OFF LOSSES FOR S
- REDUCED TURN-ON LOSSES FOR D
- HIGH OVERVOLTAGE DUE TO TRANSISTOR TURN-OFF


CAPACITIVE PHASE ZCS OR TURN-ON CONTROLLED

	ON	OFF
S	HARD	ZCS
D	ZVS	HARD




- L ACTS LIKE A LOSSLESS TURN-ON SNUBBER
- REDUCED TURN-ON LOSSES FOR S
- HIGH TURN-OFF LOSSES FOR D
- HIGH OVERVOLTAGE DUE TO REVERSE RECOVERY DIODE CURRENT

IN-PHASE SWITCHING

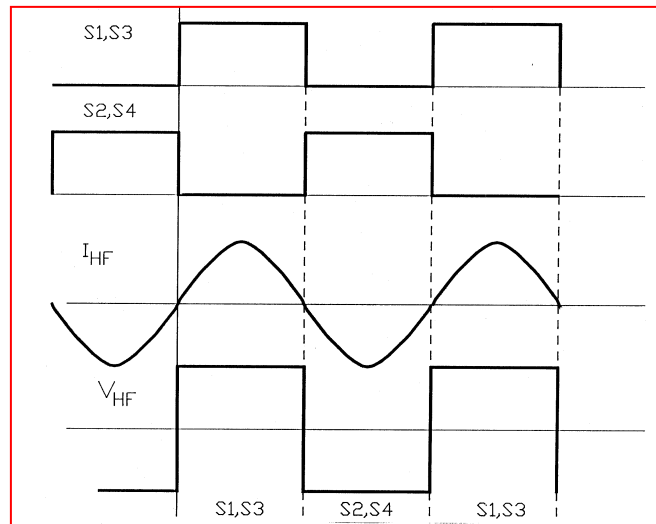

IDEAL

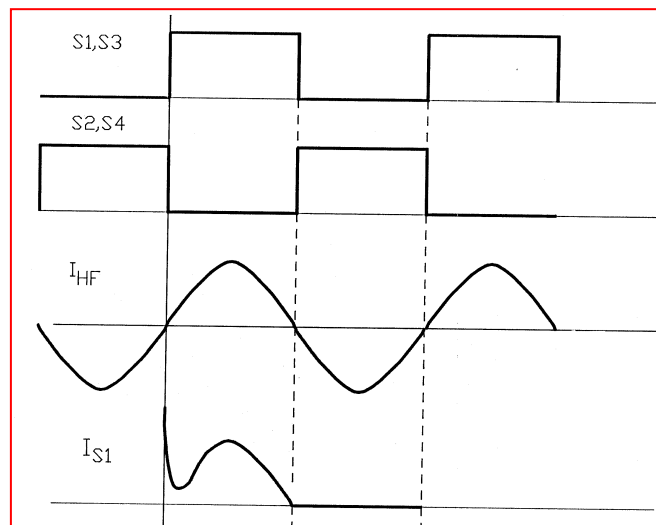- **OUTPUT VOLTAGE AND CURRENT IN PHASE.**
- **MINIMAL SWITCHING LOSSES.**
- **NO REVERSE RECOVERY PROBLEMS WITH ANTI-PARALLEL DIODES.**




REAL

- **DUE TO THE PARASITIC CAPACITOR OF THE SWITCHES (C_{oss}), AN OVERCURRENT IS GENERATED AT TURN ON, CAUSING ADDITIONAL LOSSES THAT LIMIT THE MAXIMUM OPERATING FREQUENCY OF THE INVERTER (TURN-ON LOSSES).**

SOFT-SWITCHING CONDITIONS

**TO HAVE SOFT
SWITCHING IT IS
NECESSARY TO
ACCOMPLISH:**

- $\beta_0 \leq \beta$ FOR CLAMPED
MODE.
- $0 \leq |\alpha| \leq \beta - \beta_0$ FOR ZVS
TURN-ON.

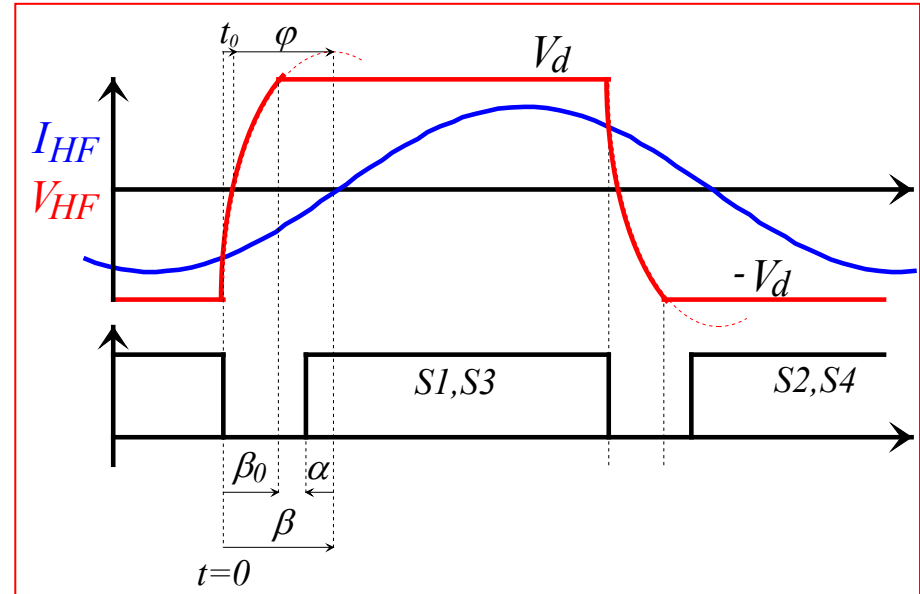

**THIS TWO CONDITIONS ENSURE THE DIODES
POLARISATION (CLAMP), AND THE TRANSISTOR TURN-ON
WHEN THE DIODES ARE STILL DRIVING (ZVS).**


CONSEQUENTLY

$$\beta \geq \arccos \left(\cos \alpha - \frac{2C\omega V_d}{I_0} \right)$$

SOFT-SWITCHING ZVS DRIVING

- **TURN-OFF BEFORE TURN-ON TO AVOID OVERLAPPING (DEAD TIMES NEEDED).**
- **CURRENT LAGGING TO AVOID REVERSE RECOVERY PROBLEMS WITH THE ANTIPARALLEL DIODES.**
- **Coss (OR SNUBBERS) HAVE TO BE FULLY CHARGED BEFORE TURN-ON (TO AVOID LOSSES).**
- **NO TURN-ON LOSSES**



SOFT-SWITCHING

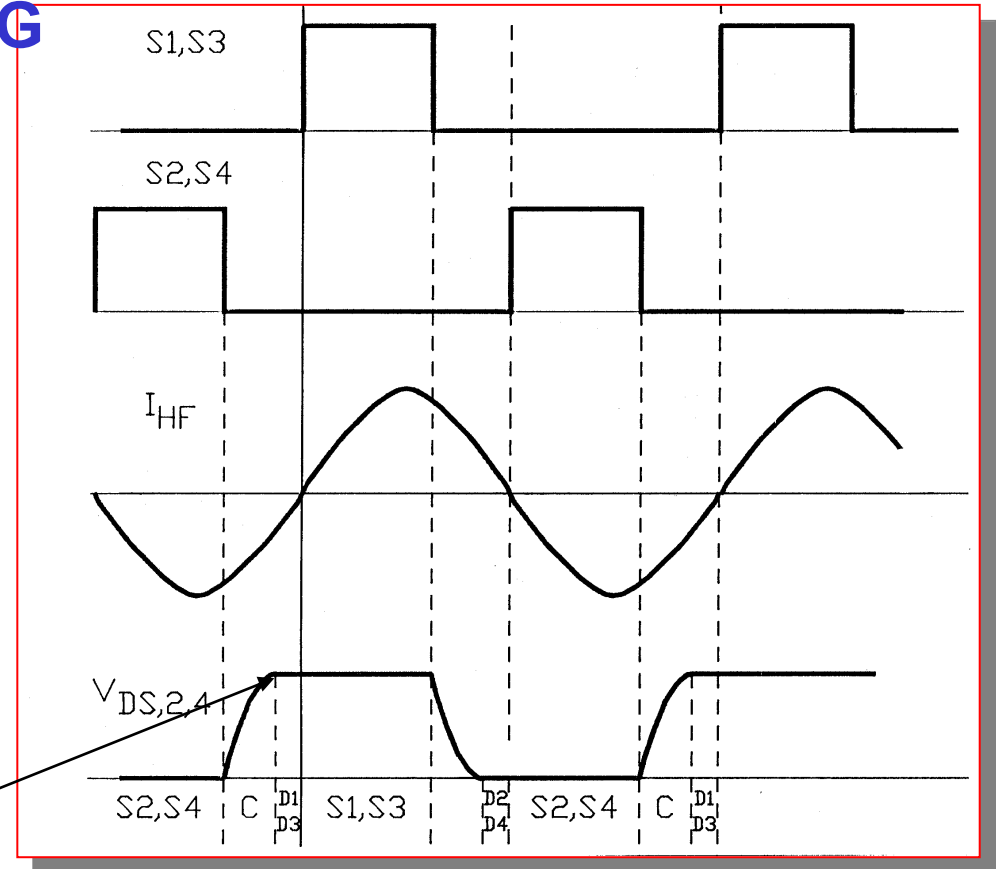

OPTIMUM SWITCHING

- **$\beta = \beta_0$: THE TURN OFF IS ADVANCED TO ENSURE CLAMPED MODE.**
- **$\alpha = 0$: THE TURN ON IS JUST AT THE ZERO CROSSING OF THE CURRENT.**

FM: FREQUENCY MODULATION

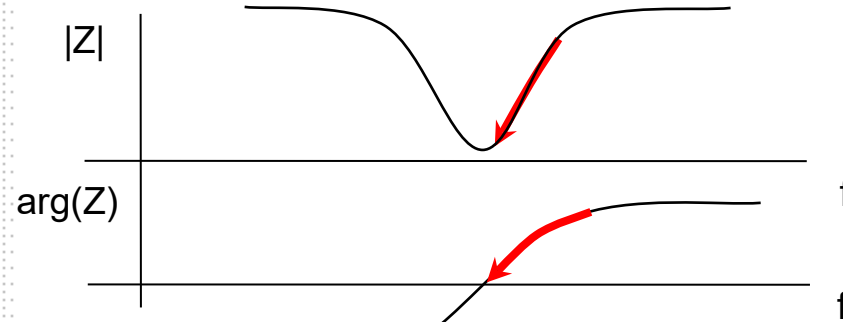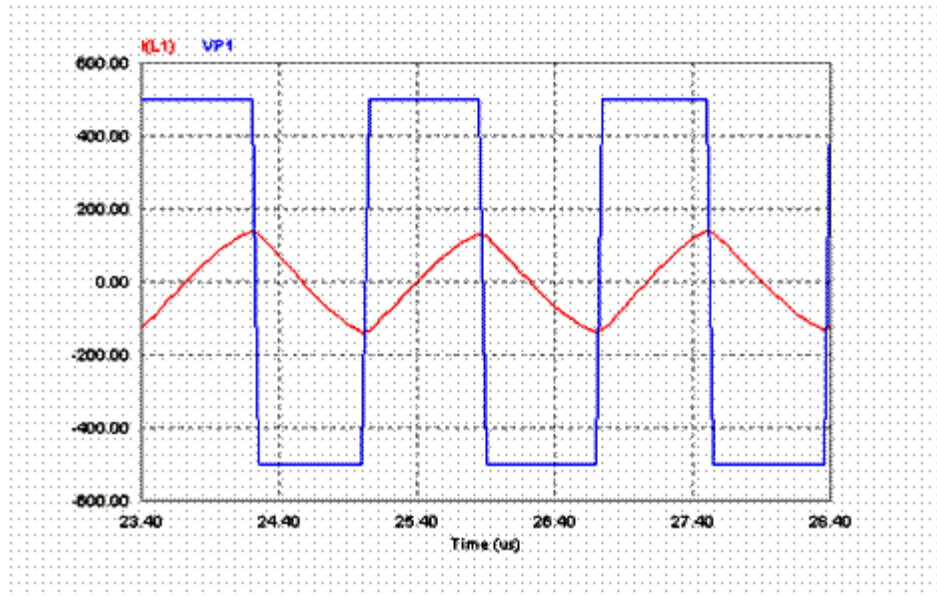


$f \downarrow \Rightarrow |Z| \downarrow \Rightarrow \arg(Z) \downarrow \Rightarrow \text{Power} \uparrow$



$f \uparrow \Rightarrow \arg(Z) \uparrow \Rightarrow \text{Power losses} \uparrow$

**INDUCTIVE MODE
PREFERRED:
WORKING
FREQUENCY
HIGHER THAN
RESONANT
FREQUENCY**


PS: Phase Shift-turn-on Controlled

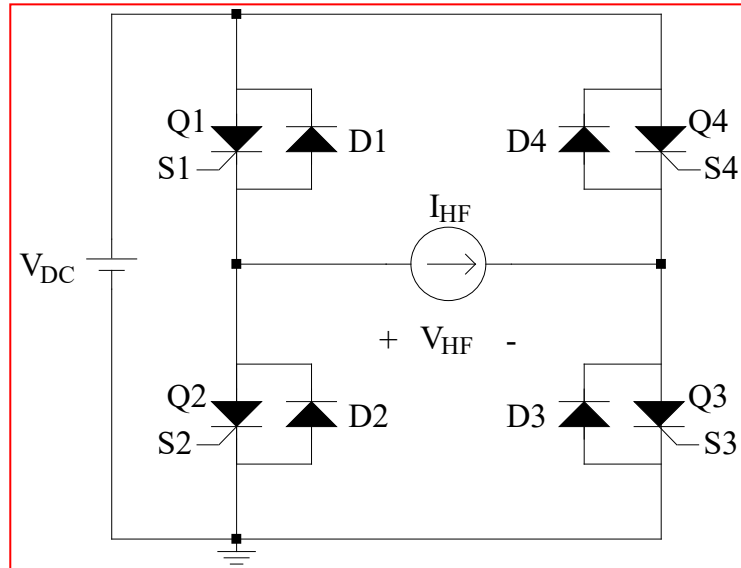

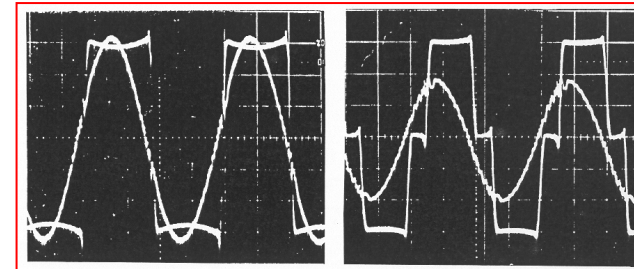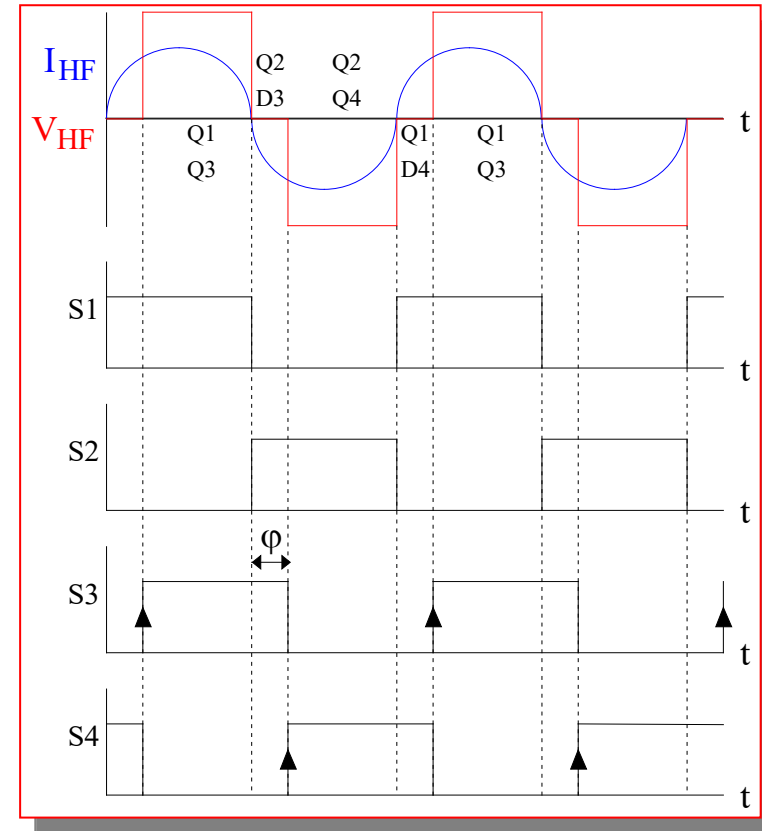
- LEFT SWITCHES COMMUTATE AT THE ZERO CROSSING OF THE OUTPUT CURRENT.
- RIGHT SWITCHES ARE DELAYED A PHASE-SHIFT ϕ .
- RIGHT SWITCHES ARE TURN-ON CONTROLLED.
- OPTIMUM FOR IGBT SWITCHES.





PS: Phase Shift-turn-off Controlled

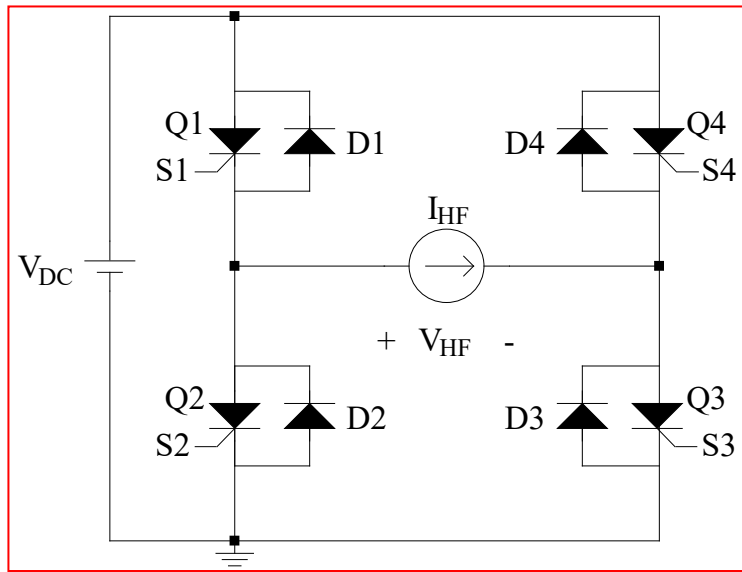

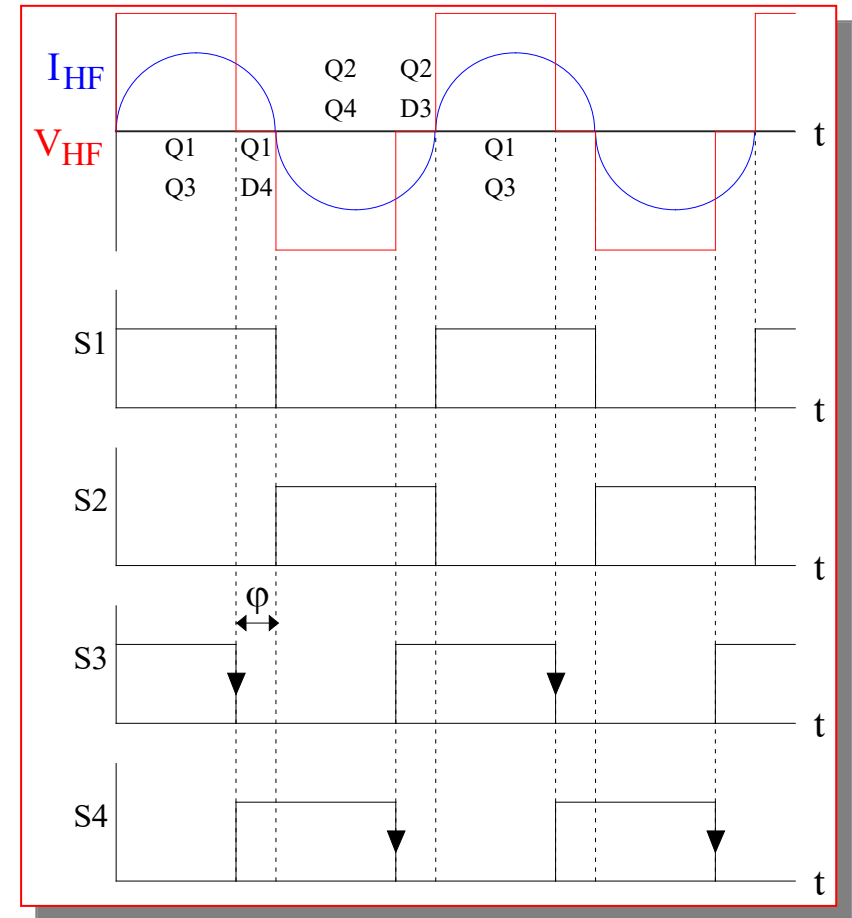- LEFT SWITCHES COMMUTATE AT THE ZERO CROSSING OF THE OUTPUT CURRENT.
- RIGHT SWITCHES ARE ADVANCED A PHASE-SHIFT ϕ .
- RIGHT SWITCHES ARE TURN-OFF CONTROLLED.
- OPTIMUM FOR MOS SWITCHES.



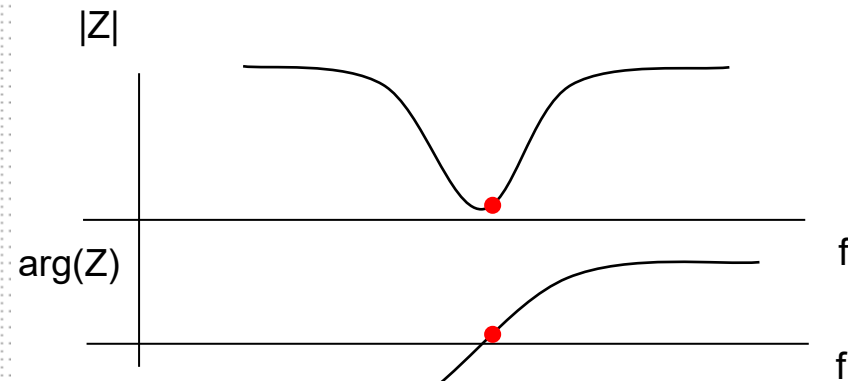
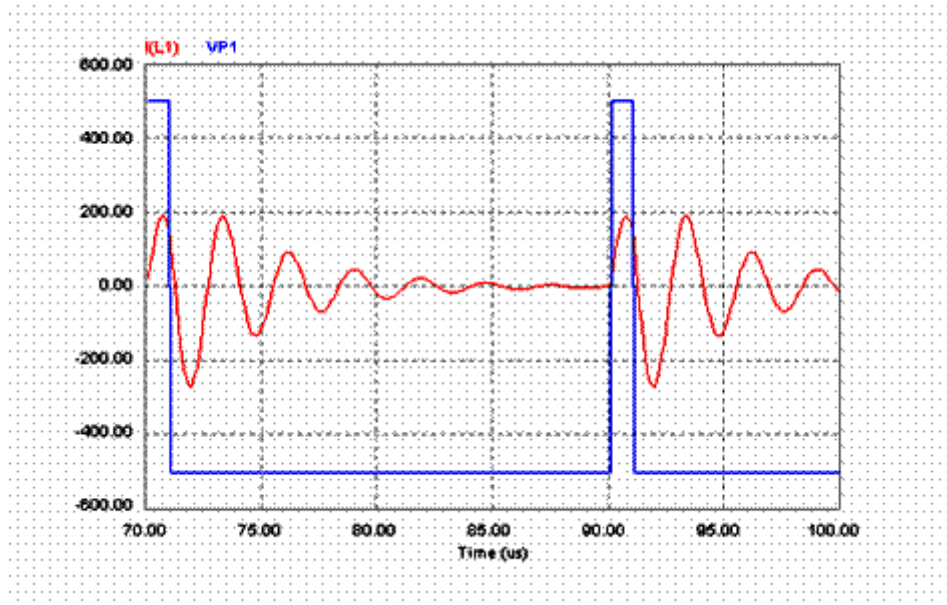
PDM: PULSE DENSITY MODULATION-IN PHASE SWITCHING



Number of pulses per cycle $\uparrow \Rightarrow$ Power $\uparrow$

$\arg(Z)$ minimum $\Rightarrow$ Power losses minimum


PDM: INVERTER WAVEFORMS

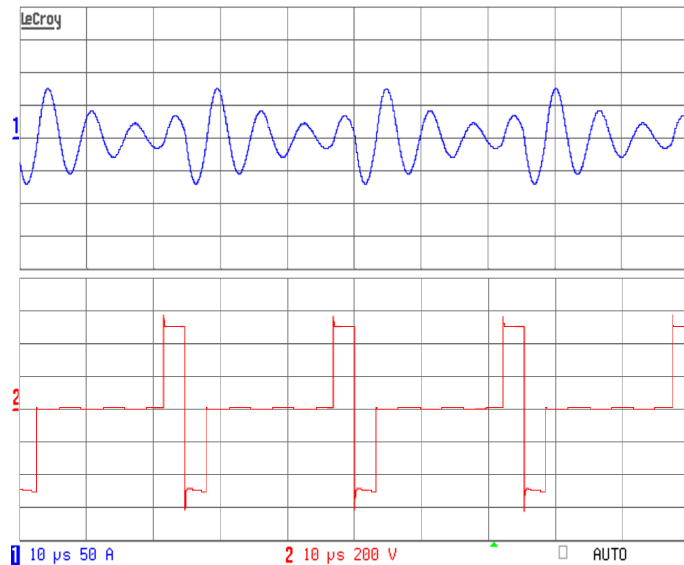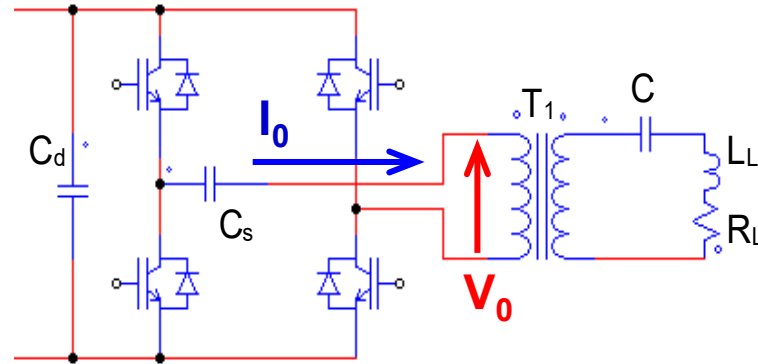


I_0
(50 A/div)

V_0
(200 V/div)

TB: 10 μs/div

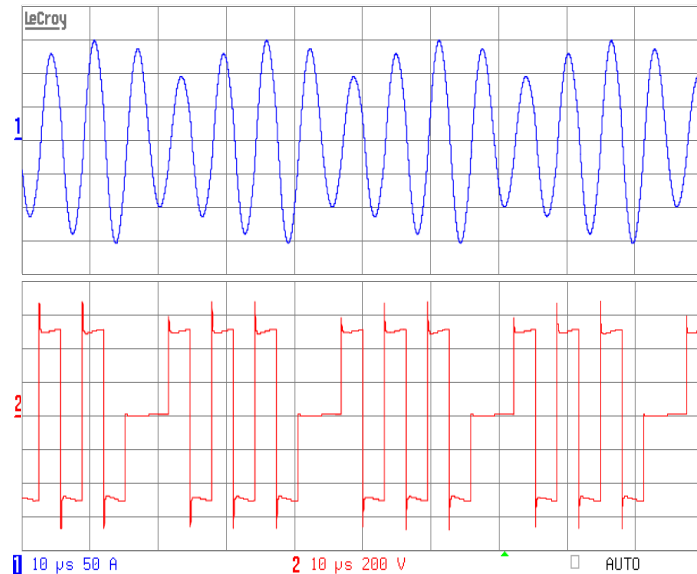

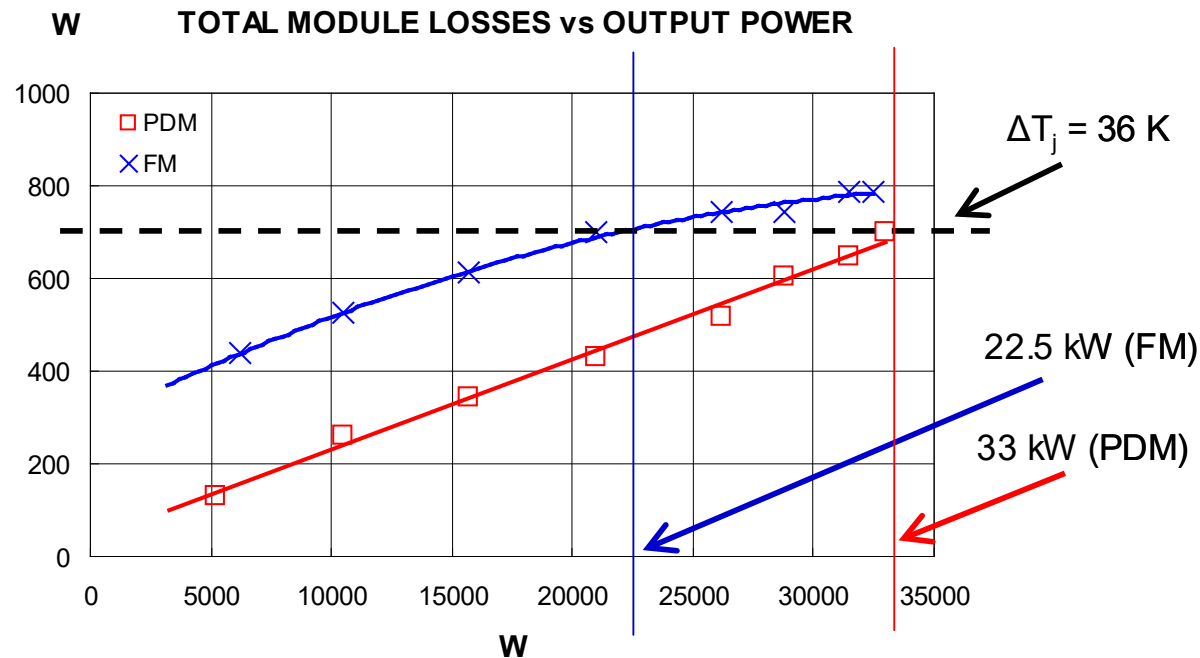
EXPERIMENTAL RESULTS COMPARATIVE STUDY: PDM vs FM



Module power losses using Frequency Modulation (FM) and Pulse Density Modulation (PDM) control techniques


The inverter output power obtained with PDM is more than 1.4 times higher than the achieved with FM control method

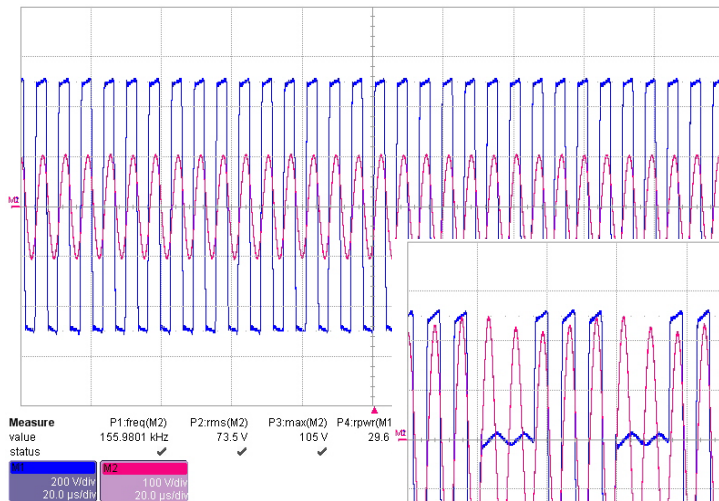SECOND POWER UPGRADING INCREASING THE MAXIMUM CURRENT PEAK




P = 33 kW
 $I_p = 110$ A
Modulation index = 1

150 kHz
 $\Delta T_j = 36$ K

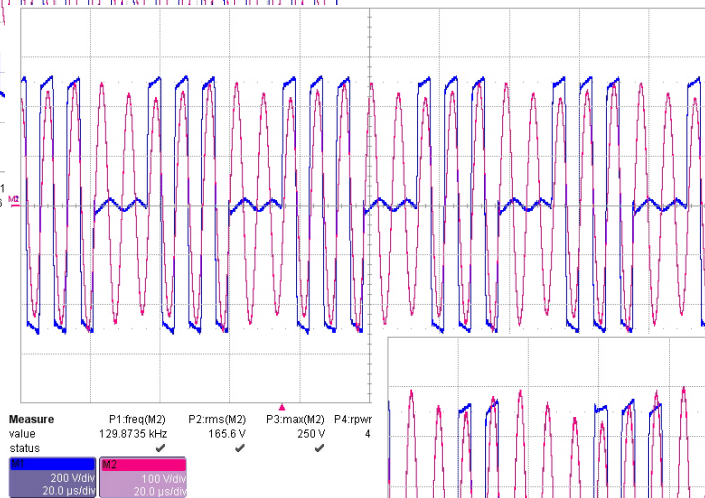

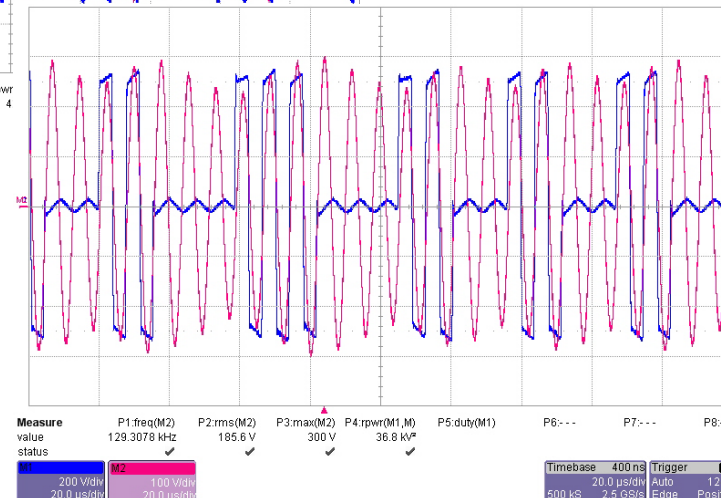
P = 46 kW
 $I_p = 250$ A
Modulation index = 1.7



P = 42 kW
 $I_p = 300$ A
Modulation index = 2

SECOND POWER UPGRADING INCREASING THE MAXIMUM CURRENT PICK

150 kHz
 $\Delta T_j = 36 \text{ K}$

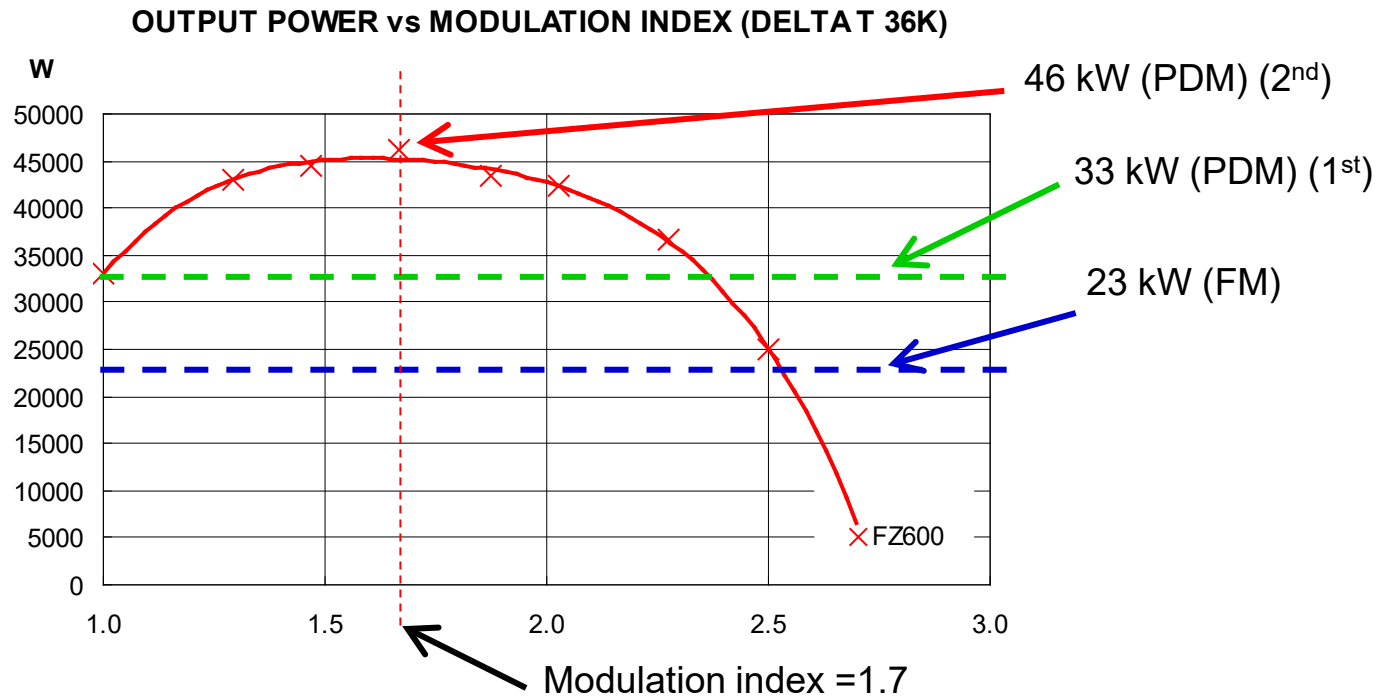

SECOND UPGRADING FACTOR = 1.4

TOTAL UPGRADING FACTOR = $1.4 \times 1.4 \approx 2$ (150 kHz)

POWER REGULATION METHODS

PULSE DENSITY MODULATION VS. FREQUENCY MODULATION

FREQUENCY MODULATION

ADVANTAGES:

- ZVS condition
- Low current ripple

DISADVANTAGES:

- High power losses at low output power level
- Frequency variation

PULSE DENSITY MODULATION

ADVANTAGES:

- ZVS and quasi ZCS condition
- Constant current frequency
- Minimum switching power losses at any power level


DISADVANTAGES:

- High current ripple


- ✓ Basic Concepts in Induction Heating
- ✓ Compensation of the Load
- ✓ Series Resonant Converters for IH
- ✓ Parallel Resonant Converters for IH**
- ✓ Semiconductors used in IH
- ✓ Applications
 - ✓ Forging
 - ✓ Hardening
 - ✓ Multipurpose Generators
 - ✓ Bonding
 - ✓ Welders
- ✓ Controllers
- ✓ Roadmap

Basic Topologies Used


IDEAL CONDITIONS

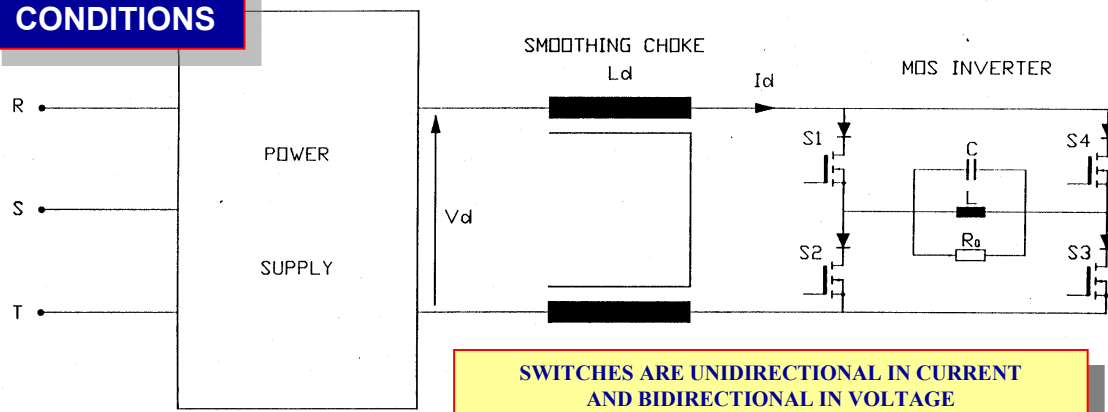



CAPACITIVE SWITCHING

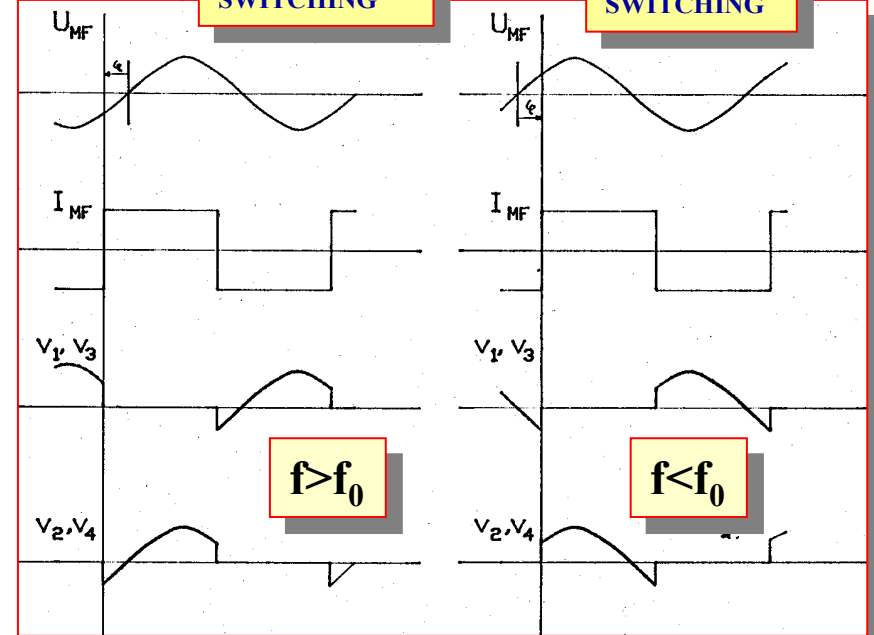


INDUCTIVE SWITCHING

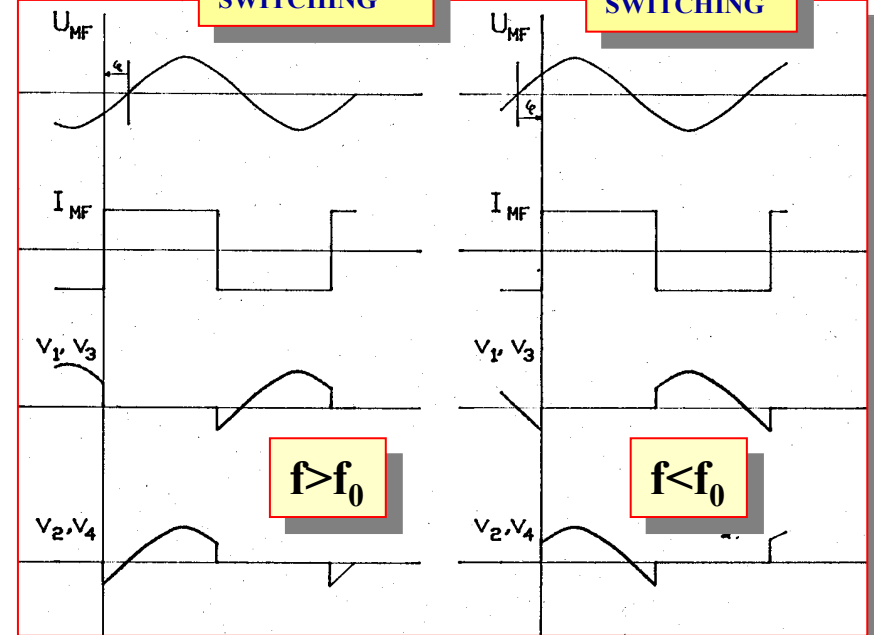

REAL WORLD CONDITIONS

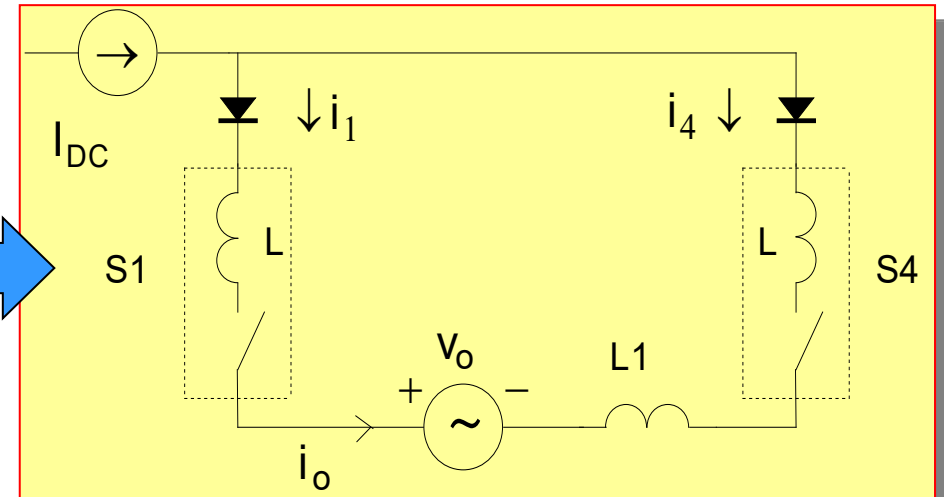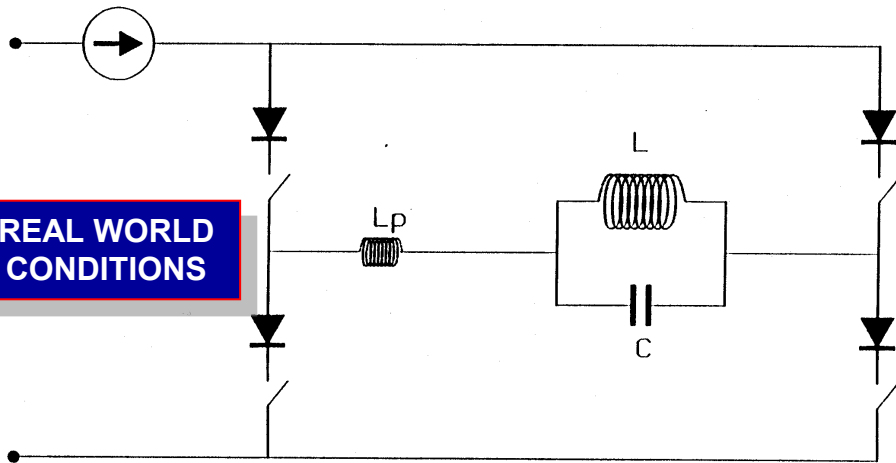


ZCS COMMUTATION

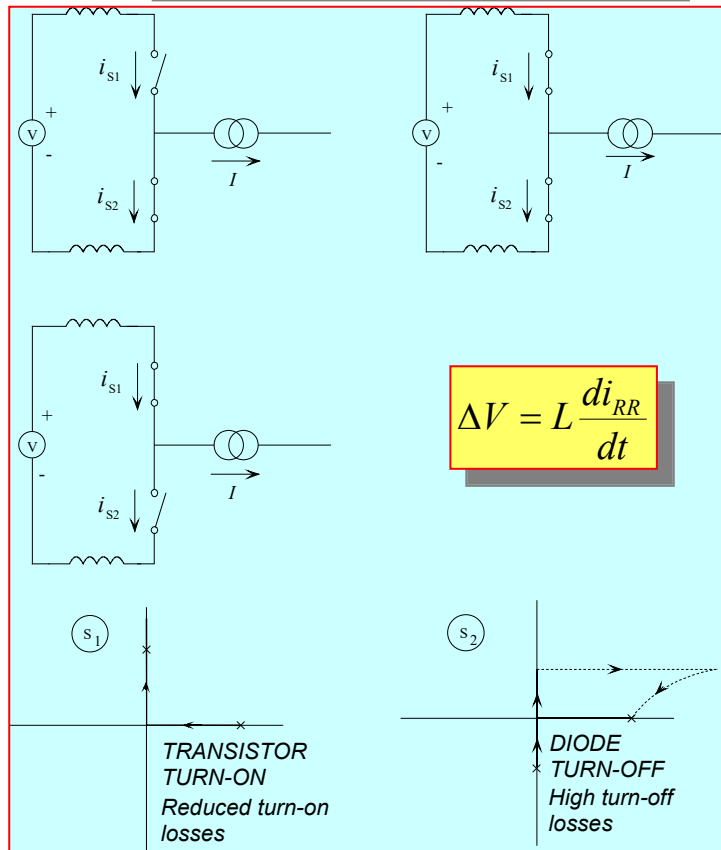

AN OVERVOLTAGE GENERATED DUE TO THE REVERSE RECOVERY CURRENT IN THE SERIES DIODES


ZVS COMMUTATION

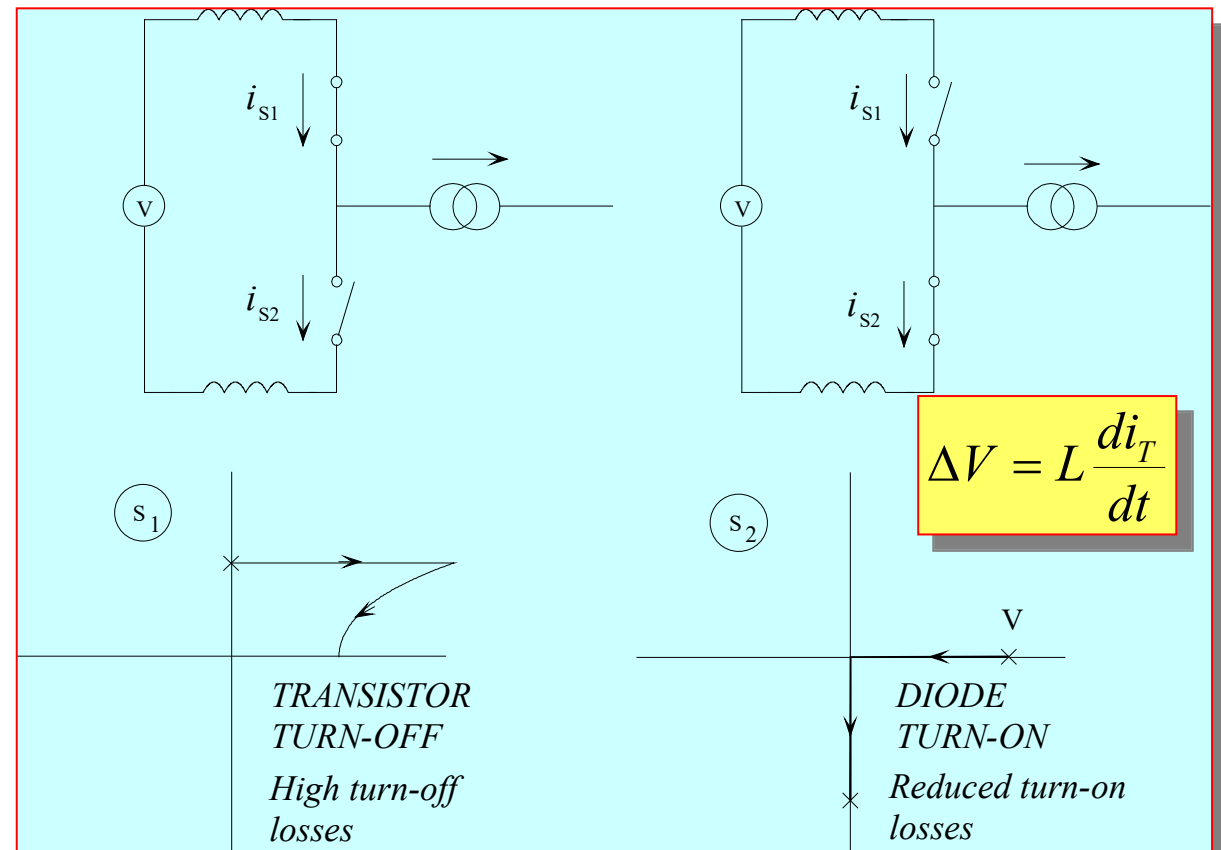

AN OVERVOLTAGE GENERATED DUE TO THE TURN-OFF OF THE TRANSISTOR


FOR INDUCTIVE PHASE ZVS OR TURN-OFF CONTROLLED

	ON	OFF
S	ZVS	HARD
D	HARD	ZCS

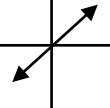

FOR CAPACITIVE PHASE ZCS OR TURN-ON CONTROLLED

	ON	OFF
S	HARD	ZCS
D	ZVS	HARD

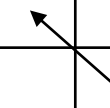

- L ACTS LIKE A LOSSLESS TURN-ON SNUBBER

- REDUCED TURN-ON LOSSES FOR S

- HIGH TURN-OFF LOSSES FOR D

- HIGH OVERVOLTAGE DUE TO REVERSE RECOVERY DIODE CURRENT

**PREFERRED SWITCHING AT LOW
FREQUENCY: CAPACITIVE MODE**

OPTIMUM SWITCHING


$$i = I_d - \frac{V_o}{L_p \omega} (\cos \omega t - \cos \beta)$$

$$i_1 = I_d - \frac{V_o}{2L_p \omega} (\cos \omega t - \cos \beta)$$

$$i_1 = \frac{V_o}{2L_p \omega} (\cos \omega t - \cos \beta)$$


OPTIMUM TURN-OFF: AT THE ZERO CROSSING POINT OF THE OUTPUT VOLTAGE ($\alpha = 0$)

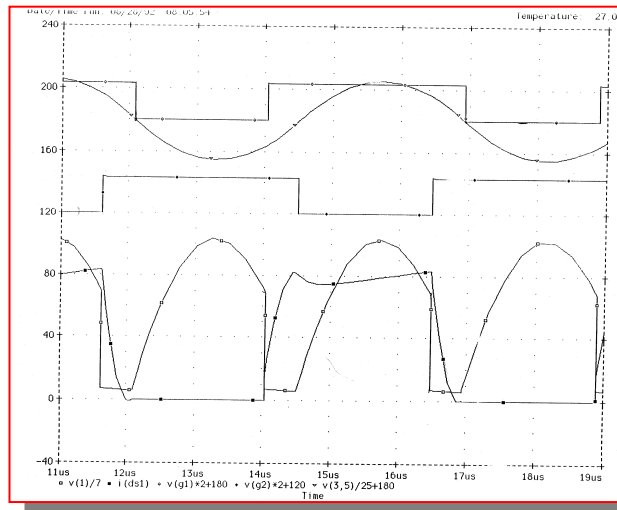
OPTIMUM TURN-ON: ADVANCED TO THE ZERO CROSSING POINT OF OUTPUT VOLTAGE SO THAT THE OUTPUT CURRENT CHANGES ITS POLARITY EXACTLY AT THIS POINT ($\beta = \beta_0$)





$$\cos \beta_0 = 1 - \frac{2L_p I_d \omega}{V_0} = 1 - \frac{k I_d f}{V_0}$$

$$\alpha = 0$$

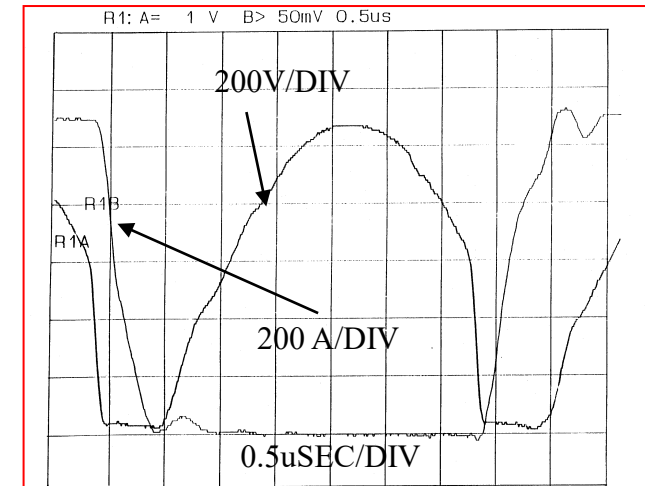

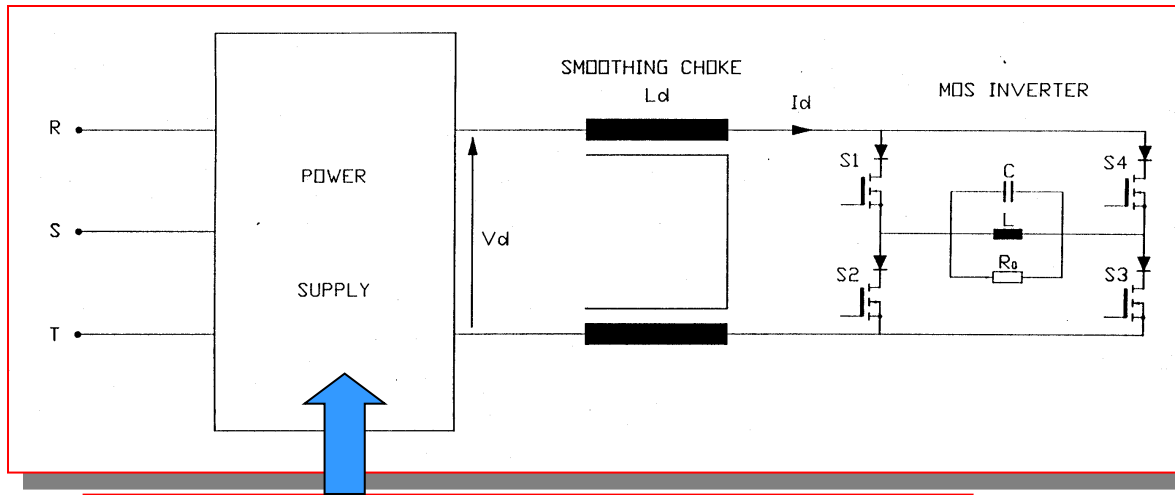

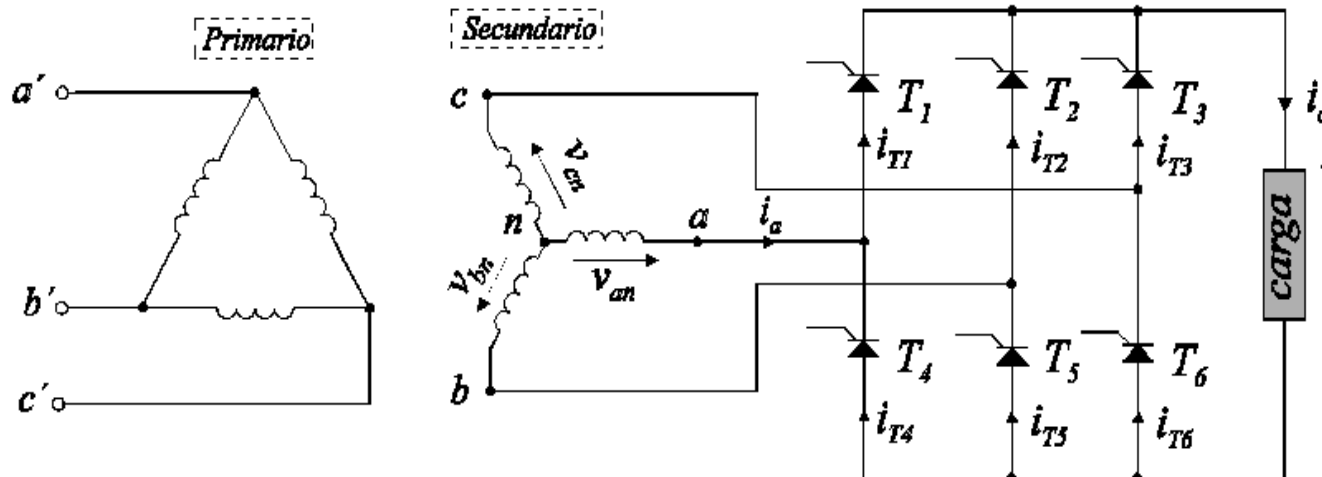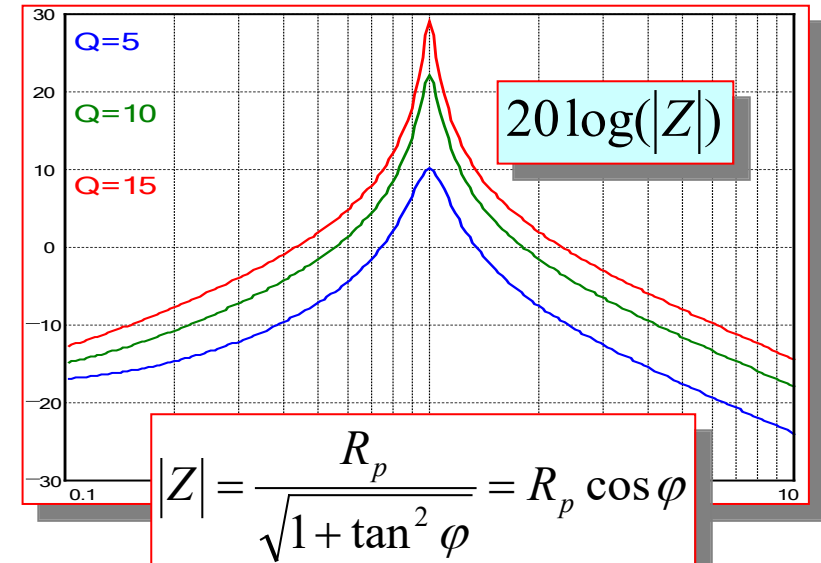As the load impedance decreases with φ ($Z = R \cos \varphi$) power regulation can only be achieved with a variable Power Supply and not by the inverters itself




$$U_{DC} = U_{di} \cdot \cos \alpha$$

donde

$$U_{di} = \frac{3 \cdot \sqrt{2}}{\pi} \cdot U_{20} = 1,35 \cdot U_{20}$$

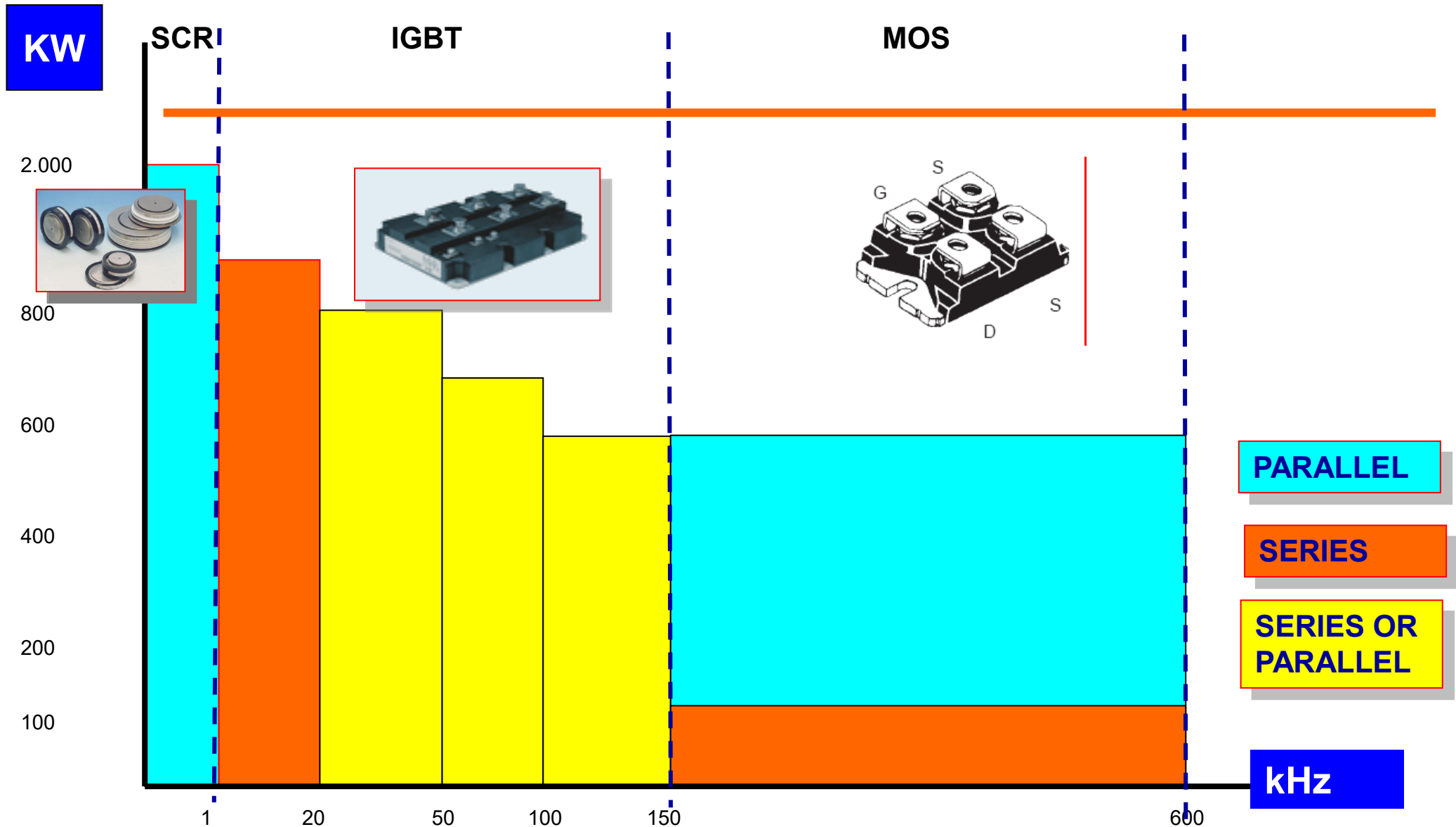- ✓ Basic Concepts in Induction Heating
- ✓ Compensation of the Load
- ✓ Series Resonant Converters for IH
- ✓ Parallel Resonant Converters for IH
- ✓ **Semiconductors used in IH**
- ✓ Applications
 - ✓ Forging
 - ✓ Hardening
 - ✓ Multipurpose Generators
 - ✓ Bonding
 - ✓ Welders
- ✓ Controllers
- ✓ Roadmap



- ✓ Basic Concepts in Induction Heating
- ✓ Compensation of the Load
- ✓ Series Resonant Converters for IH
- ✓ Parallel Resonant Converters for IH
- ✓ Semiconductors used in IH
- ✓ **Applications**
 - ✓ Forging
 - ✓ Hardening
 - ✓ Multipurpose Generators
 - ✓ Bonding
 - ✓ Welders
- ✓ Controllers
- ✓ Roadmap

Industrial processes

MELTING



HARDENING



SOLDERING




FORGING





Domestic Applications

Inducción



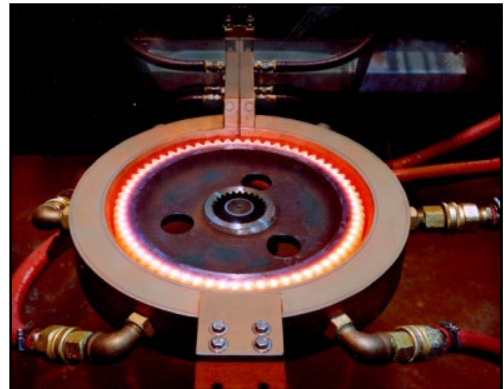

- ✓ Fast, precise, efficient, repeatable
 - Reduces energy, utility & operating costs
- ✓ Advantages of induction heating
 - Efficiency & reliability
 - Flexible, modular & reduced costs
- ✓ Less floor space
 - Compact, modular & moveable
- ✓ No warm-up time
 - Standby & hold circuitry
- ✓ Environmentally friendly
 - Low energy consumption
- ✓ High quality results
 - Reduced part distortion, less scale (forging)

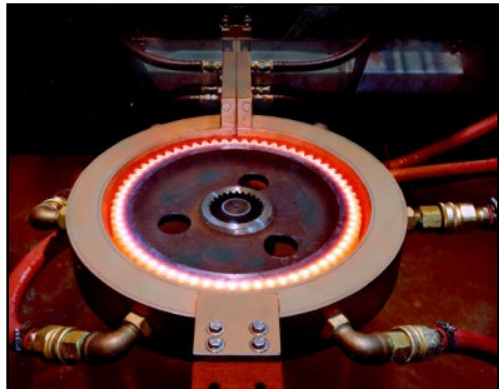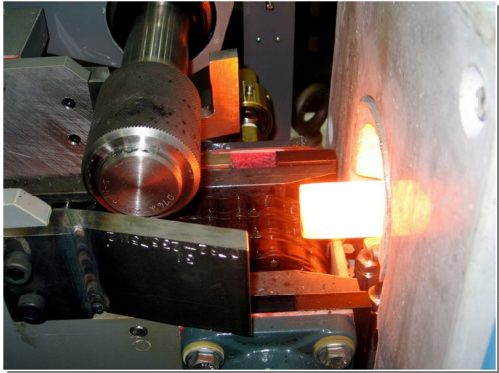

Induction heating applications

- Heating & heat treating
- Forge heating
- Mass Heating
- Other applications

Industries that benefit from induction heating

- Automotive
- Aeronautics
- Electrical motor manufacturers
- Other Industries

APPLICATION	POWER (KW)	FREQUENCY (KHZ)	TYPE OF GENERATOR
MELTING FOR INDUSTRY	<i>25-12.000</i>	<i>0,1-2,0</i>	<i>THYRISTOR</i>
FORGING	<i>5-5.000</i>	<i>0,25-5,0</i>	<i>THYRISTOR, IGBT</i>
SURFACE HARDENING > 2mm	<i>5-1.000</i>	<i>3-10</i>	<i>IGBT</i>
SURFACE HARDENING < 2mm	<i>5-500</i>	<i>3-150</i>	<i>IGBT</i>
TUBE WELDING	<i>100-1.000</i>	<i>100-600</i>	<i>MOS</i>

Automotive

Aerospace

Oil & Gas

Steel and iron
industry

White goods

Wind energy


Fastener

Fibber Optic

Medical


Jewellery

Adhesive curing	Annealing	Bonding	Bonding rubber-metal
Atmospheric brazing	Brazing	Catheter tipping	Crystal pulling
Forging	Getter firing	Hardening	Pre-heating
Staking metal-plastic	Hot forming	Levitation melting	Material testing
Melting	MOCVD	Pin Sealing	Plastic reflow
Sealing metal-glass	Shrink fitting	Soldering	Susceptor heating

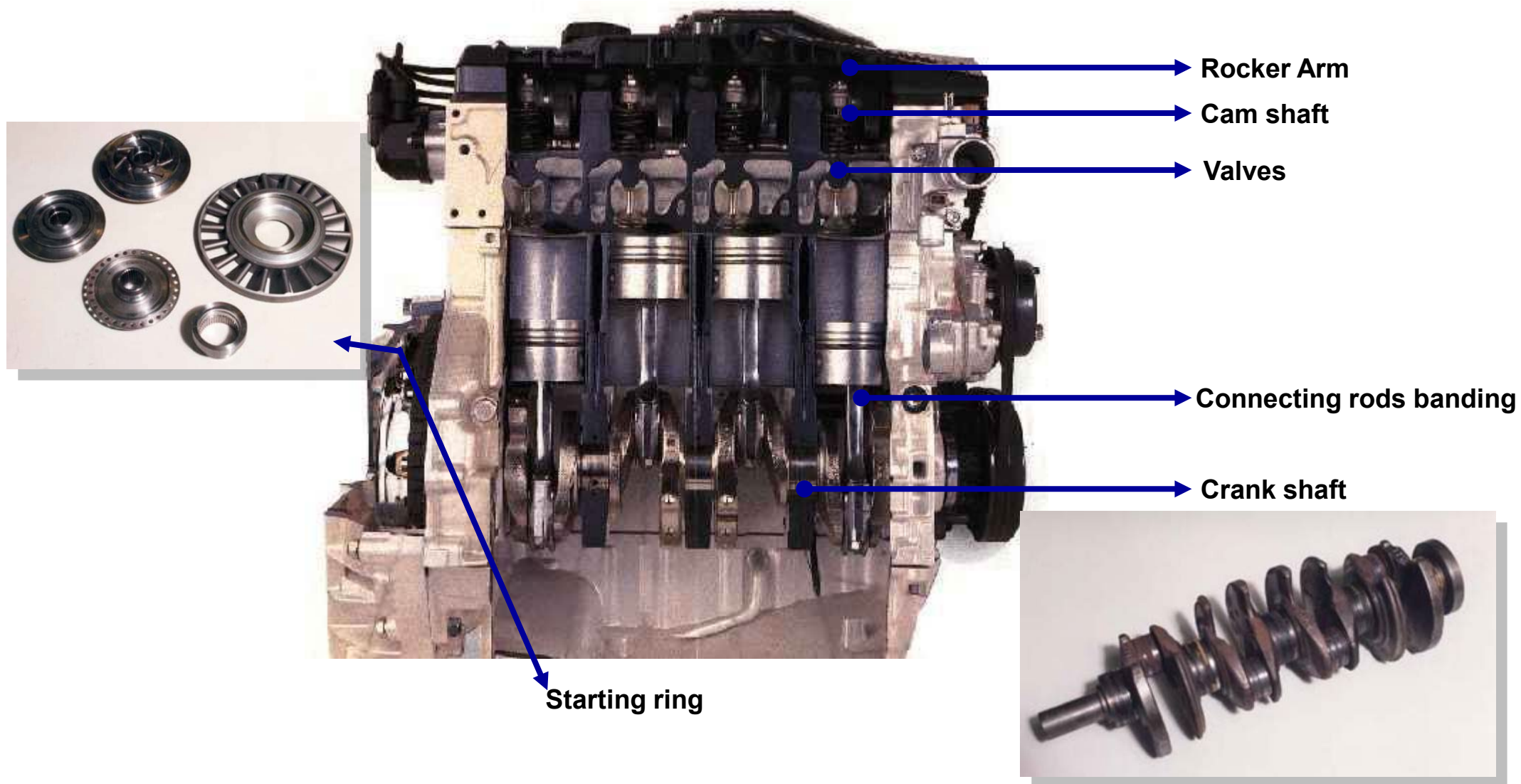




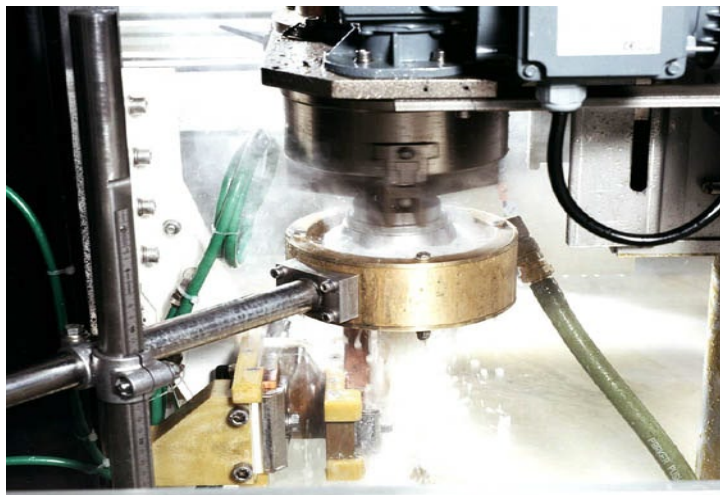Drive Shaft Hardening & Tempering Installation



CV Joint Hardening Installation

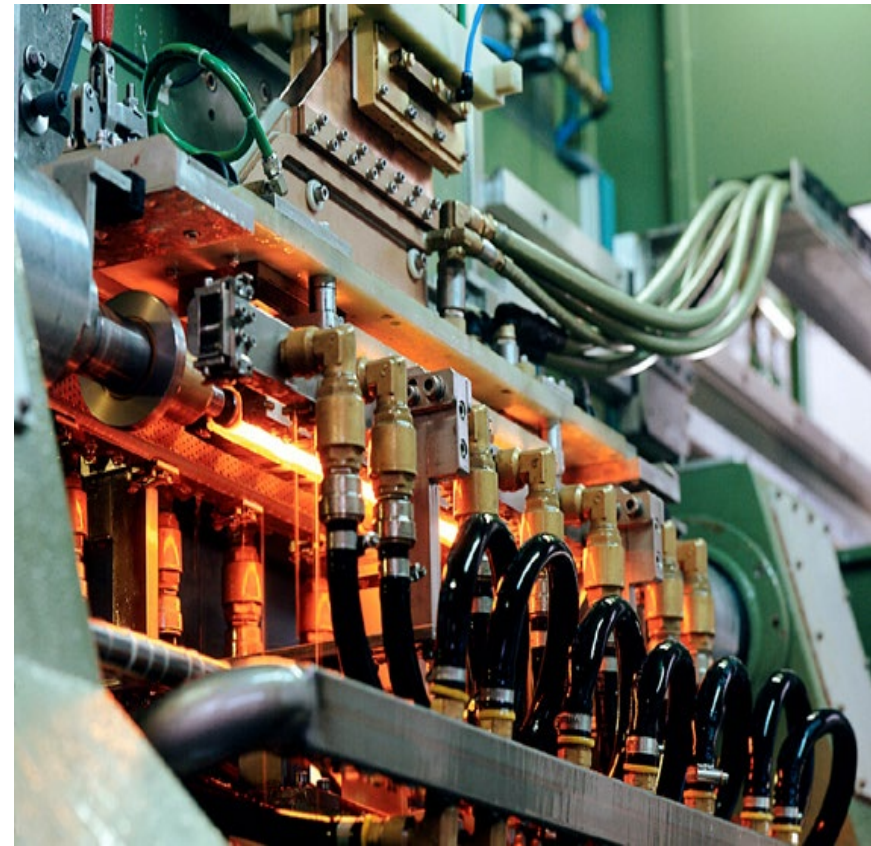


Drive Shaft Hardening Installation



- Wing to wing thermal processing
 - Turbine engines
 - Piston engines
 - Connecting rods, crankshaft, gears
 - Turbojet, turboshaft & turboprop engines



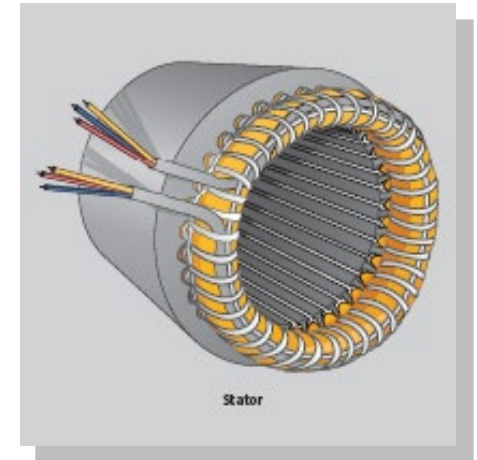- Inductions applications
 - Shrink fitting
 - Paint drying
 - Brazing & soldering
 - Curing of encapsulates
- Various induction heated parts
 - Housing for motor assembly
 - Stators & rotors
 - DC motor armatures
 - Gears & bearings





- Other industries that benefit
 - Hand & mining tools
 - Marine engines
 - Railroad: train engines, tracks
 - Off-road vehicles: motorcycles, bicycles
 - Household cooking buttons
- Various induction heated parts
 - Hammers, shovels, bits, fubars
 - Cranks & cams
 - Gears, sprockets, bearings
 - Pan Button Brazing

- ✓ Basic Concepts in Induction Heating
- ✓ Compensation of the Load
- ✓ Series Resonant Converters for IH
- ✓ Parallel Resonant Converters for IH
- ✓ Semiconductors used in IH
- ✓ **Applications**
 - ✓ **Forging**
 - ✓ Hardening
 - ✓ Multipurpose Generators
 - ✓ Bonding
 - ✓ Welders
- ✓ Controllers
- ✓ Roadmap



Mass Heating (hot & warm forging)

Slab & strip Heating


Wire & cable heating

Tube & pipe heating

Forming: bending, expanding & spinning

Extrusion: squeezing metal through a die

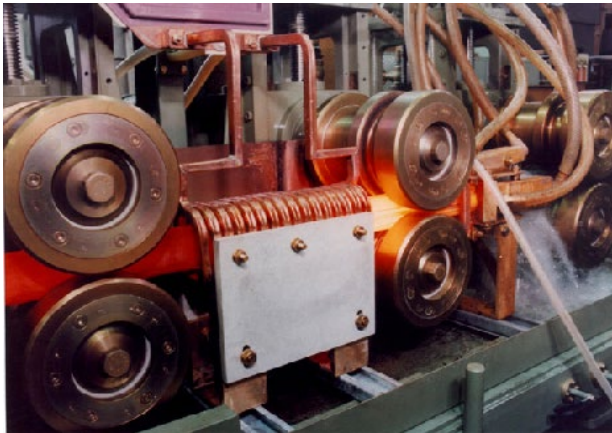Rolling: made from ingots or continuous cast metals






- Forging

Forging: billets or bars heated and are forged in press hammers or up setters

Steel components represent the majority
Aluminum, copper, brass, bronze, cobalt, nickel and titanium as well

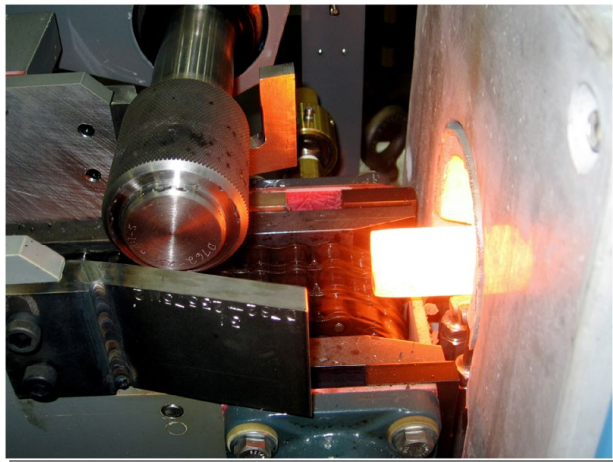- Ideal billet temperature: 1200 °C
- Advanced Temperature Profile Modeling



Power Range:

500 Vef MF
(1-5 kHz)

500 kW - 800kW


800 Vef MF
(1-3kHz)


500kW - 800kW - 1000kW - 1200kW

1200 Vef MF
(1-3kHz)


800-1500kW – 2000kW

Current-fed inverter


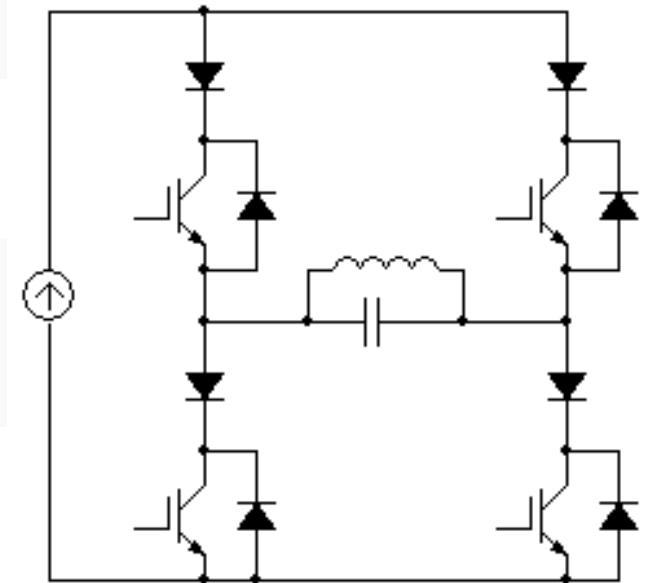


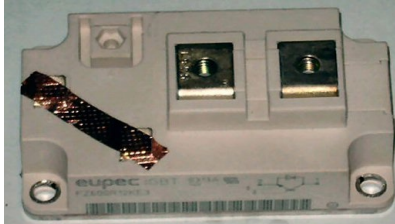

MÓDULOS DE 140 mm. x 130 mm.

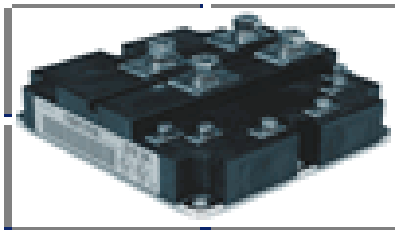

MÓDULOS DE 140 mm. x 190 mm.

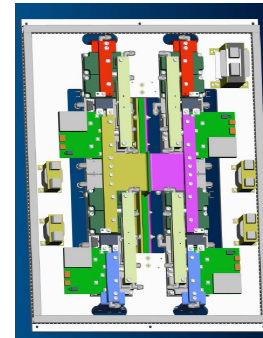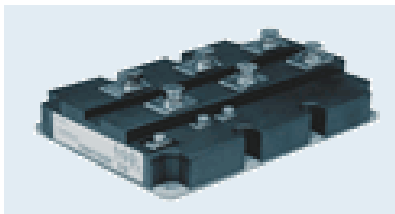




CONFIGURACIÓN nº 1



CONFIGURACIÓN nº 2



CONFIGURACIÓN nº 3

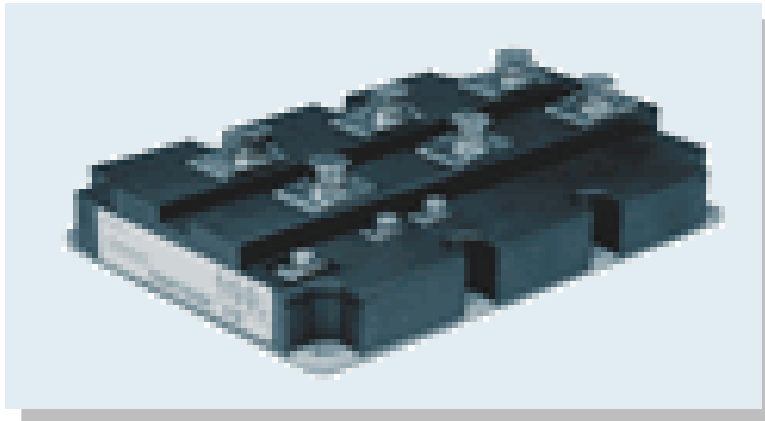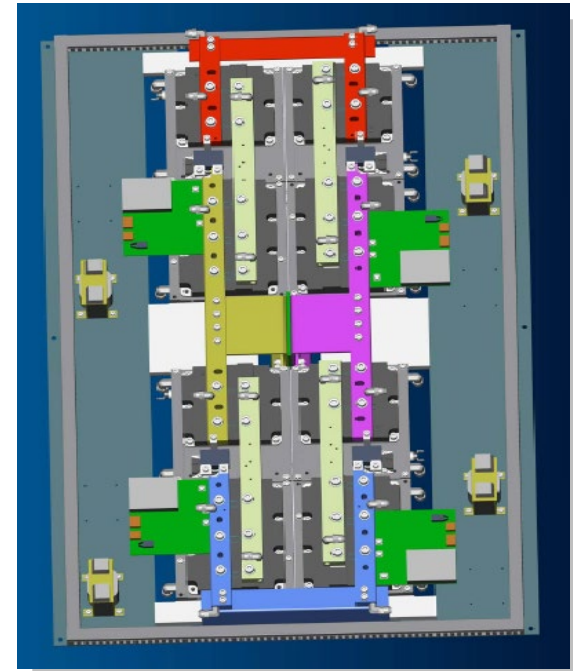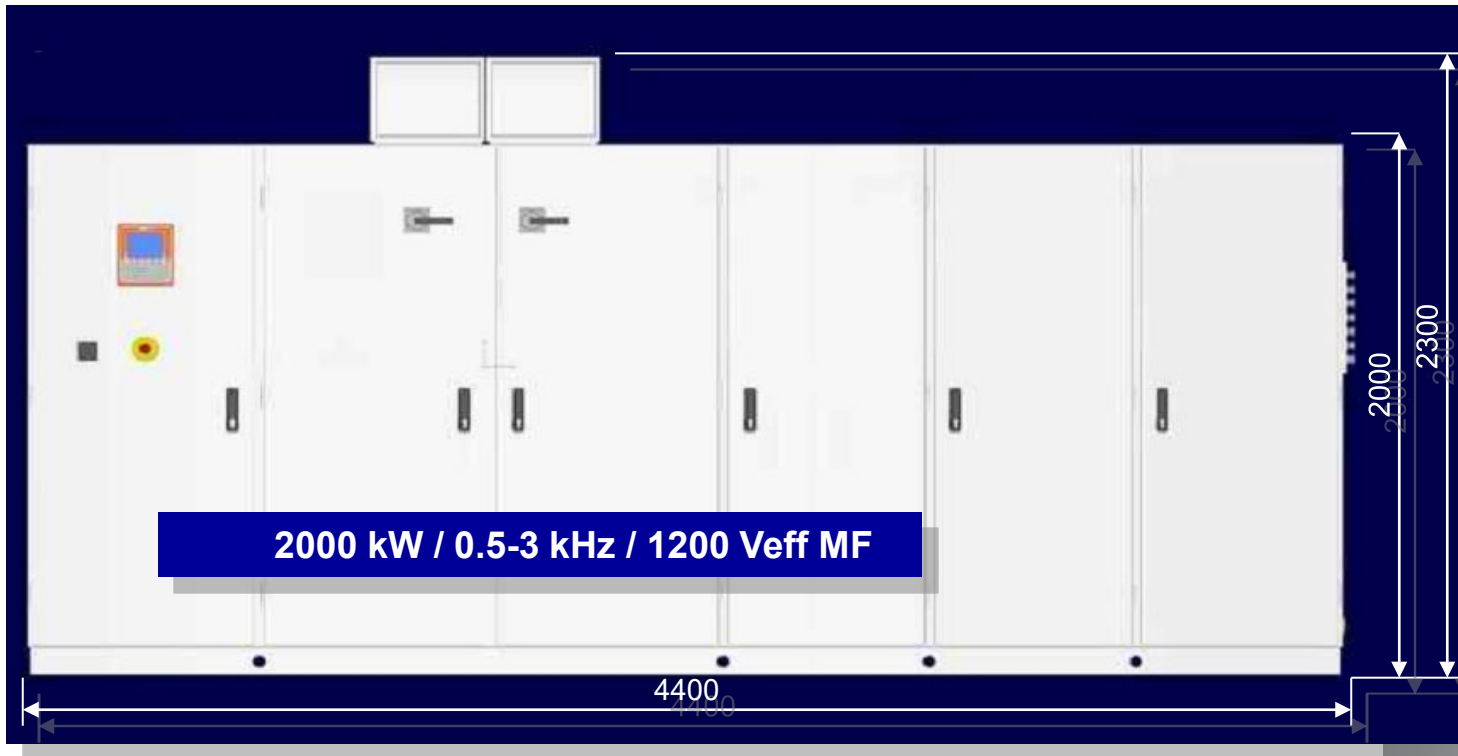

- ✓ Basic Concepts in Induction Heating
- ✓ Compensation of the Load
- ✓ Series Resonant Converters for IH
- ✓ Parallel Resonant Converters for IH
- ✓ Semiconductors used in IH
- ✓ **Applications**
 - ✓ Forging
 - ✓ **Hardening**
 - ✓ Multipurpose Generators
 - ✓ Bonding
 - ✓ Welders
- ✓ Controllers
- ✓ Roadmap




Heating & Heat Treating





Harden: surface hardening of steel
(increases wear resistance & strength)




Temper: reheating & quench cooling
(improves hardness & elasticity)

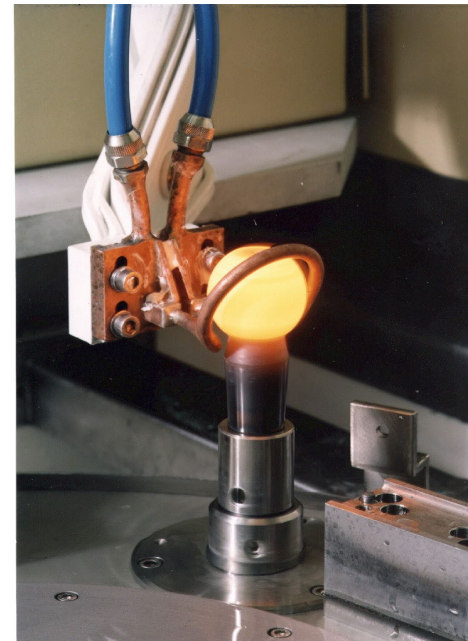Annealing: remove internal stresses
improving ductility of material



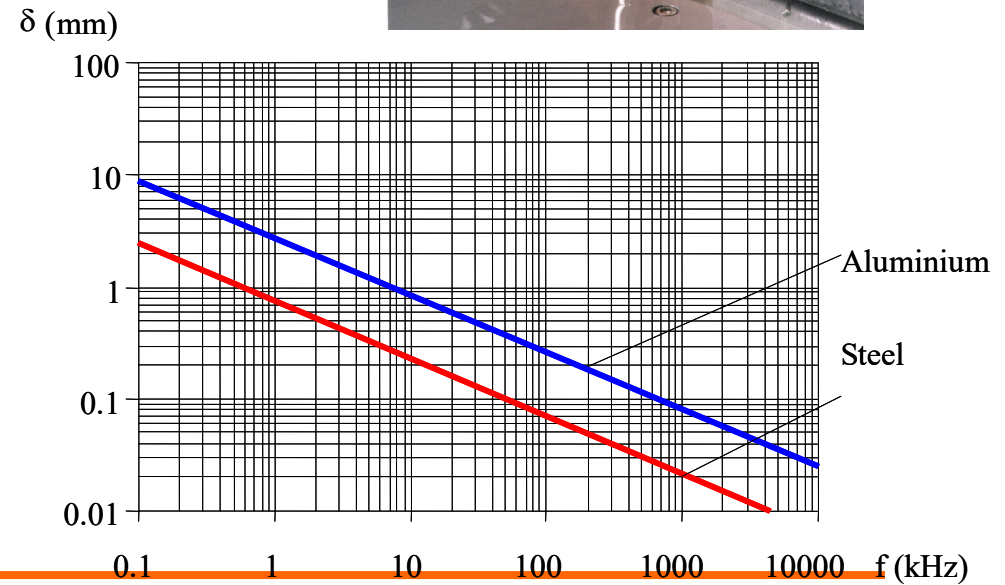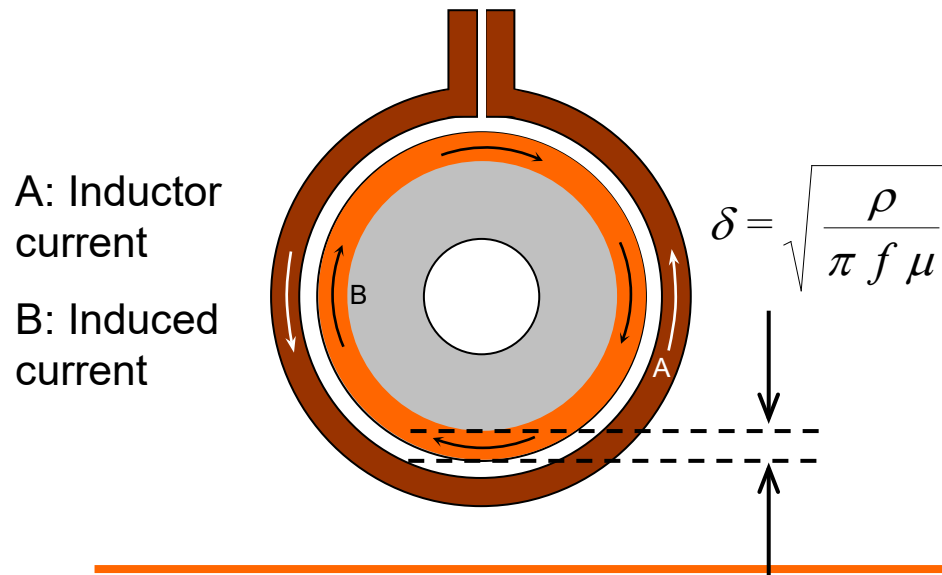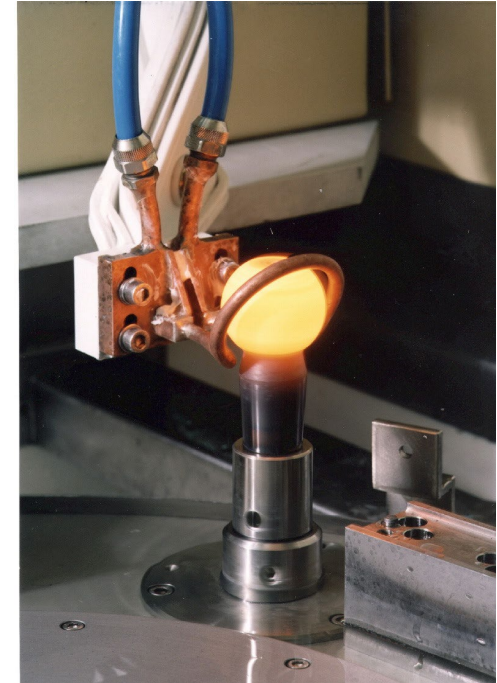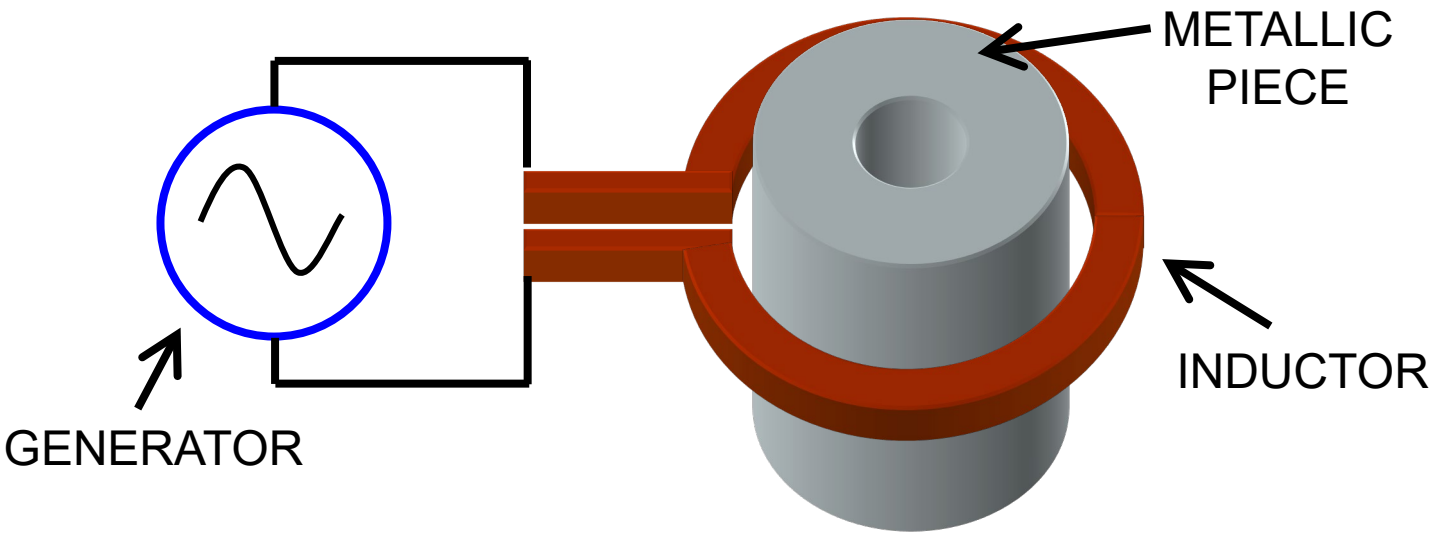


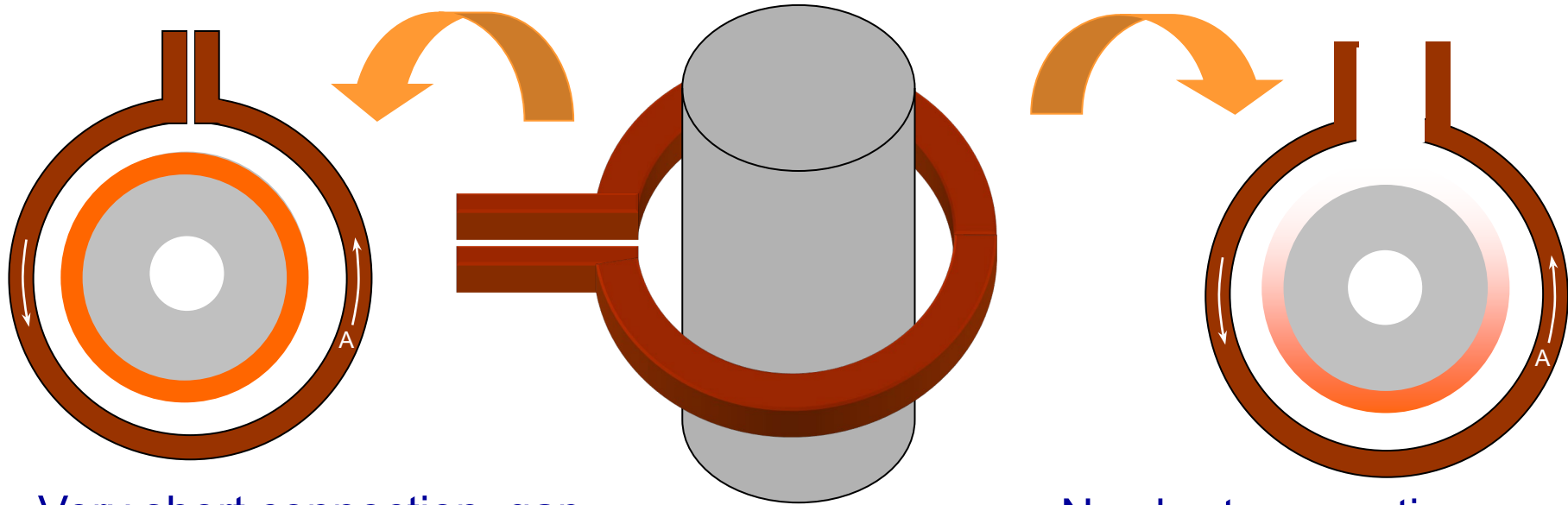


- Very short connection gap
- Piece is centred
- ➡ Uniform magnetic field
- ➡ No rotation is needed

- No short connection gap
- Piece is centred
- ➡ Non uniform magnetic field due to the gap
- ➡ Rotation is needed
- ➡ Piece or inductor can rotate, there is no difference in the magnetic pattern


BASIC INVERTER BRIDGE:

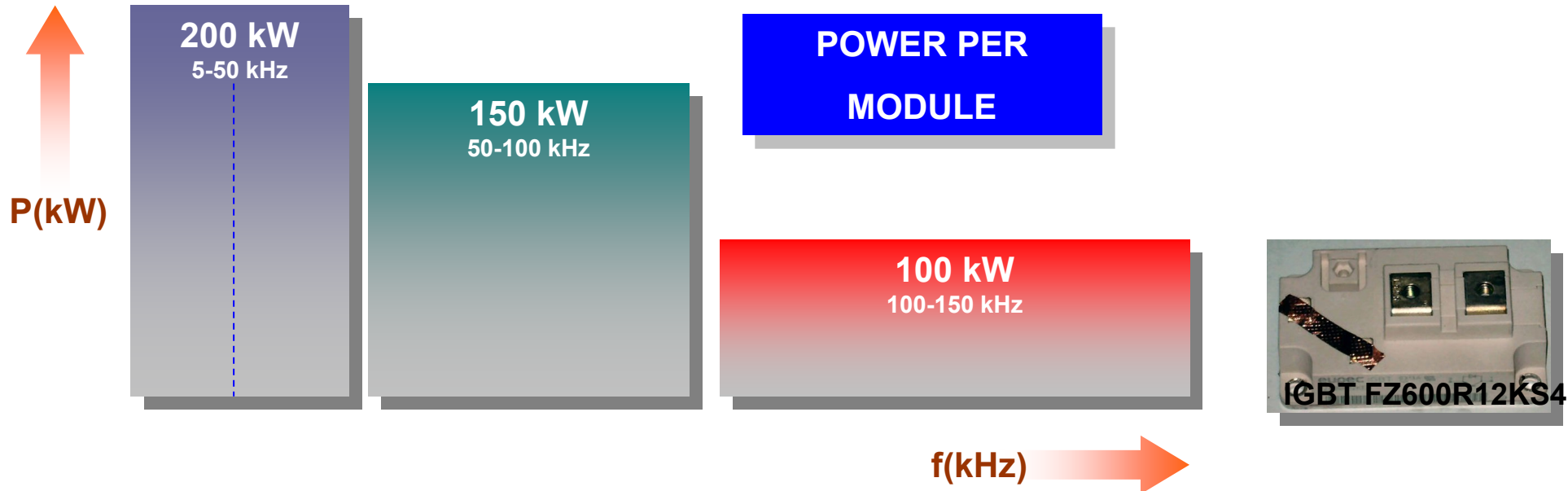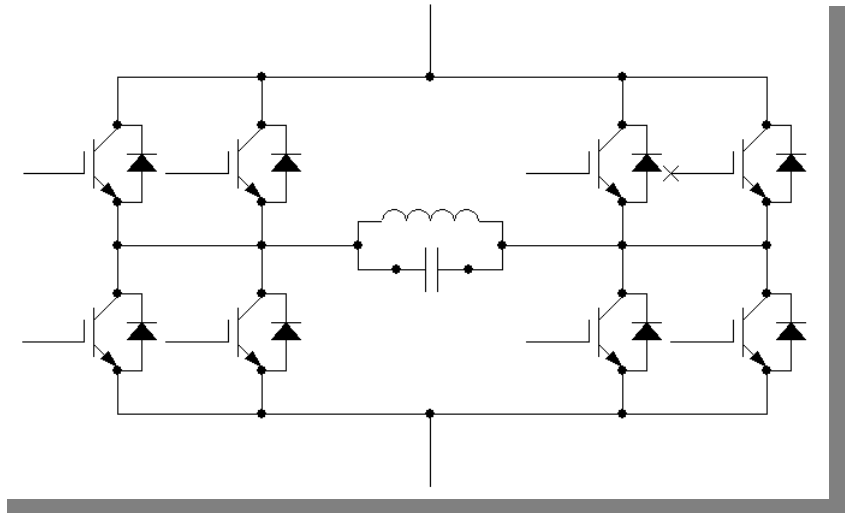- ❑ Current- Fed Inverter **with no diodes** in series with transistors.
- ❑ Frequency = 5 ÷ 150 kHz
- ❑ VMF= 500Veff
- ❑ Two frequencies are possible if both are in the same range: (5-30kHz),(30-50kHz)(50-100kHz)(100-150kHz).
- ❑ Drives cards, Peak detectors and RC networks limit the frequency range.
- ❑ Output power for reliability of 3 ÷ 6 million cycles (*).




INVERTER SIZE:

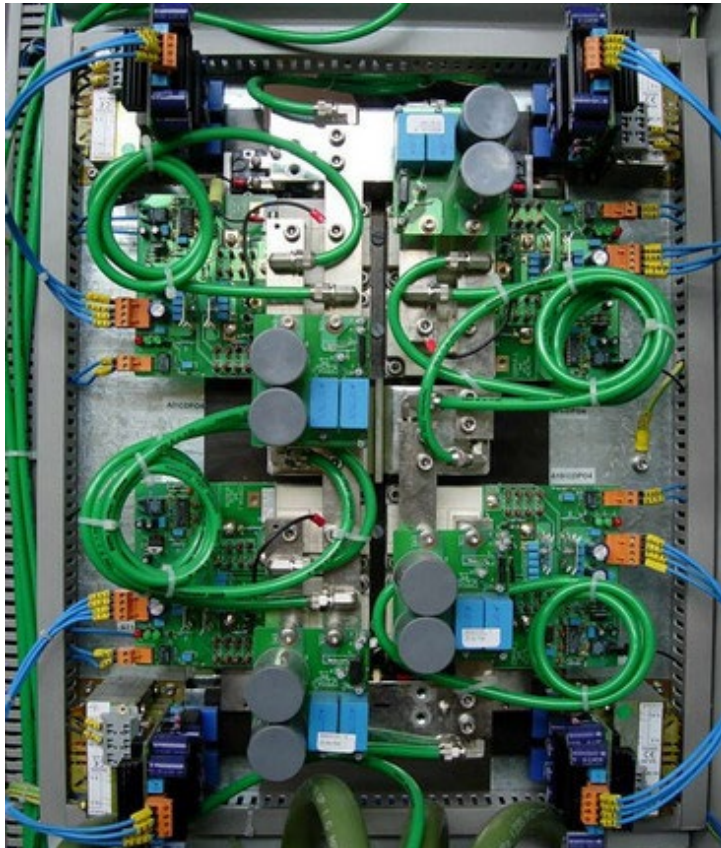
- ❑ 480 x 580 mm.
- ❑ 8 IGBTs FZ600R12KS4 are used- 62mm




APPLICABLE TO UNREGULAR SURFACES

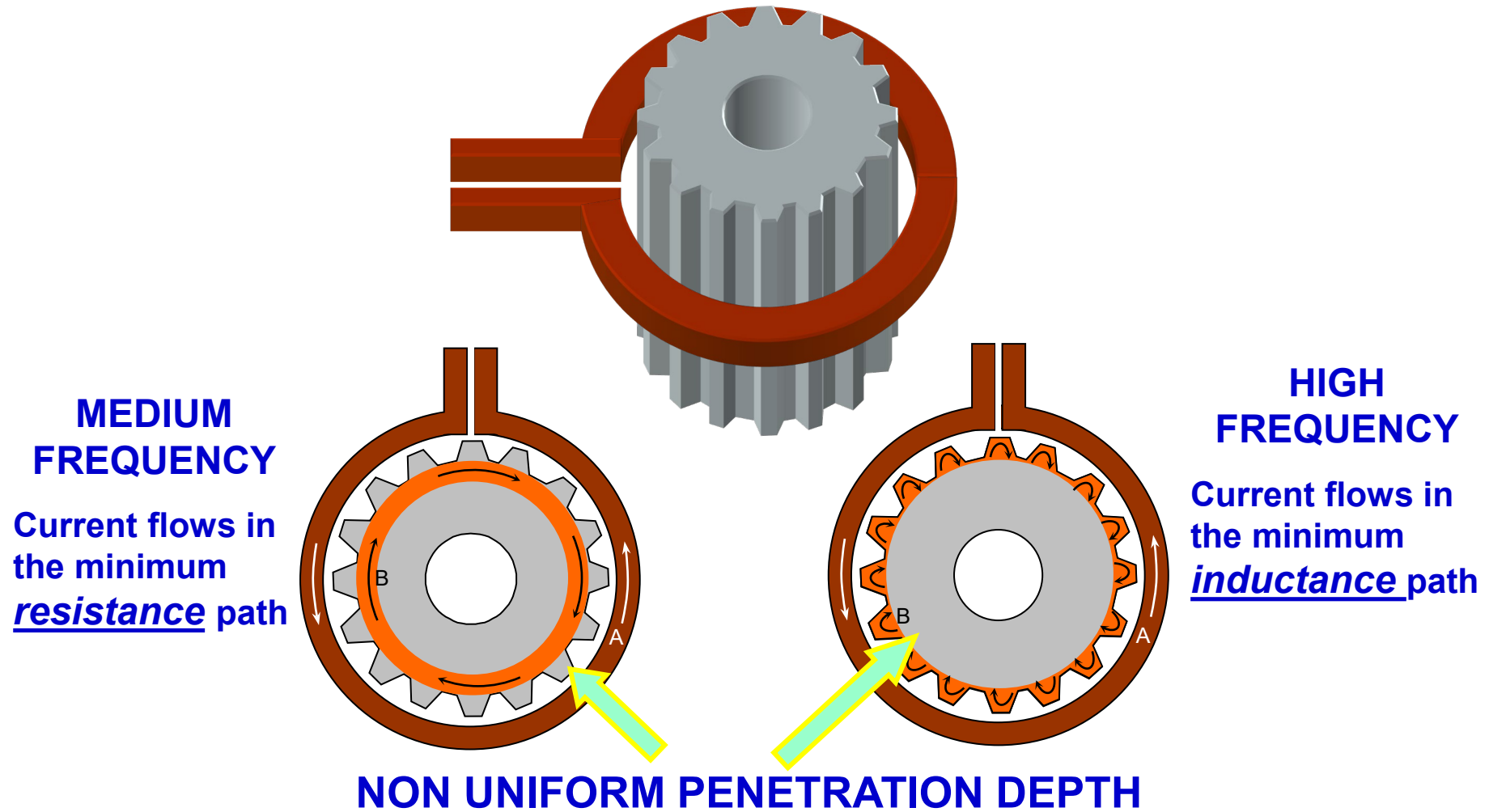

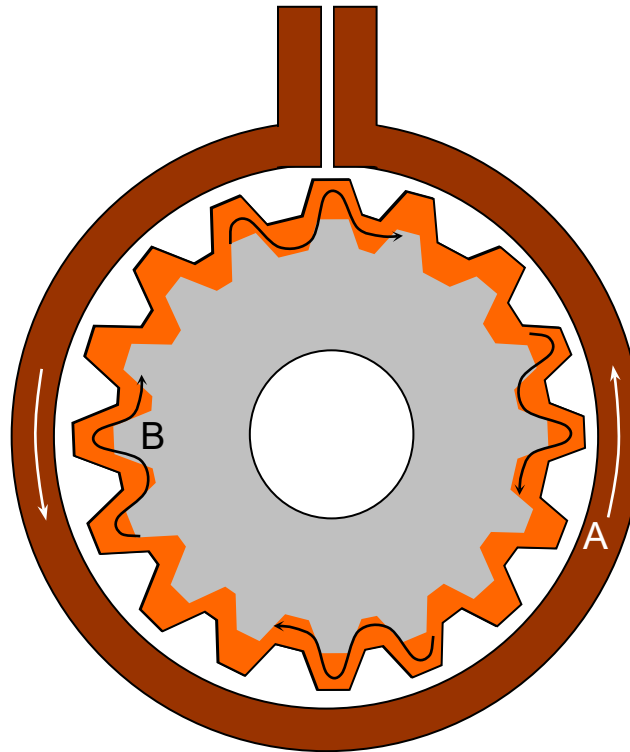
MEDIUM AND HIGH FREQUENCY SIMULTANEOUSLY APPLIED




OPTIMAL
PENETRATION DEPTH QUASI UNIFORM

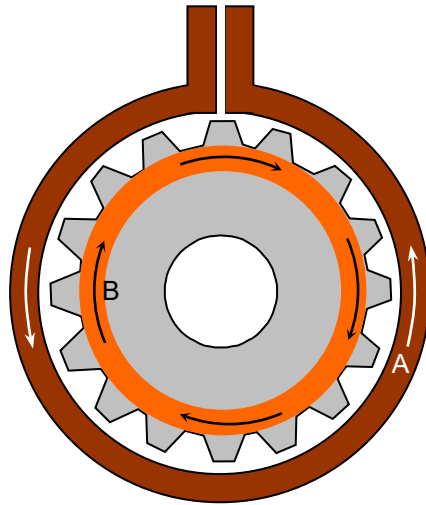

LOW FREQUENCY

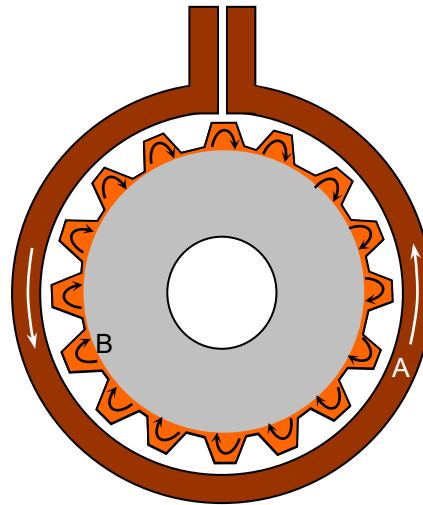

HIGH FREQUENCY

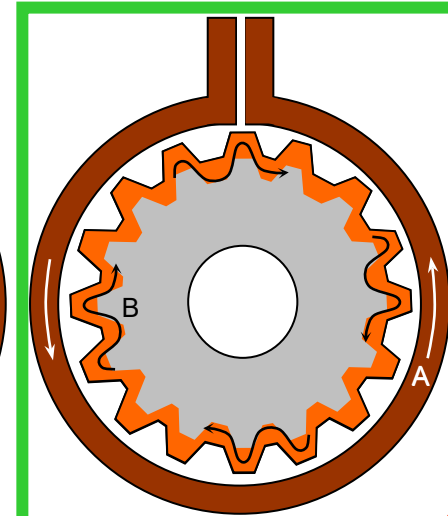

LOW+HIGH
FREQUENCY

**OPTIMUM
HARDENING**





Example: Steering Pinion

Heating time: 90 ms

Applied power: 450 kW MF + 480 kW HF simultaneously

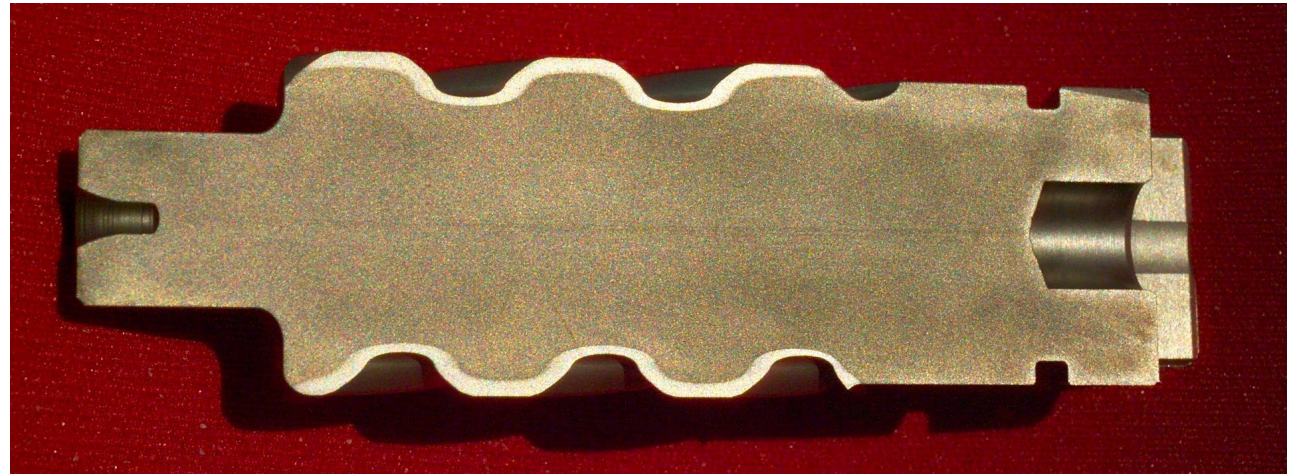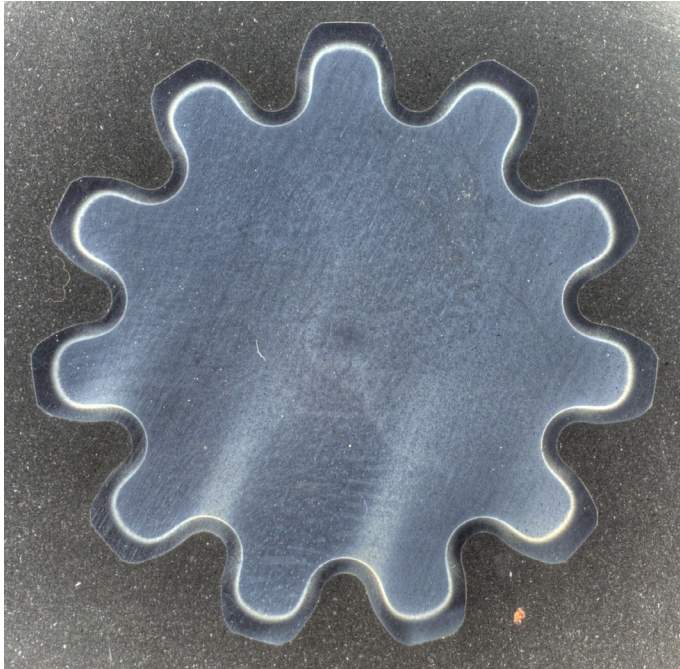Frequencies used: 11 kHz MF and 320 kHz HF




Example: Bevel Gear


Heating time: 200 ms

Applied power: 580 kW MF + 580 kW HF simultaneously

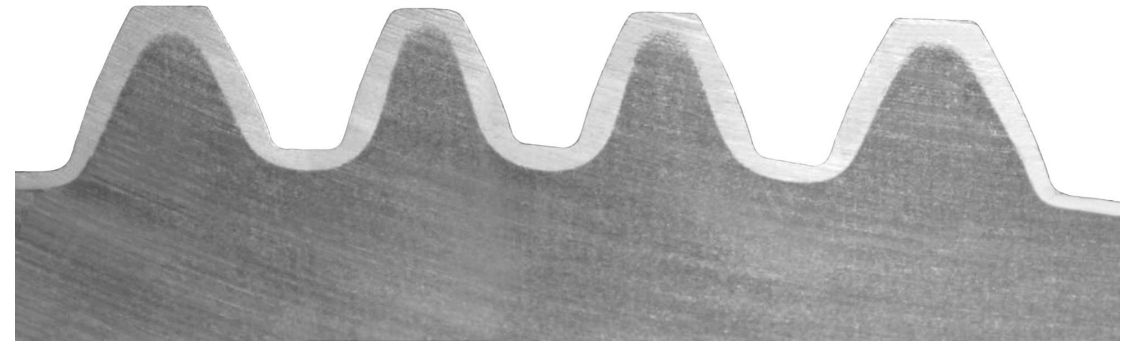
Frequencies used: 10 kHz MF and 230 kHz HF






INVERTERS: Voltage-fed

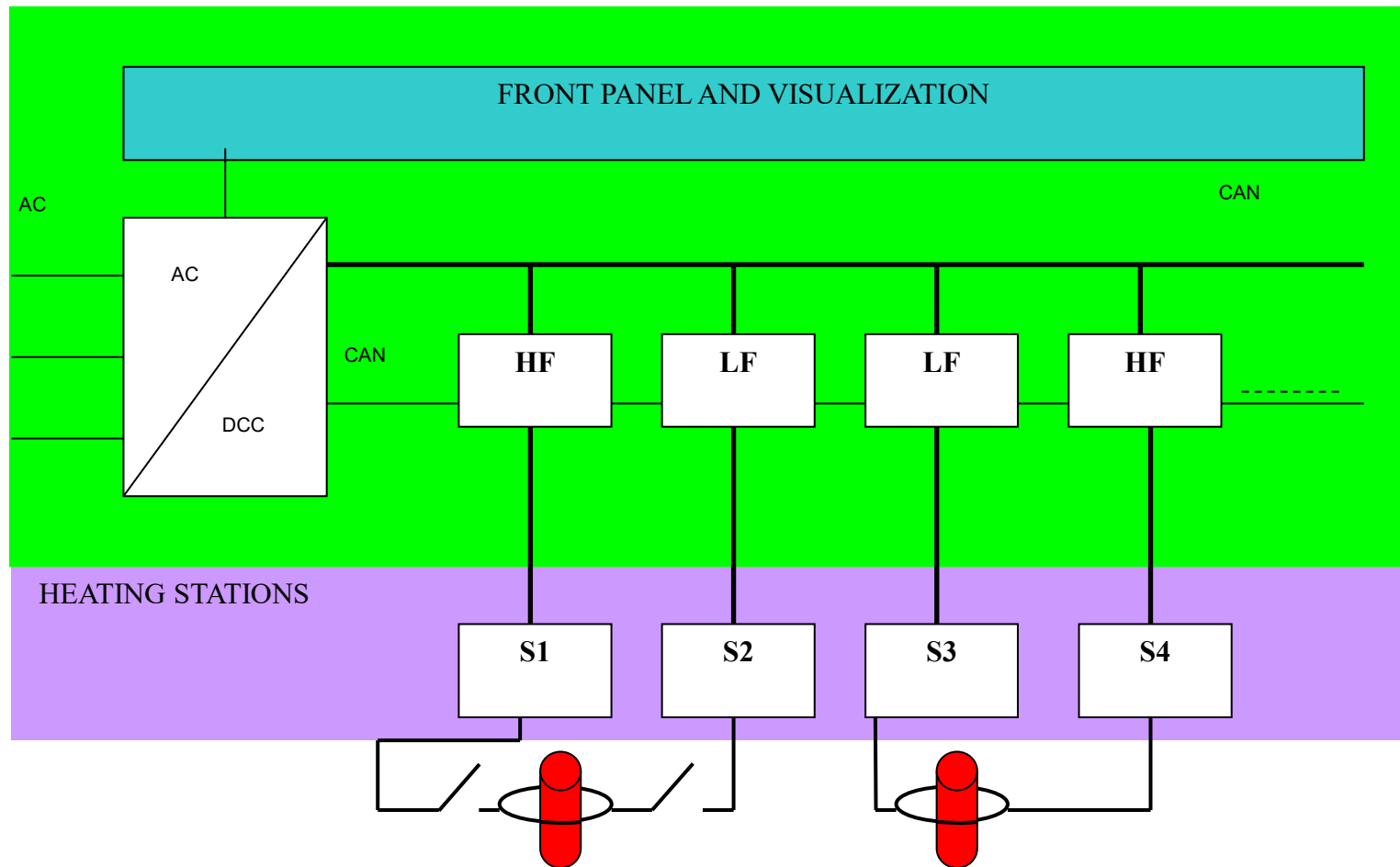


SEQUENTIAL SYSTEMS

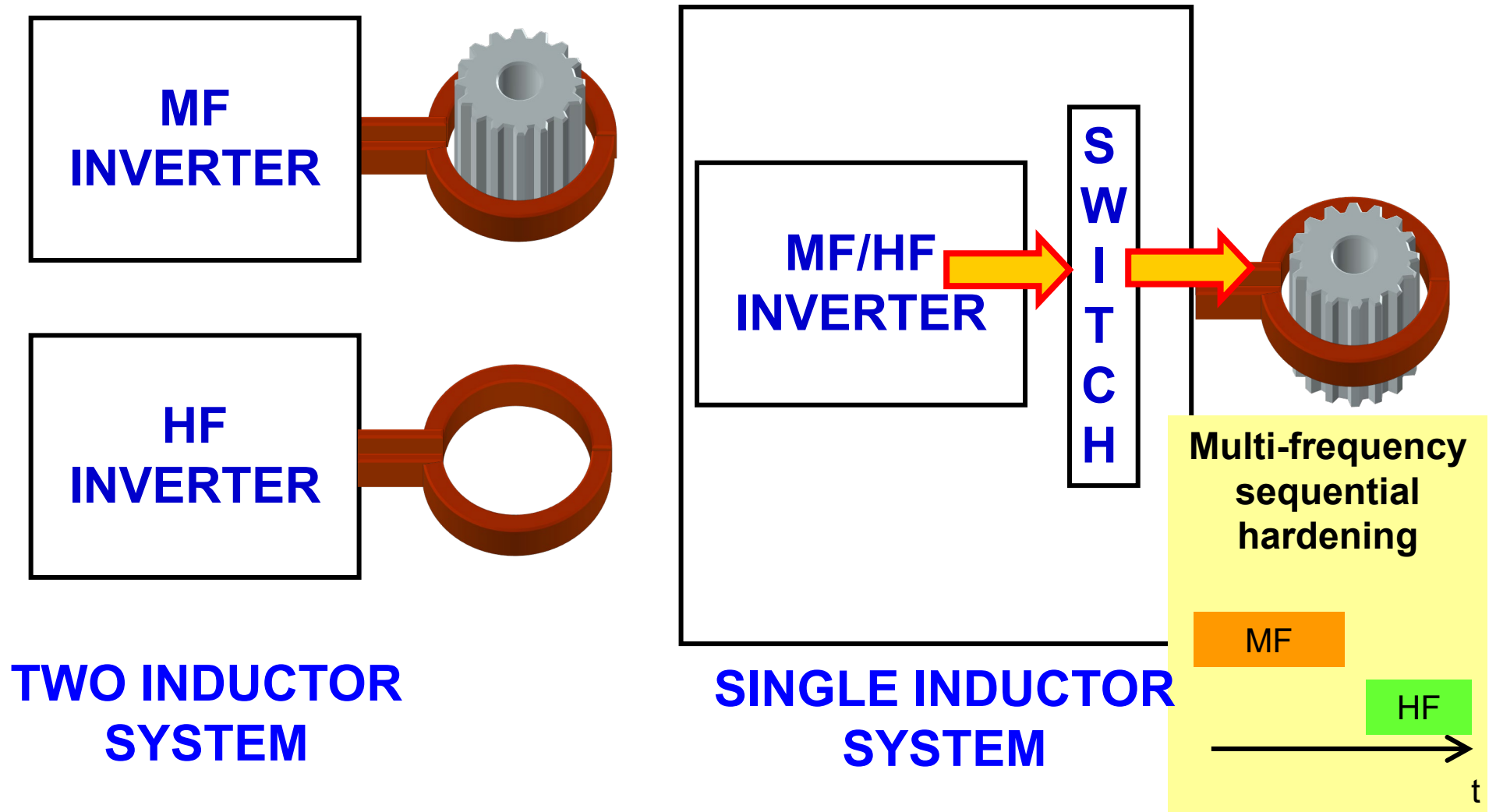

SIMULTANEOUS SYSTEMS

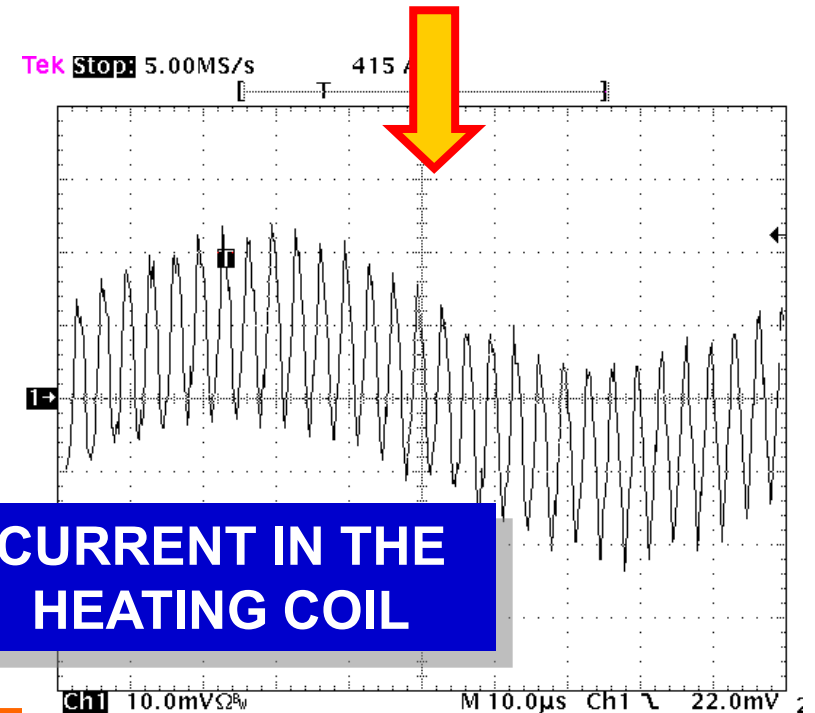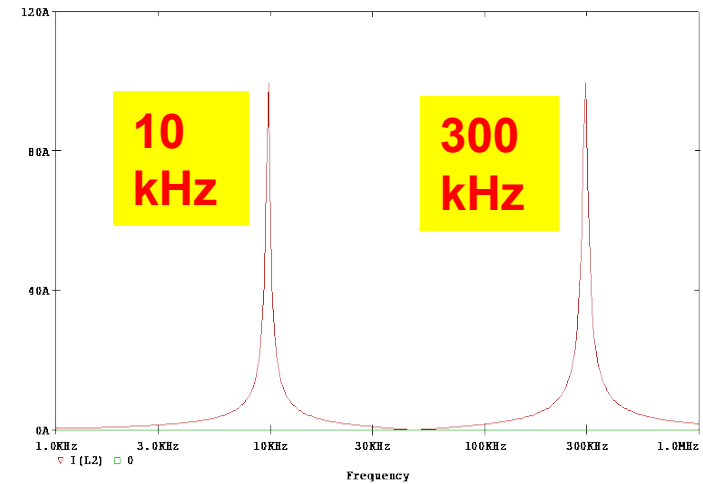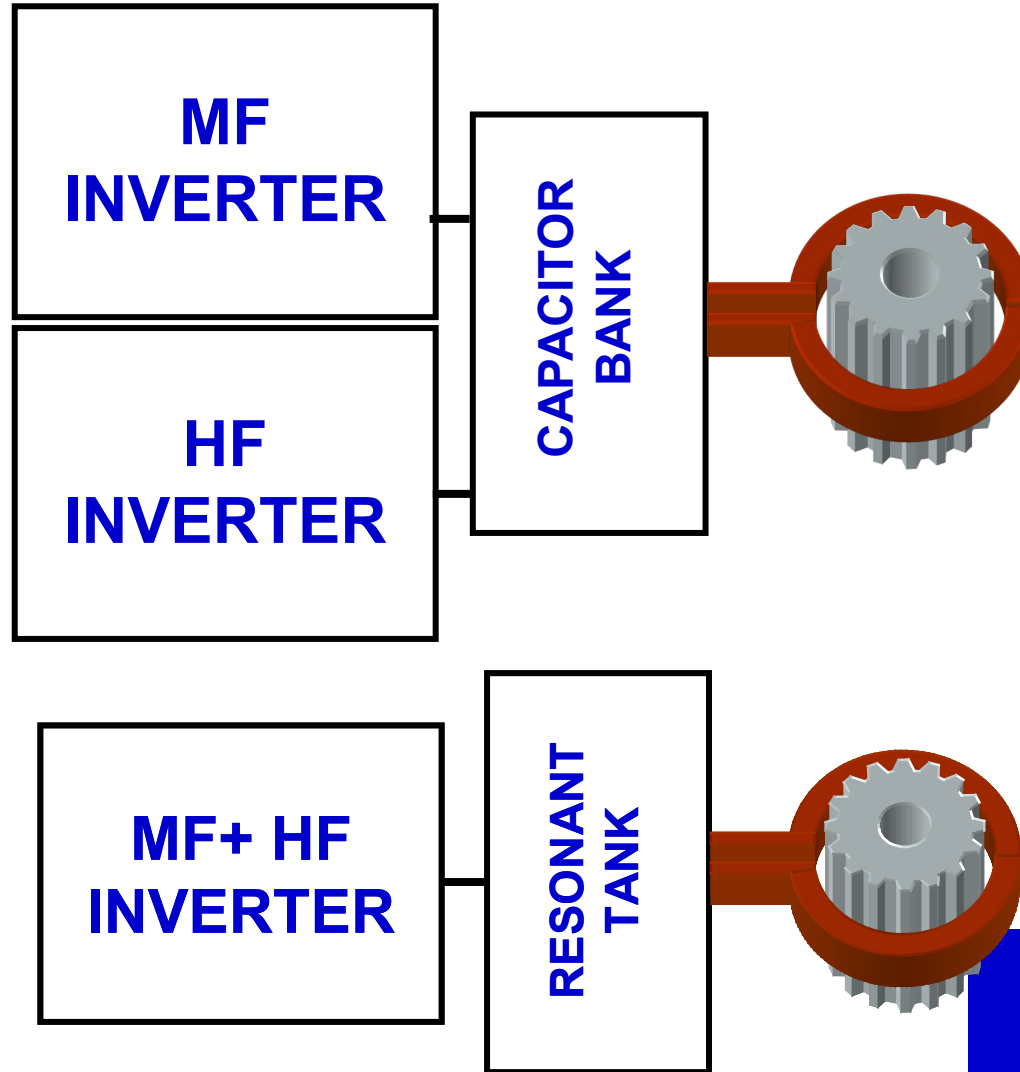

4 REACTIVE COMPONENTS

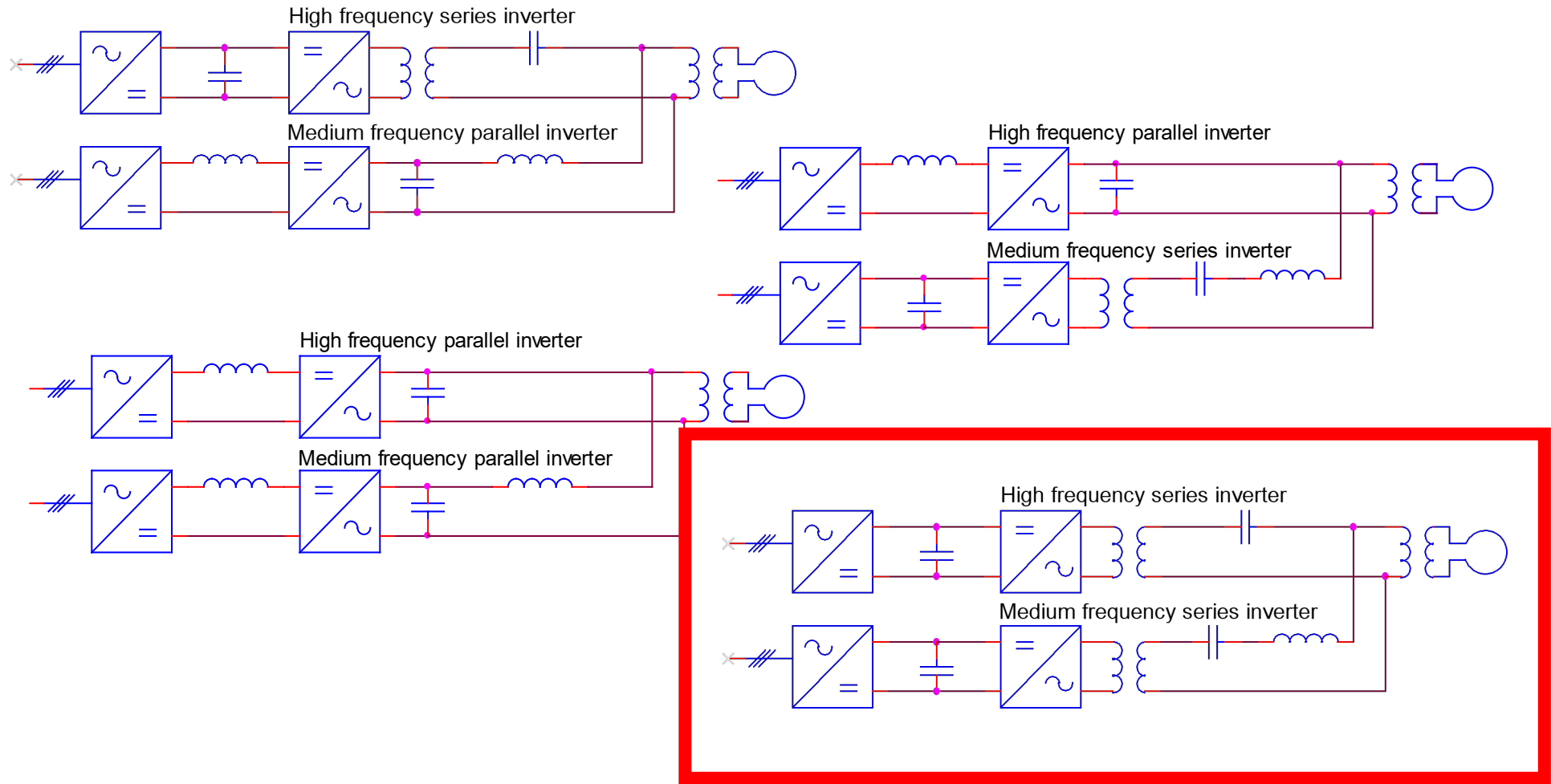


- ✓ Basic Concepts in Induction Heating
- ✓ Compensation of the Load
- ✓ Series Resonant Converters for IH
- ✓ Parallel Resonant Converters for IH
- ✓ Semiconductors used in IH
- ✓ **Applications**
 - ✓ Forging
 - ✓ Hardening
 - ✓ **Multipurpose Generators**
 - ✓ Bonding
 - ✓ Welders
- ✓ Controllers
- ✓ Roadmap

APPLICATIONS


- Processes which require more than one heating treatment, and usually two generators: **HARDENING AND TEMPERING.**
- **WIRE HEATING:** Several heating lines, with independent power control.
- **PAPER DRYING:** With power control at different areas of the roller.



MULTI-OUTPUT

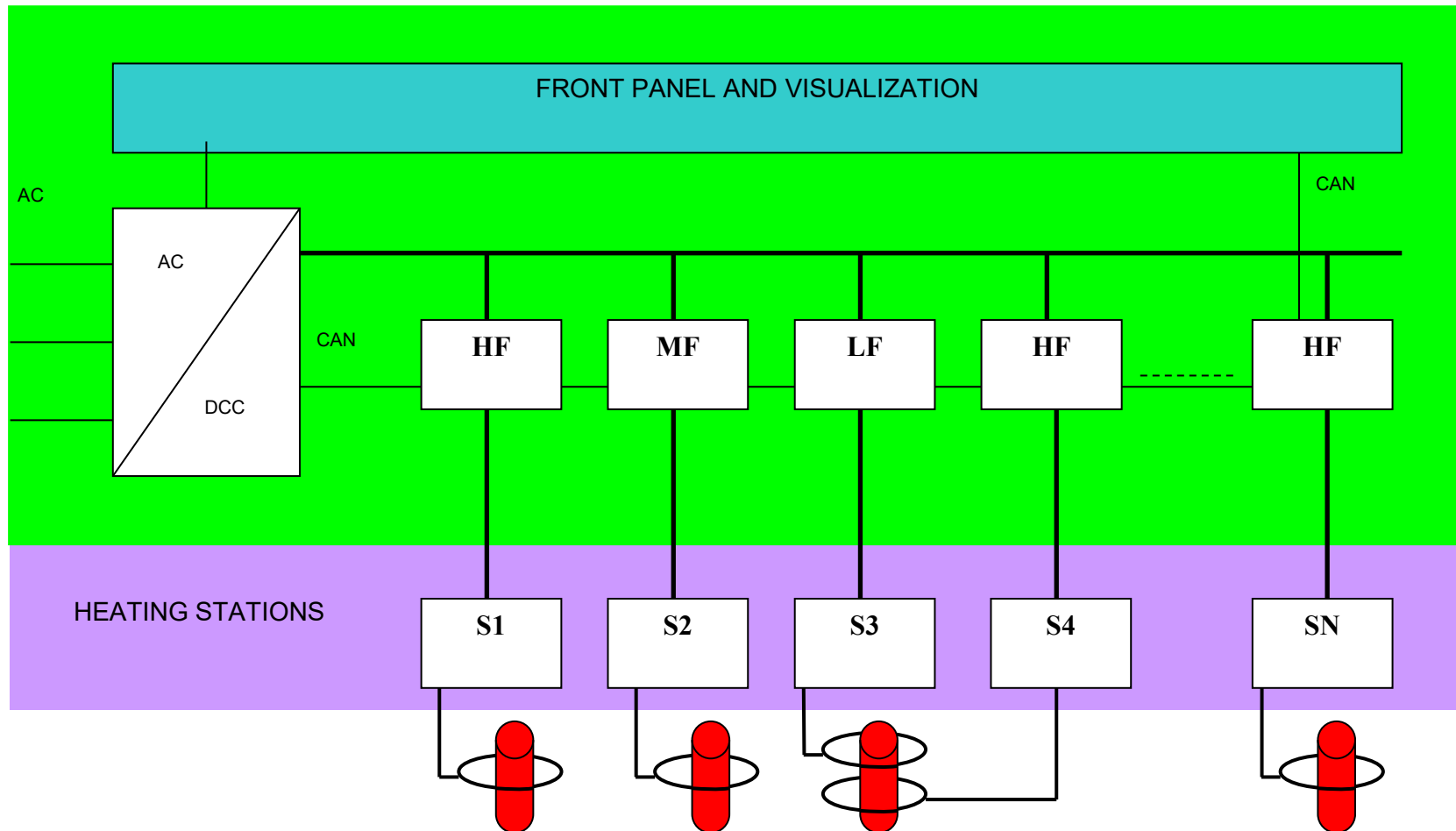

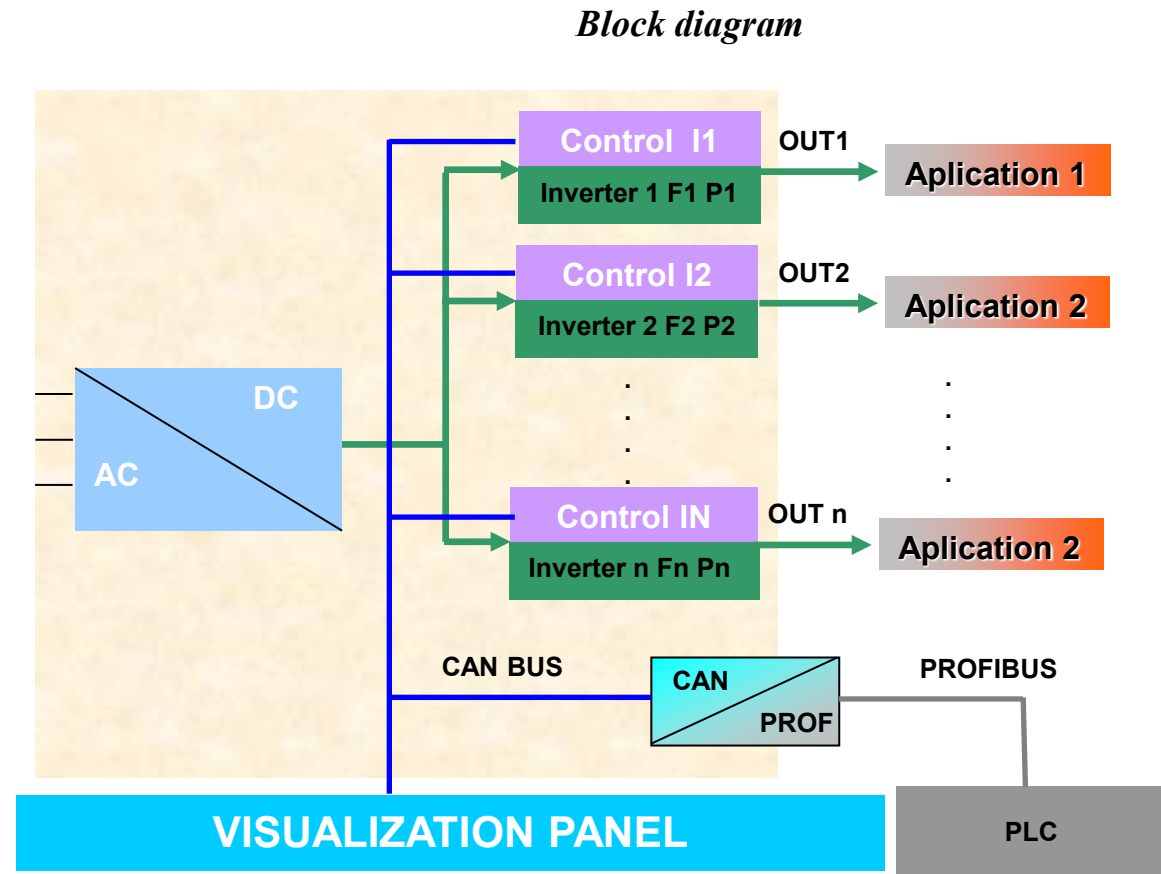
- It has several independent outputs. Power can be regulated separately. It is, in fact, as several generators in one single system.
- It has as many inverter bridges as outputs.
- It has as many controllers as outputs.
- It has one single control panel.
- Communication system integrated in the control panel.
- Total power of the system is the addition of all output powers.



MULTI-OUTPUT GENERATOR




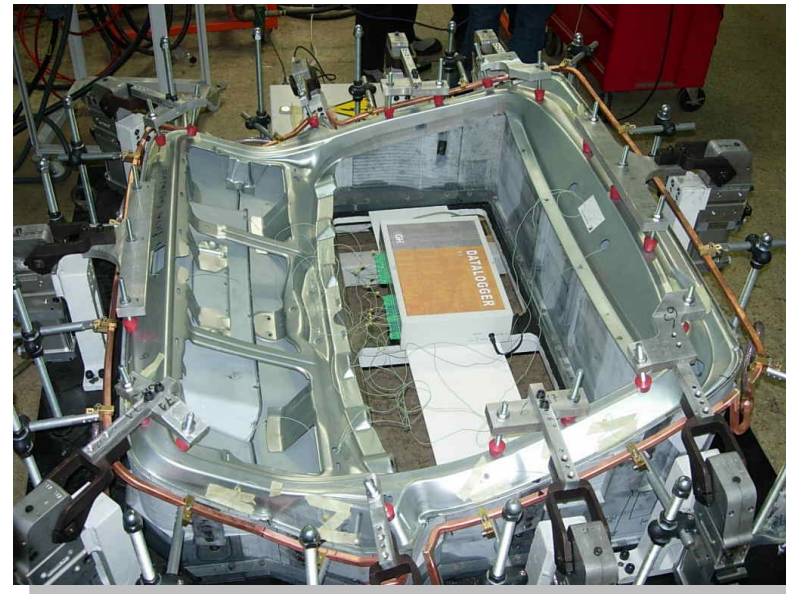- ✓ Basic Concepts in Induction Heating
- ✓ Compensation of the Load
- ✓ Series Resonant Converters for IH
- ✓ Parallel Resonant Converters for IH
- ✓ Semiconductors used in IH
- ✓ **Applications**
 - ✓ Forging
 - ✓ Hardening
 - ✓ Multipurpose Generators
 - ✓ **Bonding**
 - ✓ Welders
- ✓ Controllers
- ✓ Roadmap



Bonding

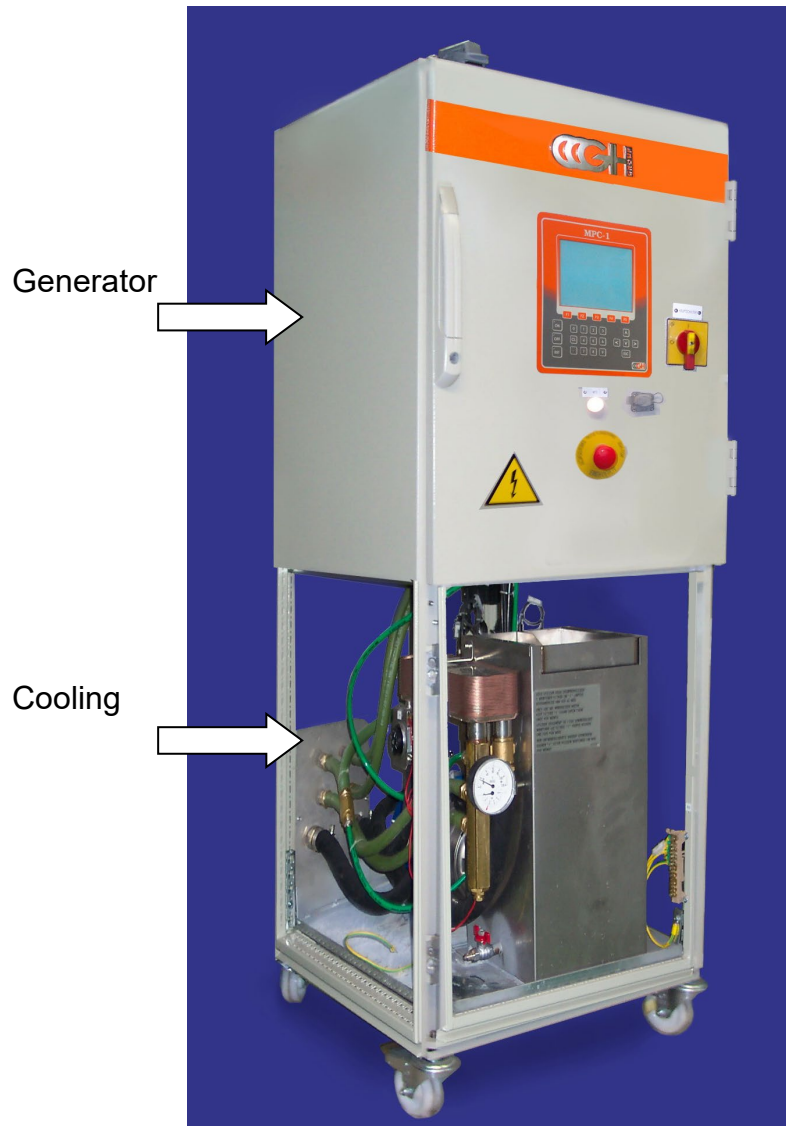Is a process used in the automotive industry for increase the resistance to corrosion the doors, hood of the car etc. It consists in heating a glue to about 200 °C so that it polymerises. This process is usually done by induction heating



POWER SECTION :

- Output power: 30 kW (inverter with half-bridge) and 40 kW.
- Up to 3 heating stations (commutation system included in the generator).

CONTROLLER:

- Digital controller for converter and process control in only one PCB.
- Industrial communication: Interbus, Profibus, Device-Net or conventional wiring.
- Graphical display.



TYPICAL FEATURES:



Programmable from the control panel or from a PC, through USB port or Ethernet.

Graphical or numerical representation of the temperature, power and energy evolution of any heating cycle.

Up to 8 temperature sensors for signal regulation. It is possible to select a master sensor or calculate the average value of all of them.


Up to 15 programs with 9 phases each (heating, stop and cooling).

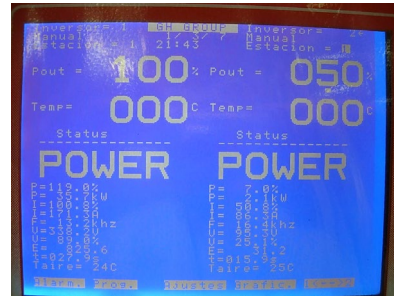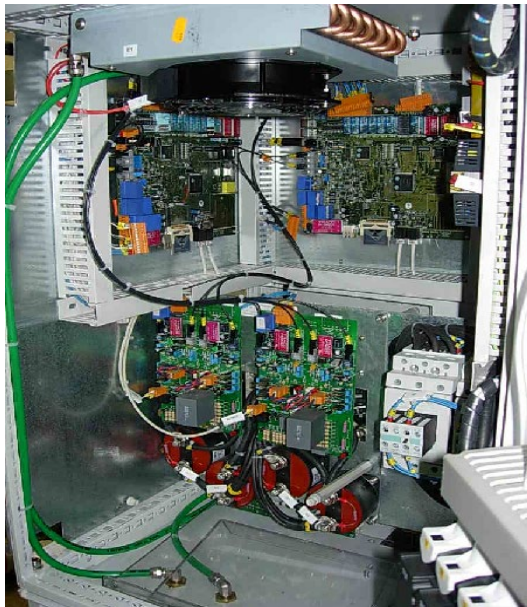- **Storage of up to 1000 heating cycles in the control panel.**
- **Quality control functionality via Ethernet. Unlimited heating cycles storage in an SQL database.**
- **Several user level with password protection (security control).**




ADDITIONAL TYPICAL FEATURES:

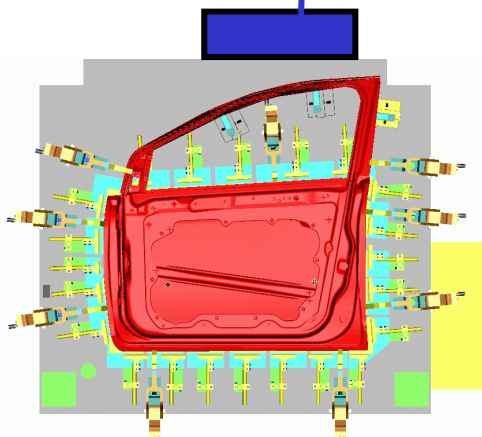- Simultaneous heating in two working power sections. One control panel.
- It works like two independent converters.
- Output power = 2 x 30 kW or 2 x 40 kW
- Each power section can have up to three output power outlets so that Dual System can manage up to six heating stations (only two simultaneous).





Heating station 1

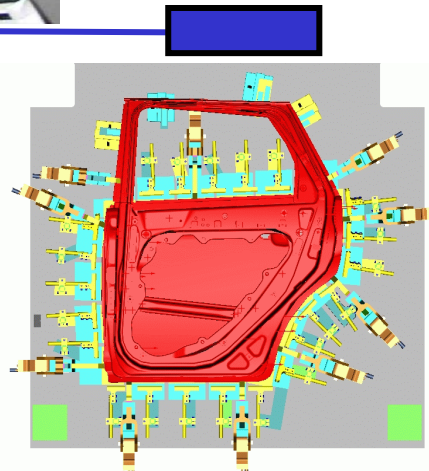


Heating station 2


TYPICAL FEATURES:

- Temperature measurement of up to 16, 32 or 48 channels.
- Data can be shown by graph or by table. Table can be exported to MS Excel file format.
- Data visualization and acquisition directly from PC software. Acquisition via USB or CANBus.
- Can be supplied from batteries (online) or mains power supply (offline). Battery level and charge led indicator.
- High noise rejection. Channels with galvanic isolation eight by eight.
- Mass storage memory. It can save up to 1000 heating process.
- Temperature data and graphs can be printed.

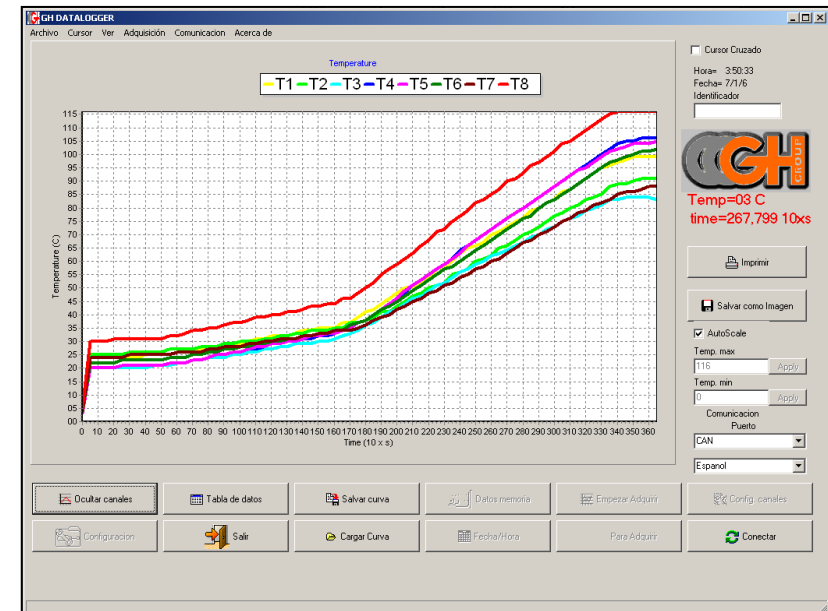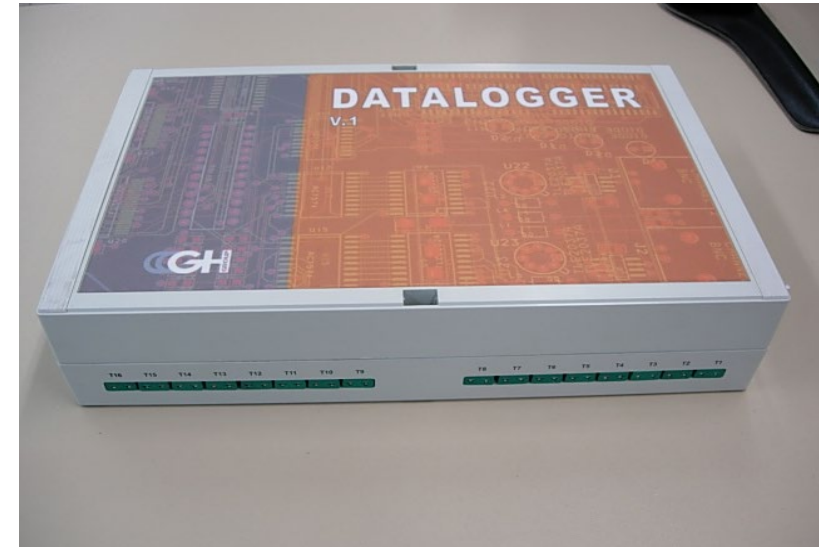

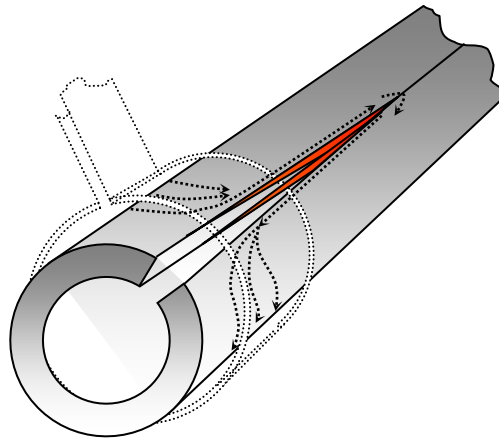
- ✓ Basic Concepts in Induction Heating
- ✓ Compensation of the Load
- ✓ Series Resonant Converters for IH
- ✓ Parallel Resonant Converters for IH
- ✓ Semiconductors used in IH
- ✓ **Applications**
 - ✓ Forging
 - ✓ Hardening
 - ✓ Multipurpose Generators
 - ✓ Bonding
 - ✓ **Welders**
- ✓ Controllers
- ✓ Roadmap



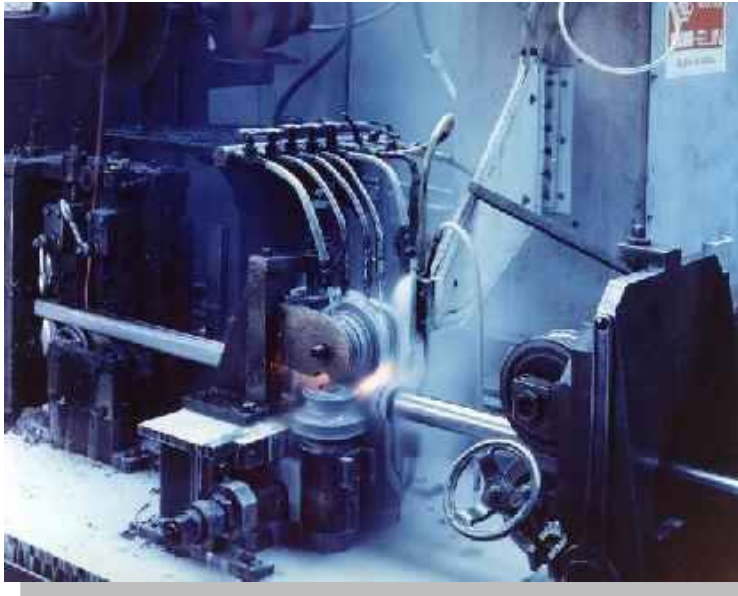

Tube welding is industrial heating application that requires in general the combination of high power and high frequency. Power ranges from 100 kW to 1,5 Mw or even higher and typical frequencies are between 200 and 400 kHz.

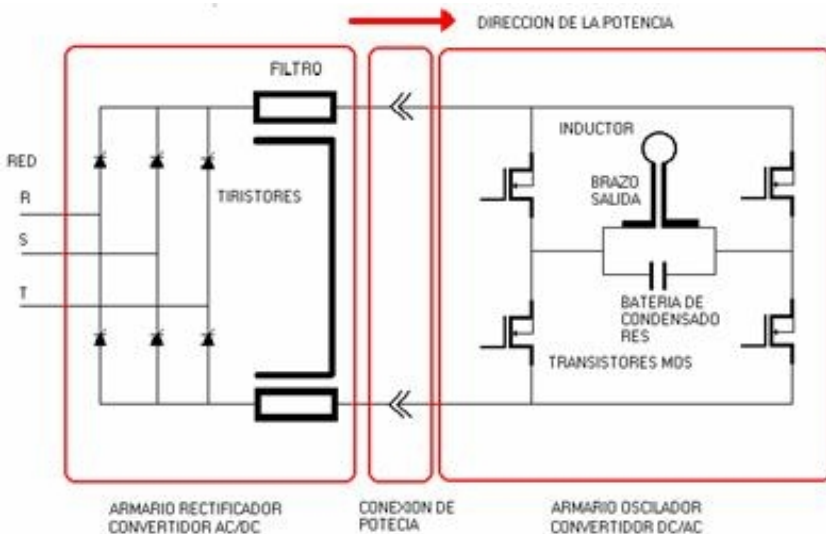Basic welders are current-fed as well as voltage-fed inverters a used in practice although the first topology is preferred due to the fact that the power supply can be separated from the inverter, which has to be very close to the application. In this case a lighter coordinate table is required.



Basic Welders

- ☐ Current-fed or Voltage-fed structure
- ☐ In Current-fed Converters the inverter can be separate from the power supply enabling a lighter coordinate table
- ☐ Frequencies in the range 200-500 kHz for most of the welding applications
- ☐ Power levels in the range 100-1.000 kW
- ☐ MOS (up to 500 kHz) or IGBT (up to 300 kHz) technology.



GOAL:

- ✓To obtain the maximum output power from the generator for every tube of the inductor range.
- ✓To get maximum generator output power for a range of pipes, regardless its thickness.

TUBE LOAD MATCHING SYSTEM:

-One method consists of an increase of the inverter current according to the following equation:

$$I_{dc} = \sqrt{\frac{Q_{max}}{Q_{min}}} \cdot Id_{cn}$$

- The apparent power of the input transformer and the current rate of the rectifier has to be increased.
- The capacitor bank has to be increased.
- Higher number of inverters is needed.

MAIN FEATURES:

- Automatic load matching while system is running.
- No moving parts.
- Good efficiency.
- Minimum reactive power needed, compared with other solutions.


GOAL:

✓ To modify the working frequency of the generator while running, in order to weld different materials with the same equipment and to select the best frequency for every tube:

- The higher the frequency, the less the power is required.
- Lower Frequency provides a more ductile welding
- Lower frequency is preferred for internal scarfing as the tools have longer life

VARIABLE FREQUENCY SYSTEM:

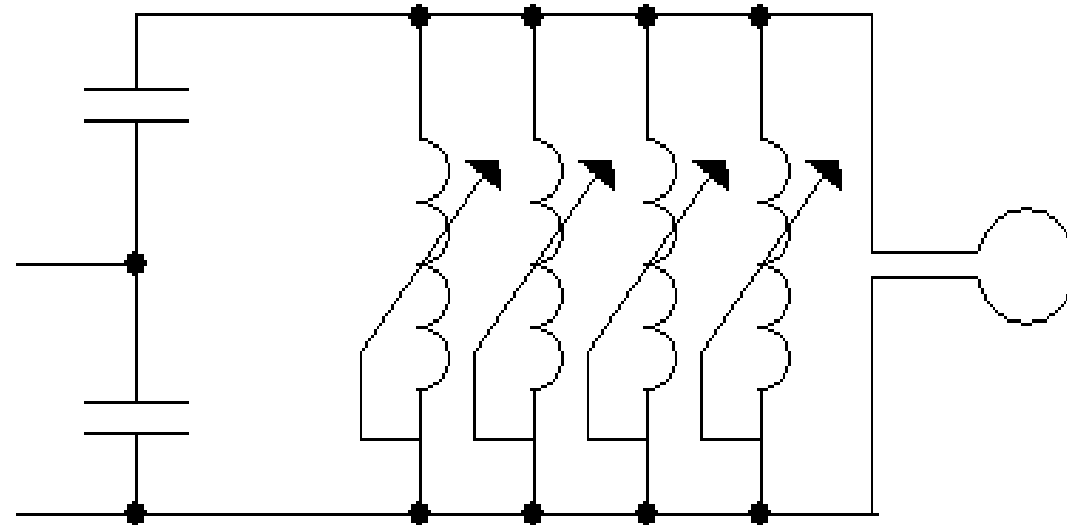- The system consists in four coils (3 turns) with a moving copper watercooled core.
- The power of the generator is increased in order to compensate the losses of the system.



GOAL:

- To modify the working frequency of the generator while running, in order to weld different materials with the same equipment and to select the best frequency for every tube:
- The higher the frequency, the less the power is required.
- Depending on the specification of the customer, varying the frequency results in different mechanical properties of the welding beam:



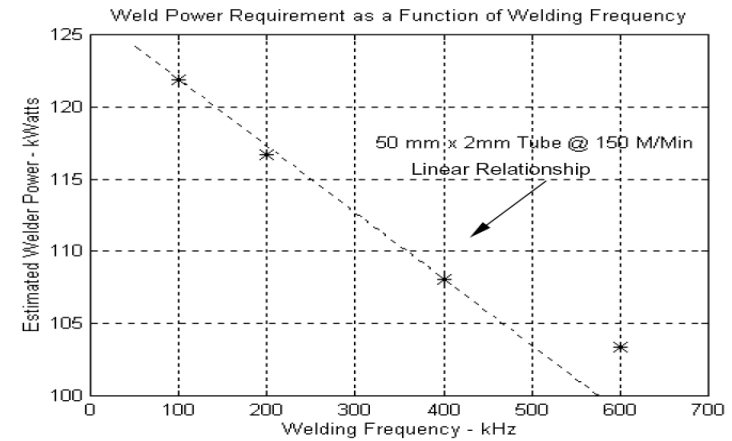


Figure 15

Ductile welding

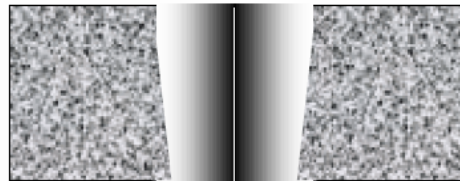

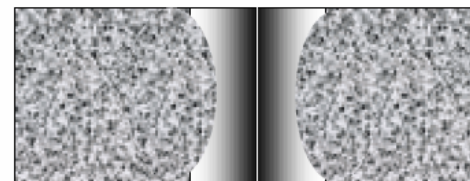Typical Heat Affected Zone for a 200 kHz welder.



Typical Heat Affected Zone for a 400 kHz welder.


Fragile welding

- Variable frequency results in repetitive quality of the welding by readjusting the optimal frequency.
- Lower frequency is preferred for internal scarfing as the tools have longer life




fmin




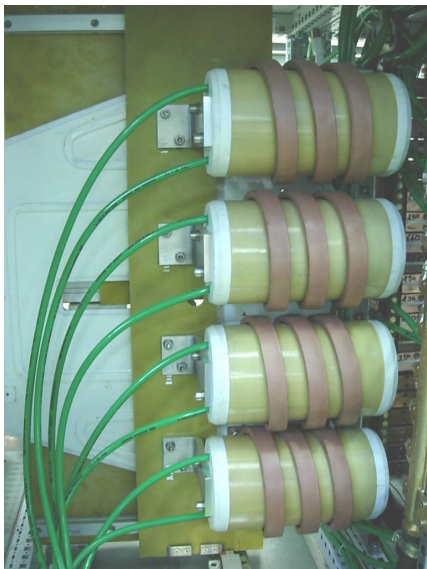
$$I_{dc} = \sqrt{\frac{Q_{\max}}{Q_{\min}}} \cdot \sqrt{\frac{f_{\max}}{f_{\min}}} \cdot I_{dcn}$$



fmax

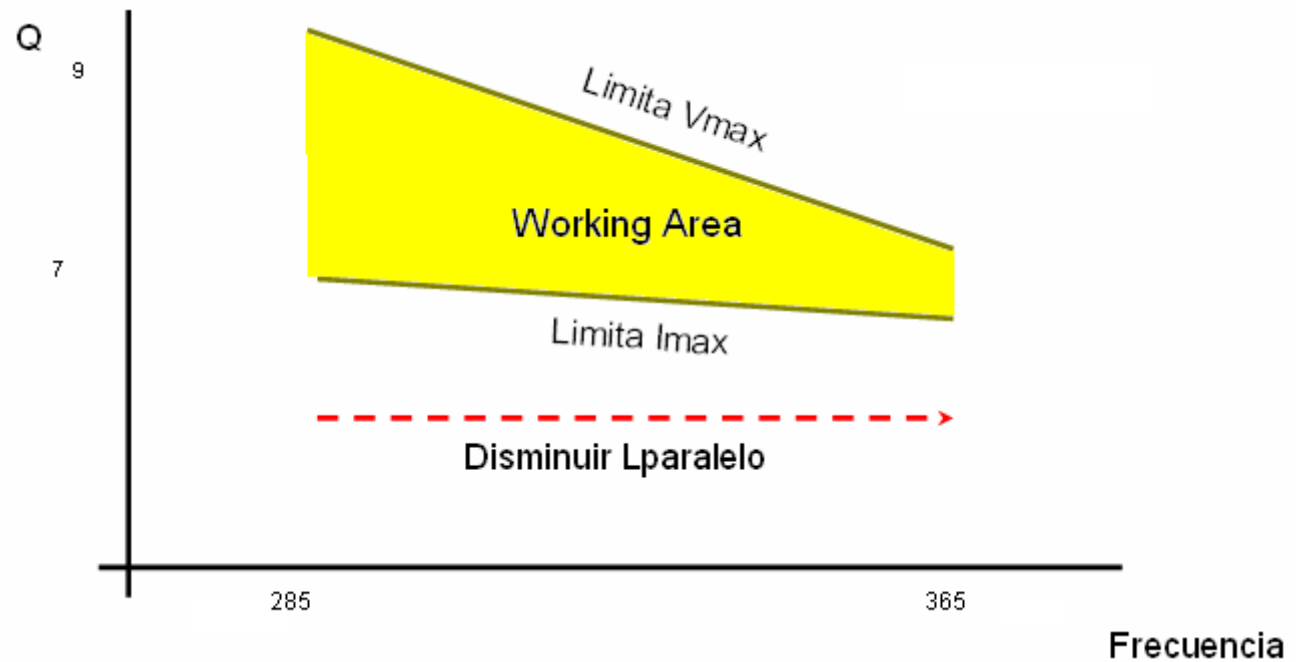
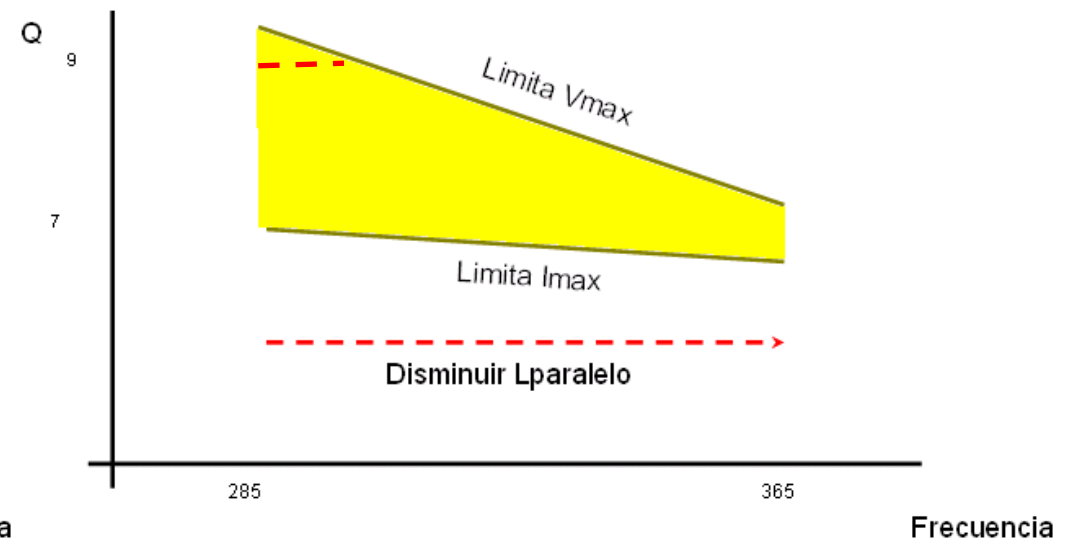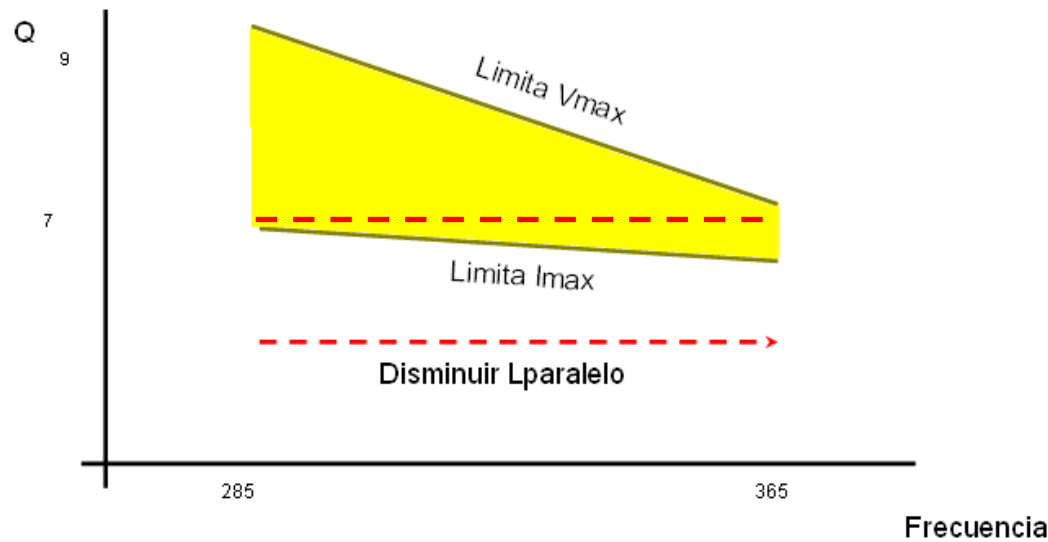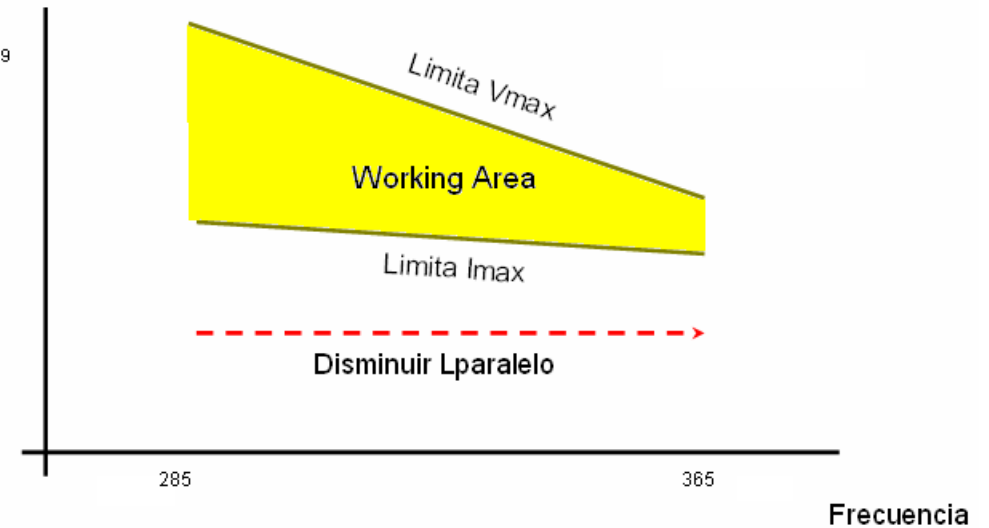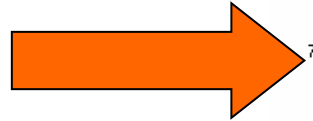
$$I_{dc} = \sqrt{\frac{Q_{\max}}{Q_{\min}}} \cdot \sqrt{\frac{f_{\max}}{f_{\min}}} \cdot I_{dcn}$$



Wide range of frequency variation for steel tubes

Other non-ferrous materials can be welded even though higher Q is needed




BASIC TUBE WELDING CONTROL:

- Manual mode.
- Automatic mode (Power-Speed control).
- Adaptative mode (Easy Power-Speed control).
- Graphs: Generator parameters (Voltage, Current, Frequency, Power).
- Alarms.


ADVANCED TUBE WELDING CONTROL:

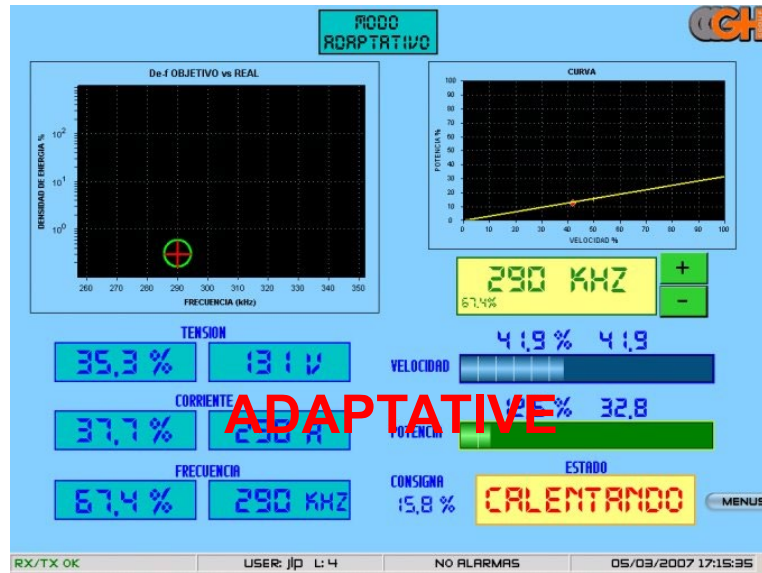- Manual mode.
- Automatic mode (Power-Speed control).
- Adaptative mode (Easy Power-Speed control).
- Graphs: Generator parameters (Voltage, Current, Frequency, Power).
- Alarms.
- Advanced system for maintenance.
- Frequency variable control if present in the generator.






ADAPTATIVE

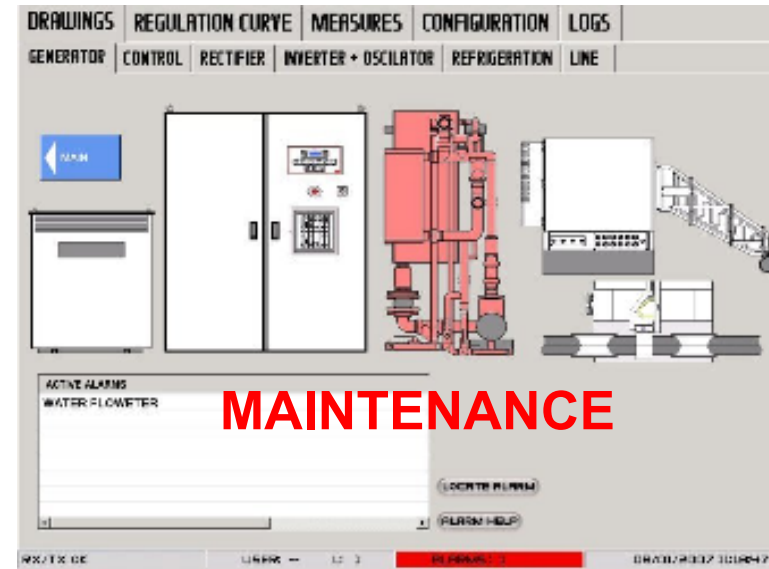

MAINTENANCE

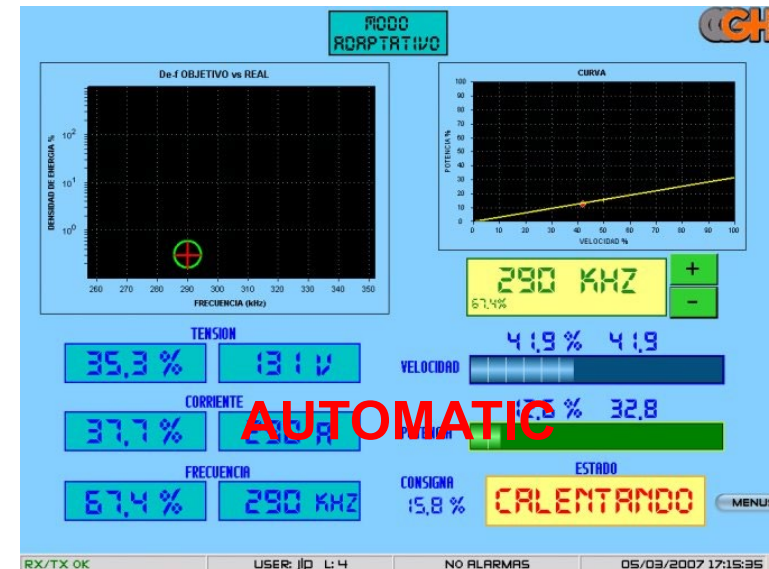

AUTOMATIC

- ✓ Basic Concepts in Induction Heating
- ✓ Compensation of the Load
- ✓ Series Resonant Converters for IH
- ✓ Parallel Resonant Converters for IH
- ✓ Semiconductors used in IH
- ✓ Applications
 - ✓ Forging
 - ✓ Hardening
 - ✓ Multipurpose Generators
 - ✓ Bonding
 - ✓ Welders
- ✓ **Controllers**
- ✓ Roadmap

PAST



ANALOG CONTROL

PRESENT



FUTURE



CAN




FULL DIGITAL CONTROL

FEATURES OF THE FULL DIGITAL CONTROL

- The new digital control gives a new look to our generators and also new functionalities.
- The graphical screen shows the information more clearly in a wider screen.
- The settings of the generator are entered in a configuration screen through the keyboard instead of using potentiometers. Different settings can be stored in the memory for different running conditions.
- It is possible to manage the generator from a PLC system through a PROFIBUS network.
- The cooling system can be configured and monitored from the visualization pannel MPC-1.


PRESENT

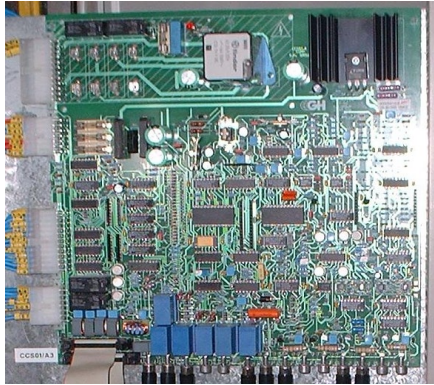

ANALOG CONTROL



DIGITAL VISUALISATION

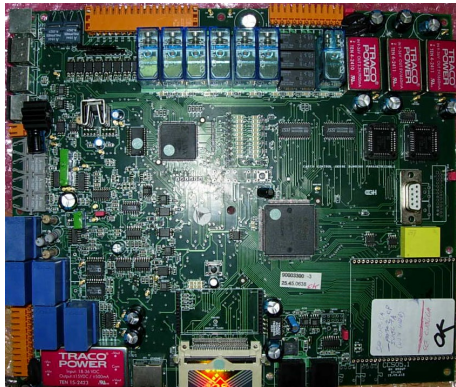


DIGITAL CONTROL



DIGITAL VISUALISATION

FUTURE

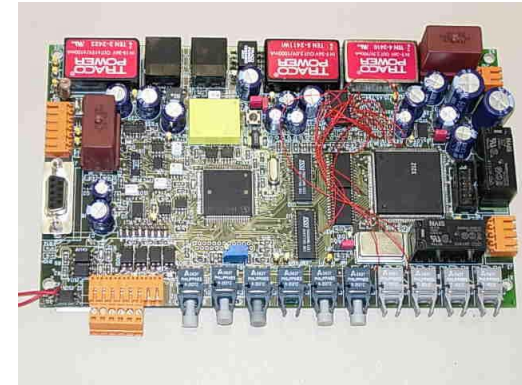

FULL DIGITAL CONTROL




DIGITAL VISUALISATION

FEATURES


- Power section control loops are fully digital.
- Inverter control and application control parameters could be upgraded from a PC software.
- High and low frequency applications.
- Inverter bridge alarms management and application data acquiring included on board.
- CAN-BUS module connection. It simplifies and decrease wiring and error possibility.
- Through CAN-BUS system could be expanded for more stations, application measuring channels, etc.
- Energy measurement with high accuracy.
- Mass data storage. It can save heating process data, alarms history, etc.
- Heating process could be adjusted with a cycle controlled with 9 different heating phases. Energy or temperature cycles. On this way, this cycle could be adjusted for any type of part.
- Could control continuous applications. For example Power/Speed control.
- Could manage visualization and control for small size generators

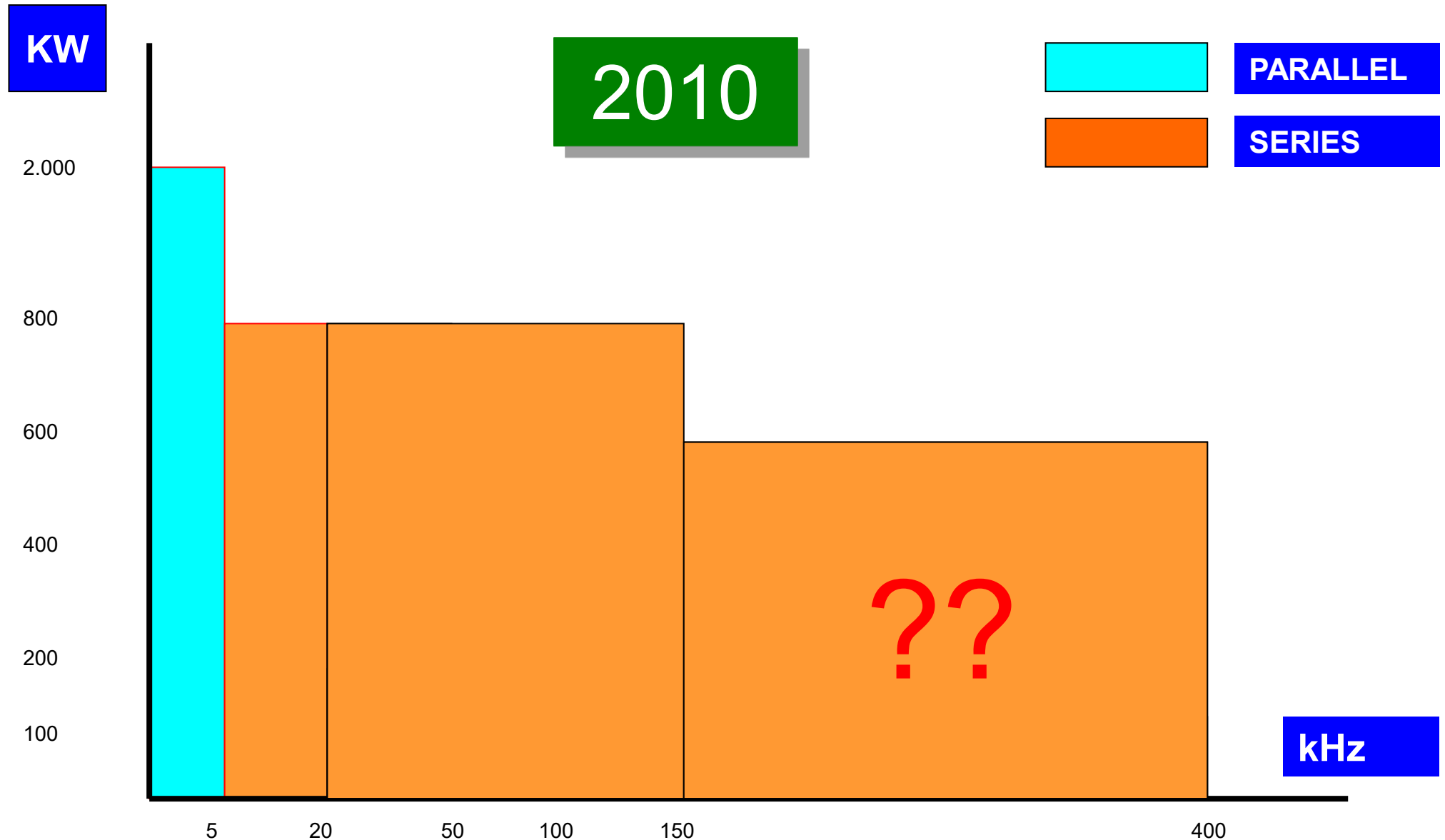- ✓ Basic Concepts in Induction Heating
- ✓ Compensation of the Load
- ✓ Series Resonant Converters for IH
- ✓ Parallel Resonant Converters for IH
- ✓ Semiconductors used in IH
- ✓ Applications
 - ✓ Forging
 - ✓ Hardening
 - ✓ Multipurpose Generators
 - ✓ Bonding
 - ✓ Welders
- ✓ Controllers
- ✓ **Roadmap**



2007/08


2010

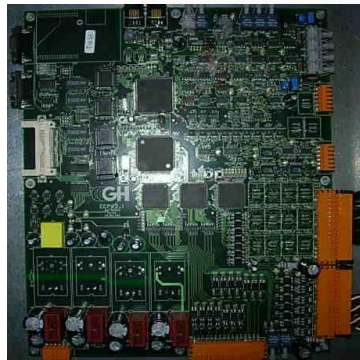

CAN



Digital Parallel Controller

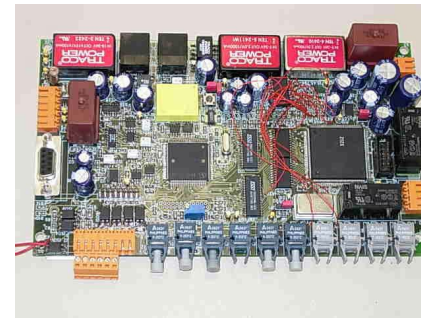


CAN



Full Digital Series/ Parallel
FPGA Controller



CAN

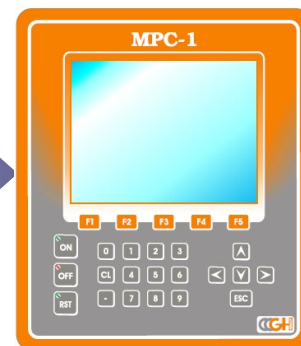

Digital Series Controller

THANK YOU VERY MUCH
FOR YOUR ATTENTION



Escola Tècnica Superior d'Enginyeria



VNIVERSITAT
ID VALÈNCIA 